

MEMS Capacitor Sensor Laboratory

Dr. Lynn Fuller, Dr. Ivan Puchades

Webpage: <http://people.rit.edu/lffeee>

Microelectronic Engineering

Rochester Institute of Technology

82 Lomb Memorial Drive

Rochester, NY 14623-5604


Tel (585) 475-2035

Fax (585) 475-5041

Email: Lynn.Fuller@rit.edu


Department webpage: <http://www.microe.rit.edu>

4-11-13 capacitor_Lab.ppt

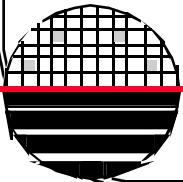

OUTLINE

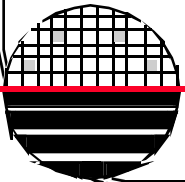Parallel Plate Capacitors – Force/Position Sensor
Water Level Sensor
RC Oscillator
Capacitance to Analog to Digital Output
Resonant LC Wireless Capacitor Sensor
Bluetooth Wireless Capacitor Sensor




CAPACITORS

Capacitor –

$$C = \epsilon_0 \epsilon_r \text{Area}/d$$

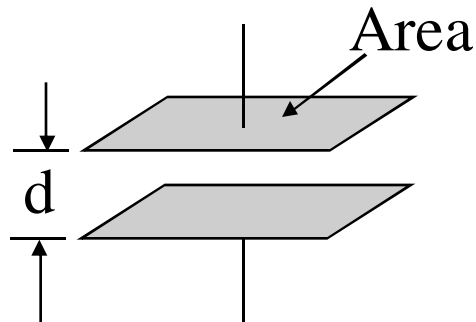
where ϵ_0 is the permittivity of free space
 ϵ_r is the relative permittivity
Area is the overlap area of the two
conductor separated by distance d



$$\epsilon_0 = 8.85\text{E-}14 \text{ F/cm}$$


$$\epsilon_r \text{ air} = 1$$

$$\epsilon_r \text{ SiO}_2 = 3.9$$

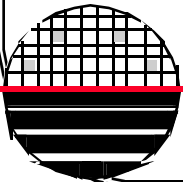



CAPACITOR CALCULATIONS

| | | | | | | | |
|--|--|--|--|----------------------|--|--------------------------|--|
| Rochester Institute of Technology | | | | | | 8-Apr-08 | |
| Dr. Lynn Fuller | | Microelectronic Engineering, 82 Lomb Memorial Dr., Rochester, NY 14623 | | | | | |
| To use this spread sheet enter values in the white boxes. The rest of the sheet is protected and should not be changed unless you are sure of the consequences. The results are displayed in the purple boxes. | | | | | | | |
| Capacitance of Two Parallel Plates | | | | | | | |
| Capacitance = $\epsilon_0 \epsilon_r \text{Area} / d$ | | | | C = | | 3.43E-11 F | |
| ϵ_0 = Permittivity of free space | | | | | | 8.85E-14 F/cm | |
| ϵ_r = relative permittivity = | | | | | | 2 | |
| Area = | | | | | | 5.81E+01 cm ² | |
| number of pairs of plates, N = | | | | | | 1 | |
| distance between plates, d = | | | | | | 3000 μm | |
| If round plates, Diameter = | | | | | | 0 μm | |
| If rectangular plates, length = | | | | | | 7.62E+04 μm | |
| If rectangular plates, width = | | | | | | 7.62E+04 μm | |
| Force Between Two Parallel Plates | | | | Force = | | 5.71E-07 N | |
| Electrostatic Force = $\epsilon_0 \epsilon_r \text{Area} V^2 / 2d$ | | | | Applied Voltage, V = | | 10 volts | |

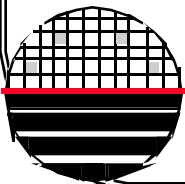

CAPACITANCE BETWEEN TWO PLATES

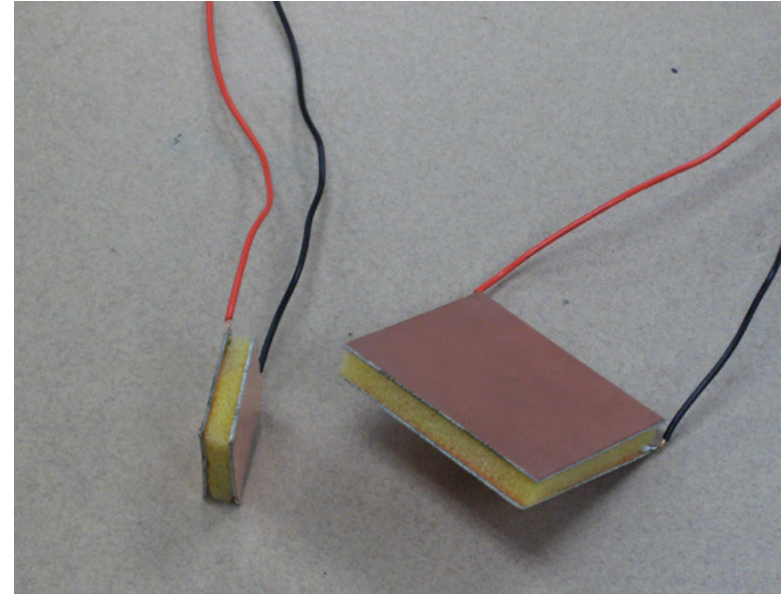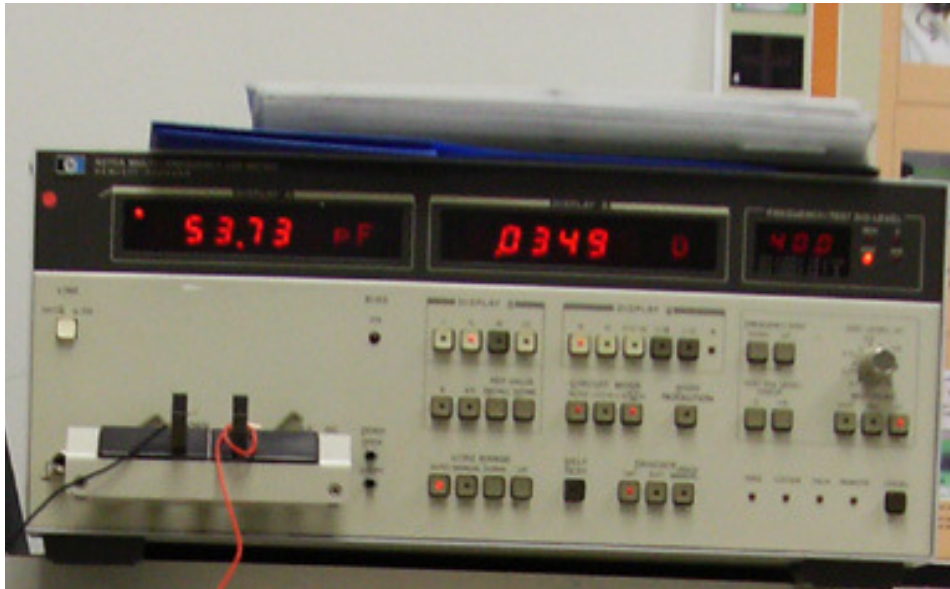
Design and build capacitors made of two metal plates separated by a thin foam insulator that can be compressed for various applied forces. Calculate capacitance and measure capacitance, compare results to theoretical.



Capacitance of two wires 3' long

Capacitance of 2" x 2" plates 1/2" gap

Capacitance of 1" x 1" plates 1/4" gap

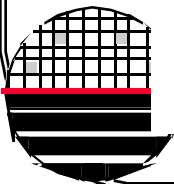


$\epsilon_r \text{ air} < \epsilon_r \text{ foam} < \epsilon_r \text{ rubber}$
 $1 < \epsilon_r \text{ foam} < 3$

CAPACITIVE FORCE SENSOR



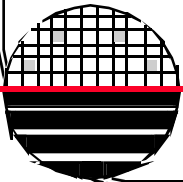Rochester Institute of Technology
Microelectronic Engineering




LIQUID LEVEL CAPACITOR SENSOR

Calculate Capacitance,
3" x 3" plates
1/32" gap

Measure Capacitance
Immersed in Water
at 1/2, 1, 1 1/2 and 2"

$\epsilon_r = \sim 80$ for water

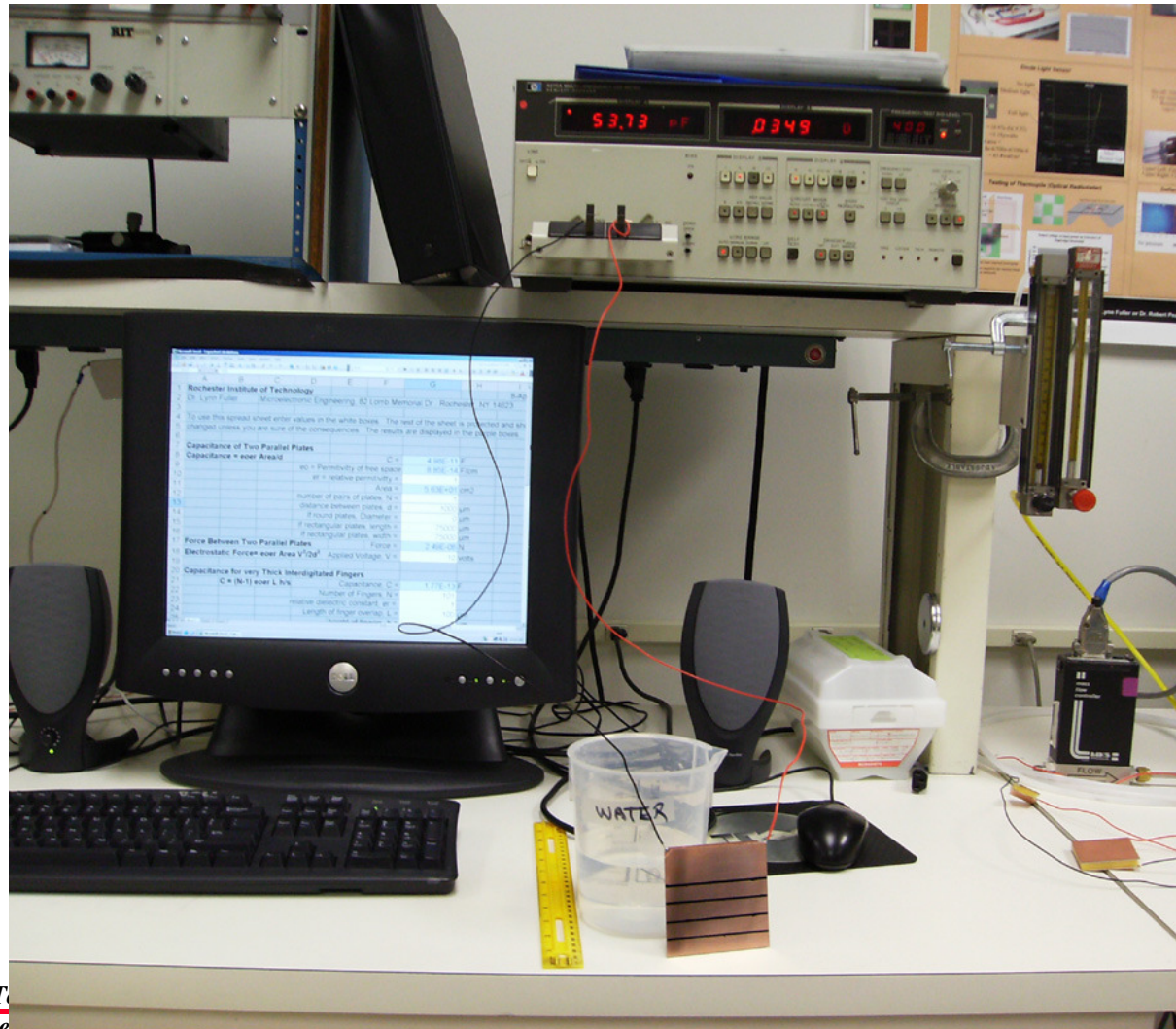


CAPACITIVE WATER LEVEL SENSOR




**Capacitive Water Level
Sensor**

Dr. Lynn Fuller


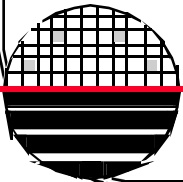


*Rochester Institute of Technology
Microelectronic Engineering*

COMPARATOR

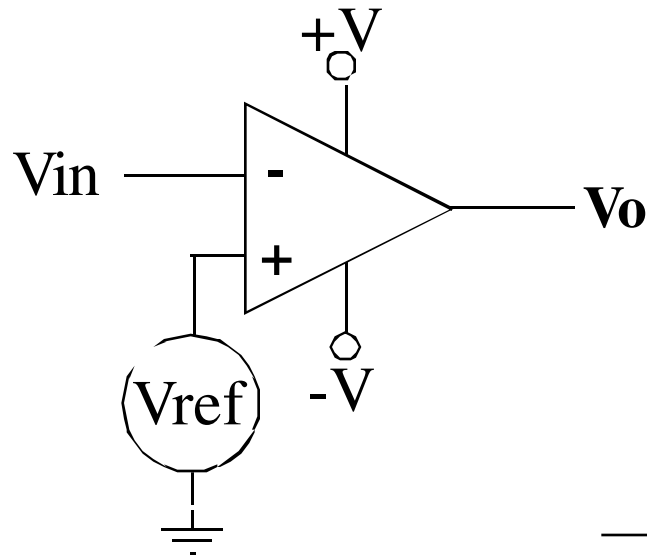

Theoretical


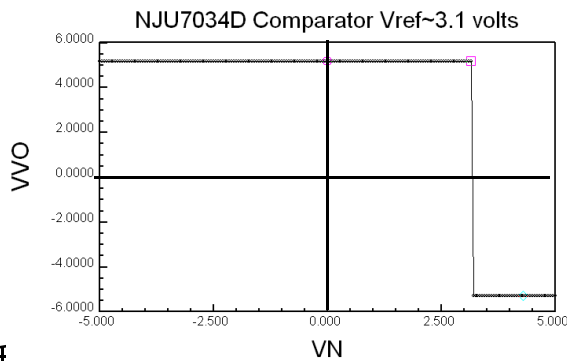
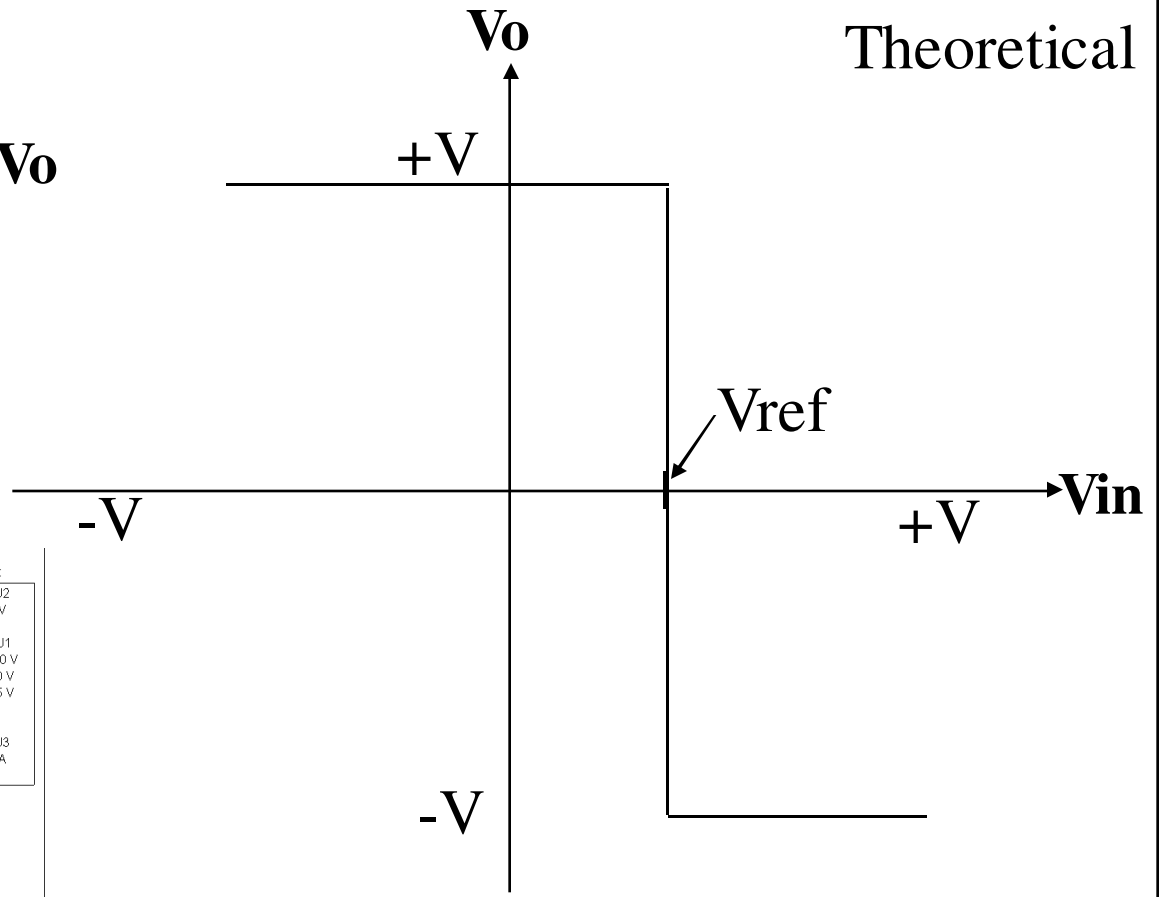


Conditions:
 Con: SMU2
 Val: 3.00 V
 Swp: SMU1
 Start: -5.00 V
 Stop: 5.00 V
 Step: 0.05 V
 Pts: 201
 Con: SMU3
 Val: 0.00 A

Measured

| Fit #1 | Fit #2 | Cursors: X | Y |
|--------|--------|------------|-------|
| None | None | 3.15 | 5.15 |
| **** | **** | 4.30 | -5.30 |
| **** | **** | 0.00 | 5.15 |




BISTABLE CIRCUIT WITH HYSTERESIS

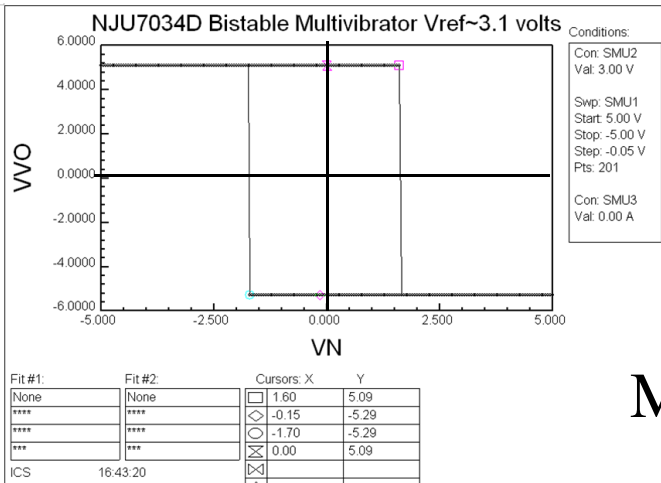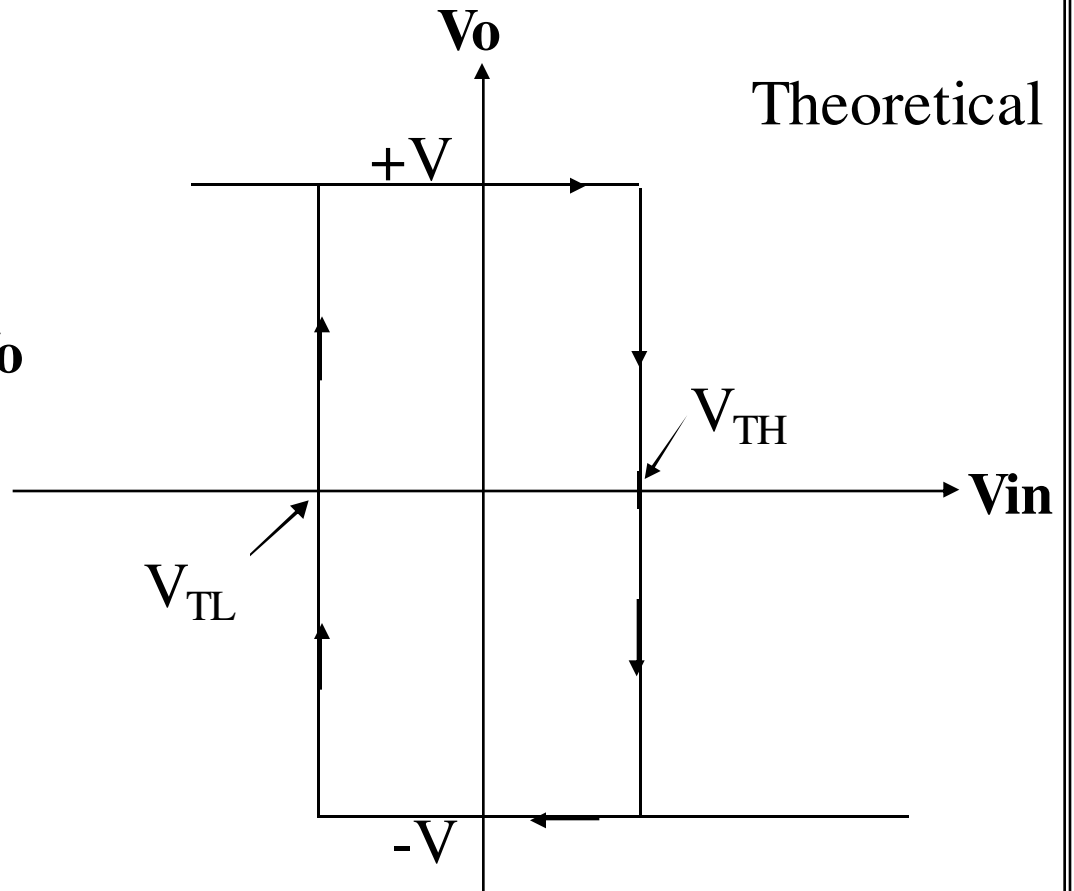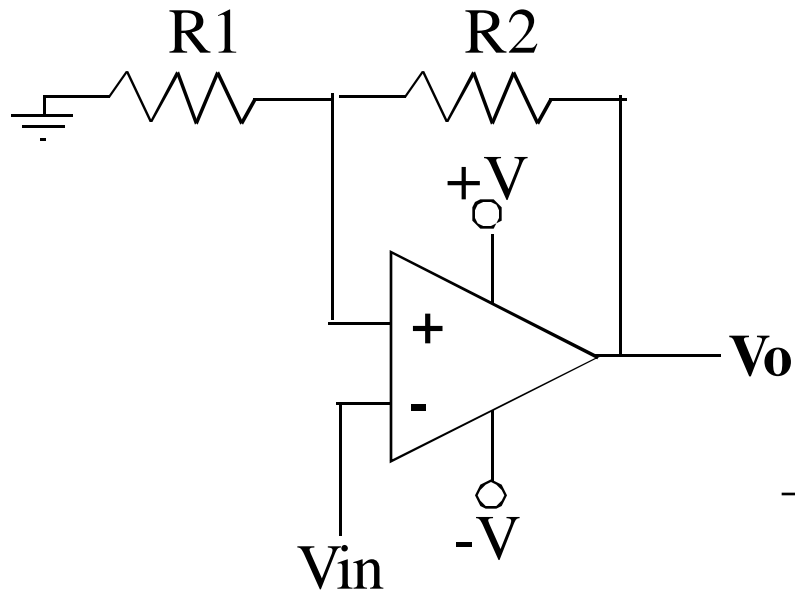

Measured


Sedra and Smith pg 1187

RC INTEGRATOR

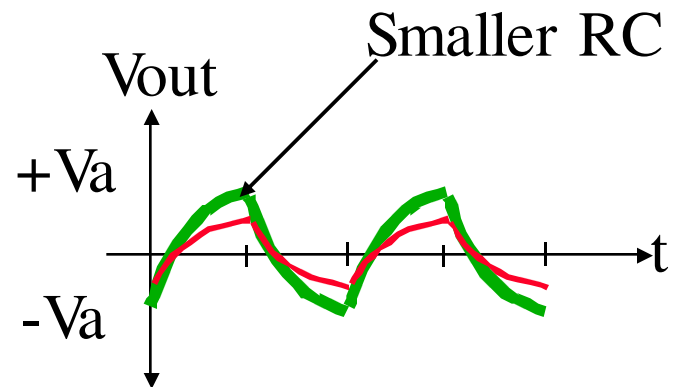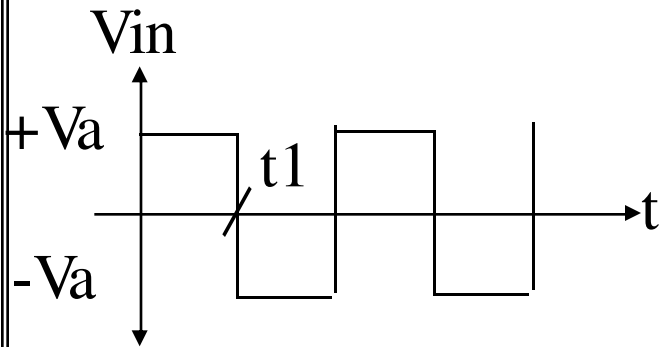
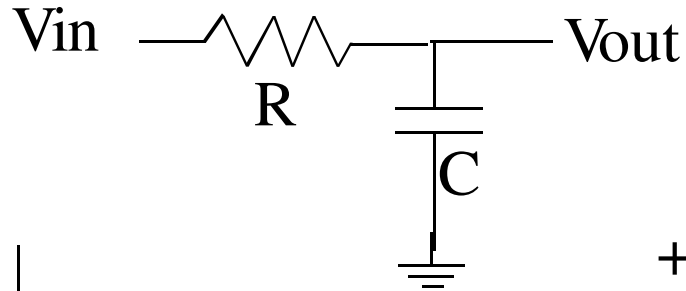


$$V_{out} = (-V_a) + [2V_a(1 - e^{-t/RC})] \quad \text{for } 0 < t < t_1$$

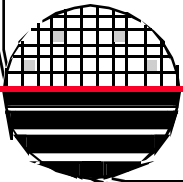
If $R=1\text{MEG}$ and $C=10\text{pF}$ find $RC=10\mu\text{s}$
 so t_1 might be $\sim 20\mu\text{s}$



OSCILLATOR (MULTIVIBRATOR)

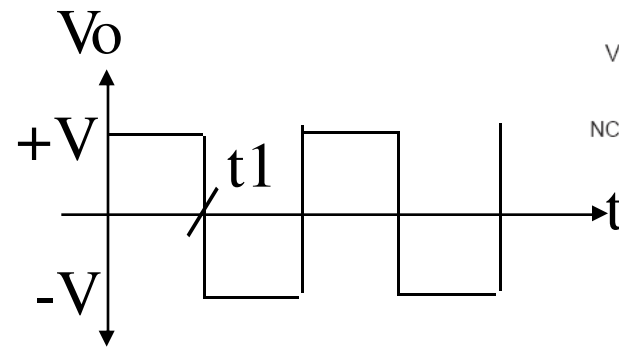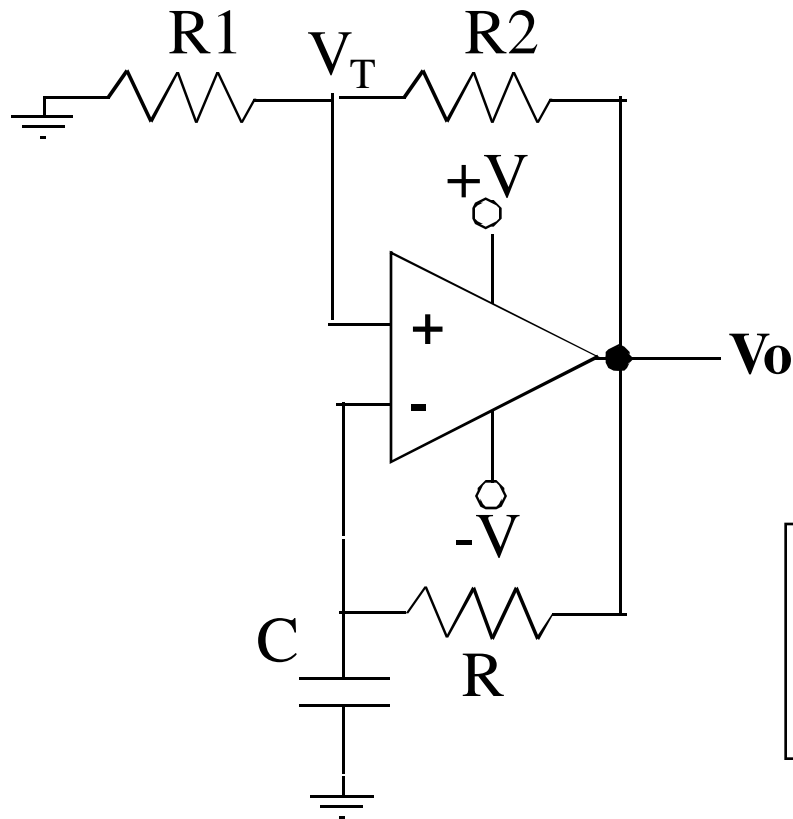

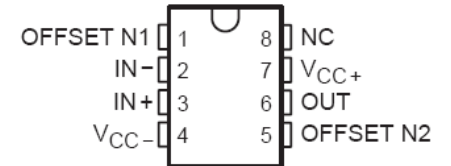
TL081, TL081A, TL081B
D, P, OR PS PACKAGE
(TOP VIEW)




NC - No internal connection

$$\text{Period} = T = 2RC \ln \left(\frac{1 + V_T/V}{1 - V_T/V} \right)$$

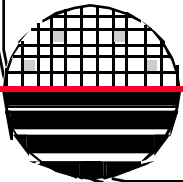
Bistable Circuit with Hysteresis and RC Integrator




OSCILLATOR OUTPUT

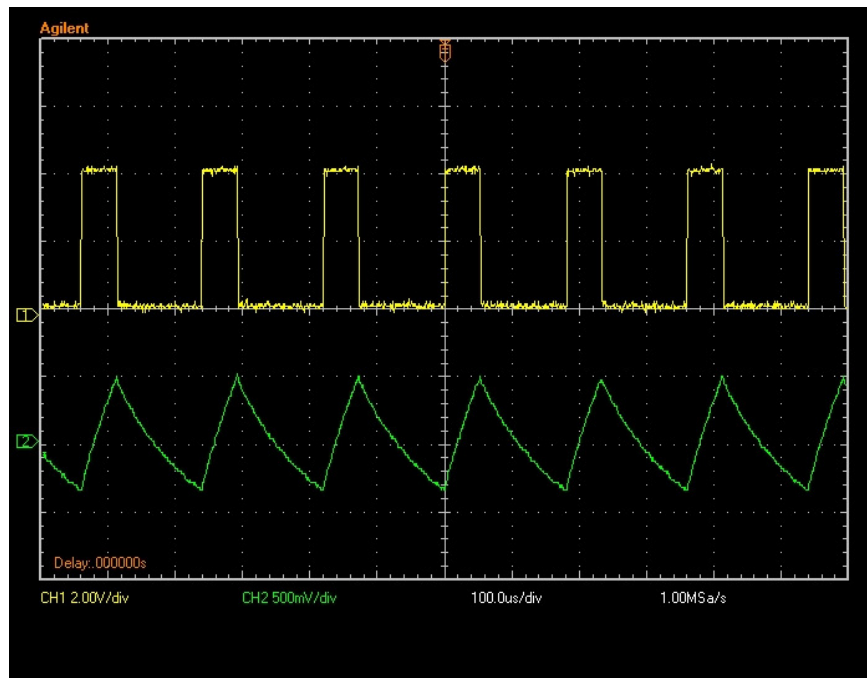

1.2 Mohm No Force Applied C ~50pf

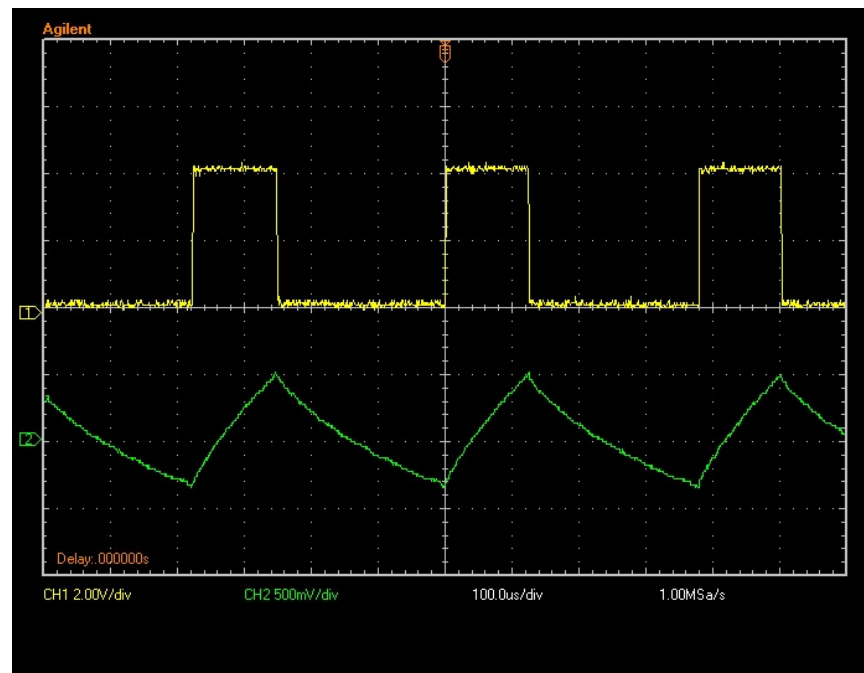


1.2 Mohm with Force Applied C~100pf

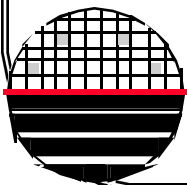


CAPACITIVE SENSOR AND RC OSCILLATOR

**Capacitor Sensor
RC Oscillator**



**Dr. Lynn Fuller
Ivan Puchades**

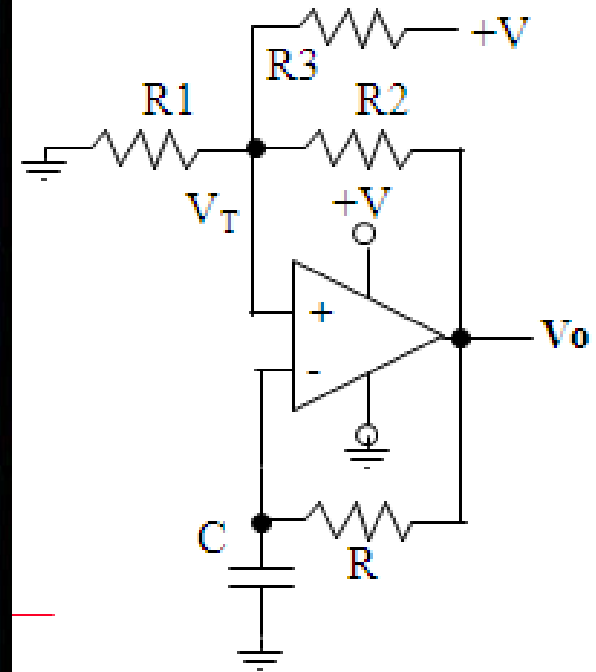

*RC Oscillator
movie*

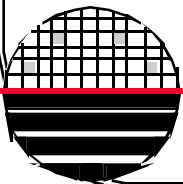

BASIC IDEA

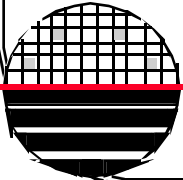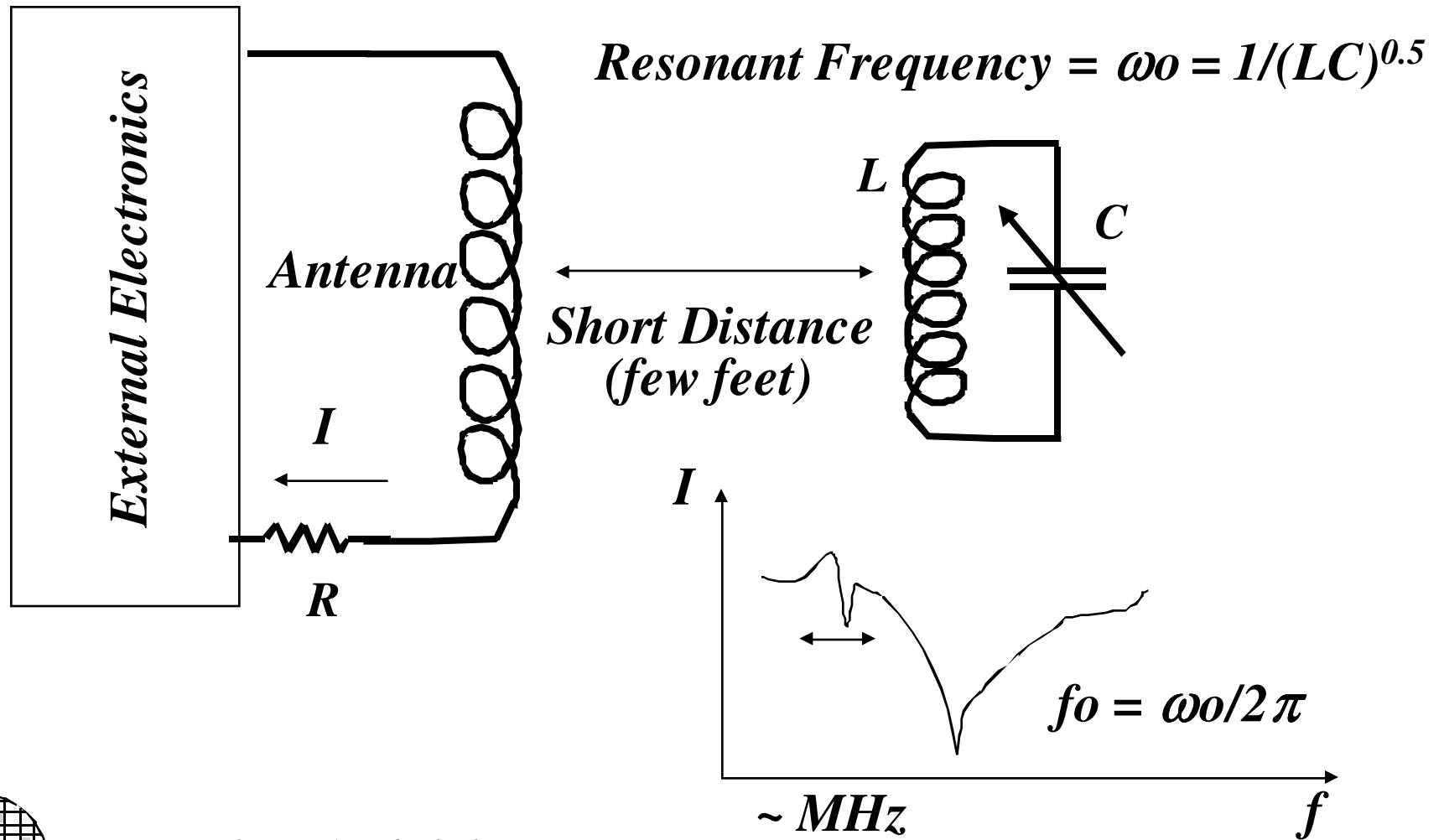


INVESTIGATE RESONANT LC CIRCUIT



Network Analyzer




I vs. Frequency

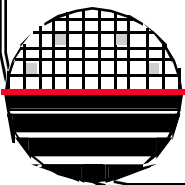

PICKUP COIL CURRENT WITHOUT RESONANT CIRCUIT

REF LEVEL /DIV MARKER 41 500 000.000Hz
0.000dBm 10.000dB MAG(R) -62.626dBm

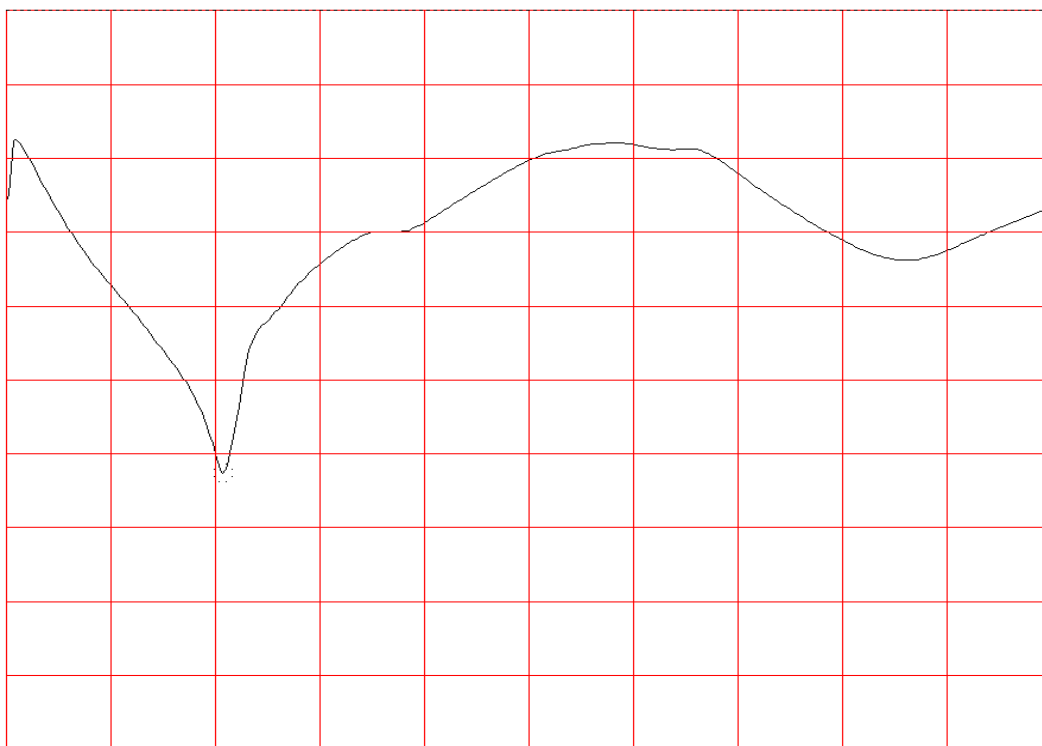

START 0.000Hz STOP 200 000 000.000Hz
AMPTD -10.0dBm
4/11/2013 9:05:57 AM


Rochester Institute of Technology
Microelectronic Engineering

PICKUP COIL CURRENT WITH RESONANT CIRCUIT

REF LEVEL 0.000dBm /DIV 10.000dB MARKER 41 500 000.000Hz
MAG(R) -61.426dBm


Resonant Frequency

$$\omega_0 = 1/(LC)^{0.5}$$

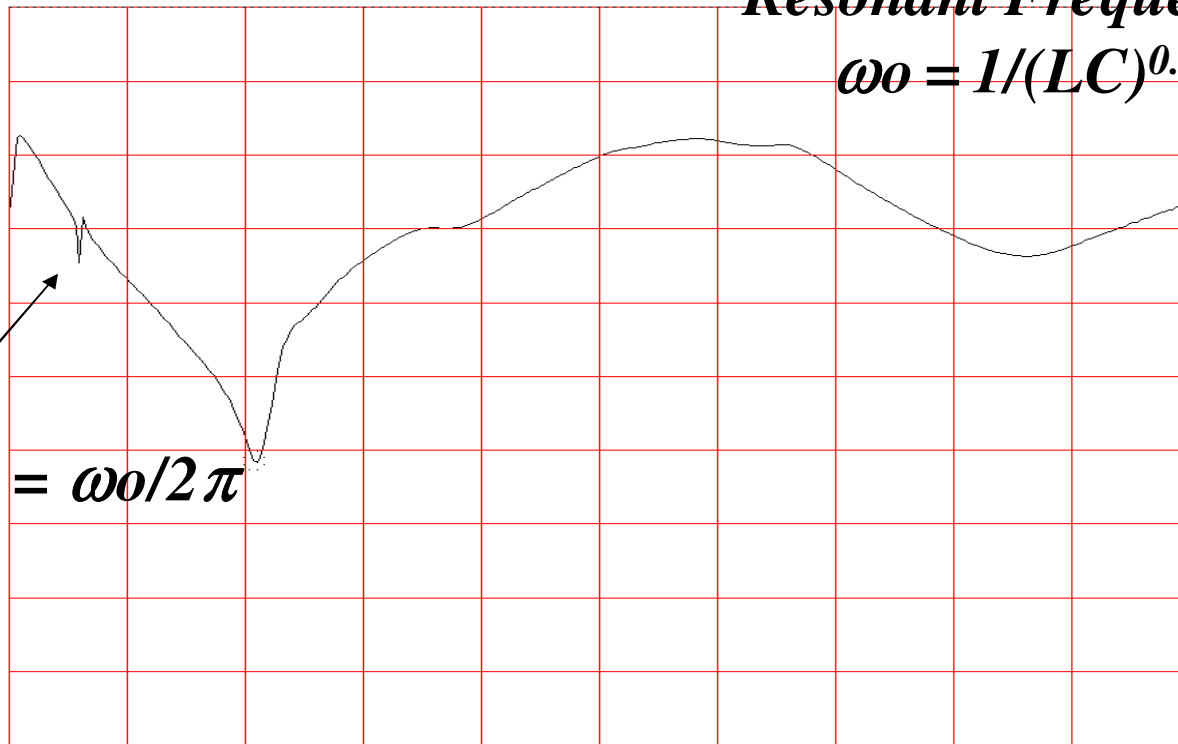

Due to, $f_0 = \omega_0/2\pi$

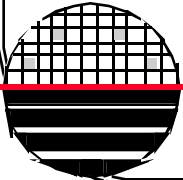START 0.000Hz STOP 200 000 000.000Hz
AMP/DIV -10.000dBm




ZOOM IN ON RESONANCE DUE TO LC

REF LEVEL / DIV MARKER 11 837 500.000Hz
-22.000dBm 2.000dB MAG (R) -34.388dBm


Resonant Frequency

$$\omega_0 = 1/(LC)^{0.5}$$

$$f_0 = \omega_0/2\pi$$

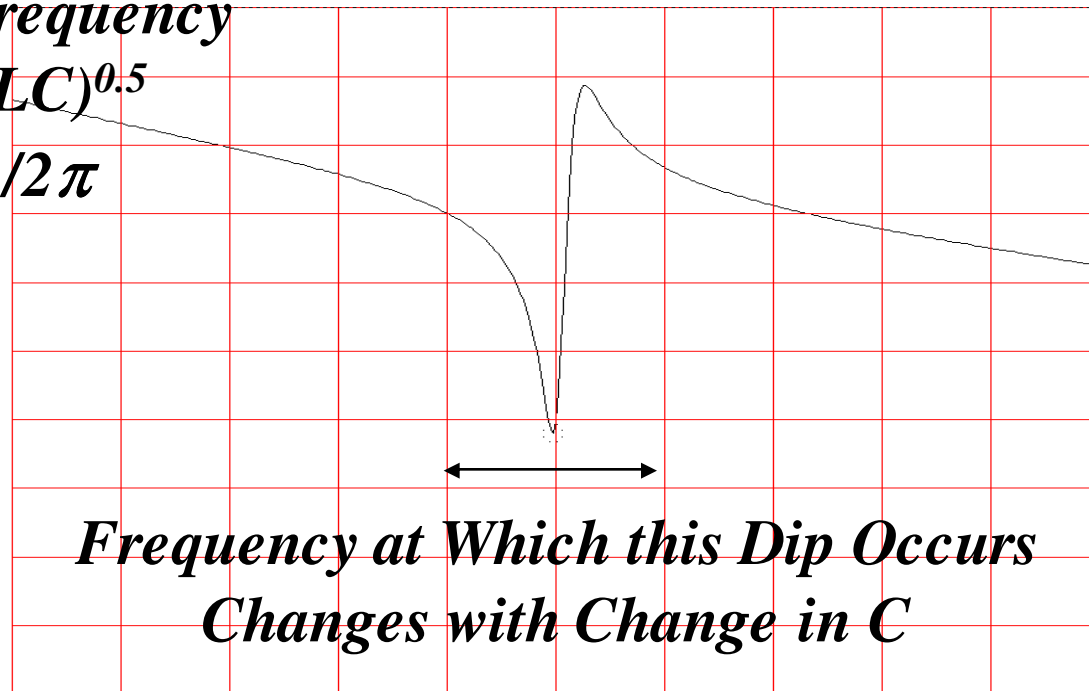


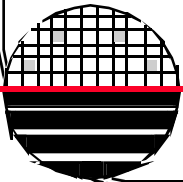CENTER 11 850 000.000Hz SPAN 5 000 000.000Hz
AMP TD 0.2419 dBm





RESONANT LC SENSOR FOR TEMPERATURE


BATMON
movie

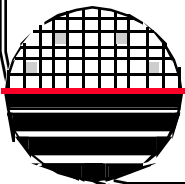


CAPACITANCE TO ANALOG VOLTAGE TO DIGITAL

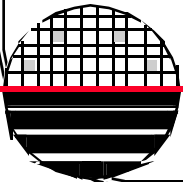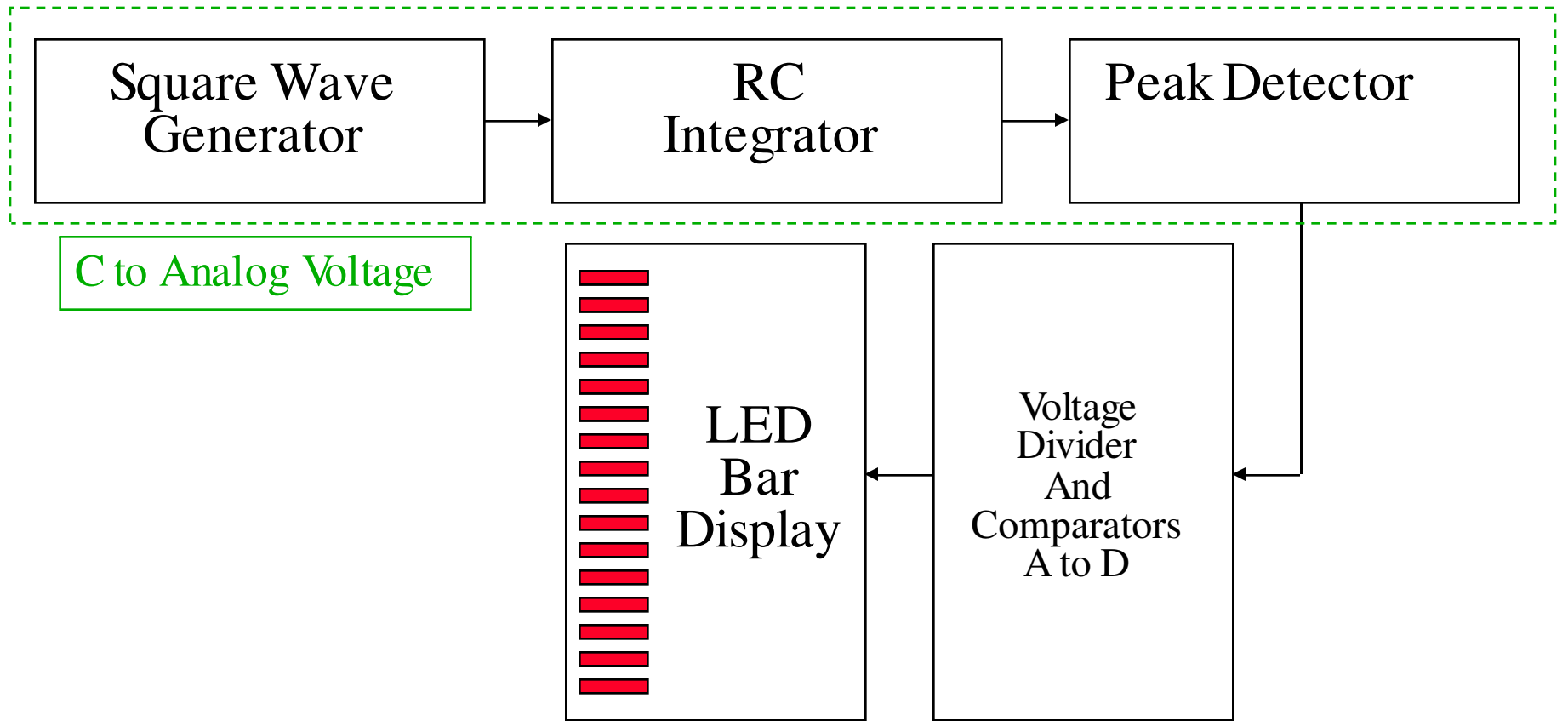


CAPACITOR SENSOR ELECTRONICS

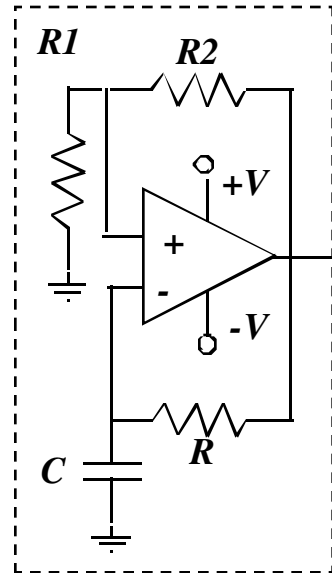


Square Wave Generator

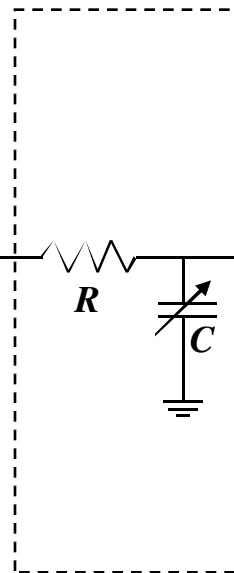


RC Integrator

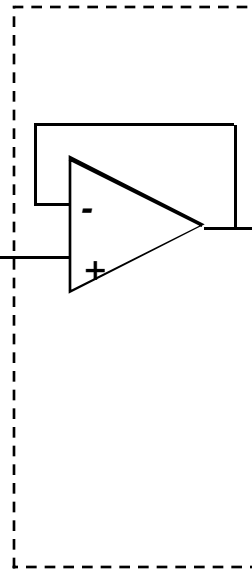


Buffer

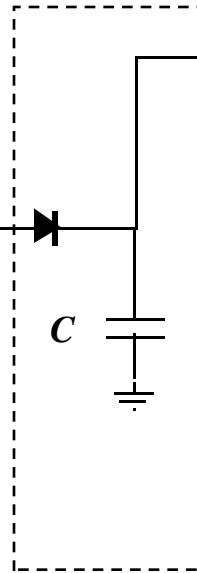

Peak Detector

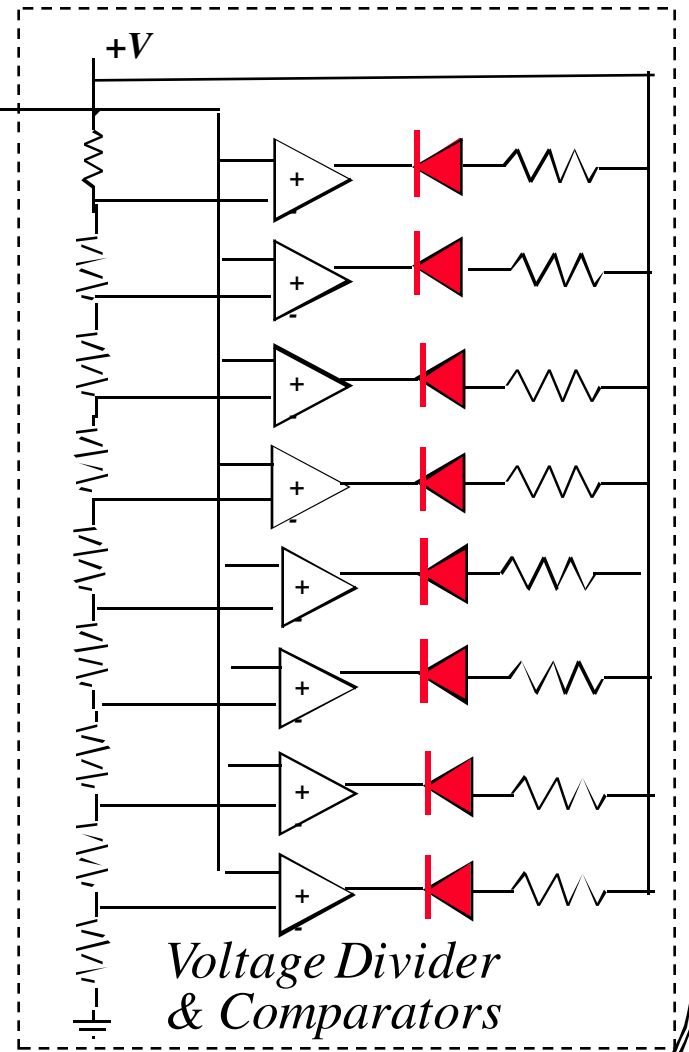


Voltage Divider & Comparators

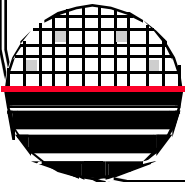

CAPACITANCE SENSOR AND SIGNAL CONDITIONING


**Capacitor Pressure
Sensor**

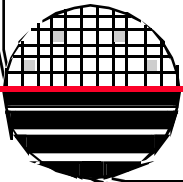**Dr. Lynn Fuller
Ivan Puchades
Ellen Sedlack**



*Rochester Institute of Technology
Microelectronic Engineering*

BLUETOOTH WIRELESS CAPACITOR SENSOR

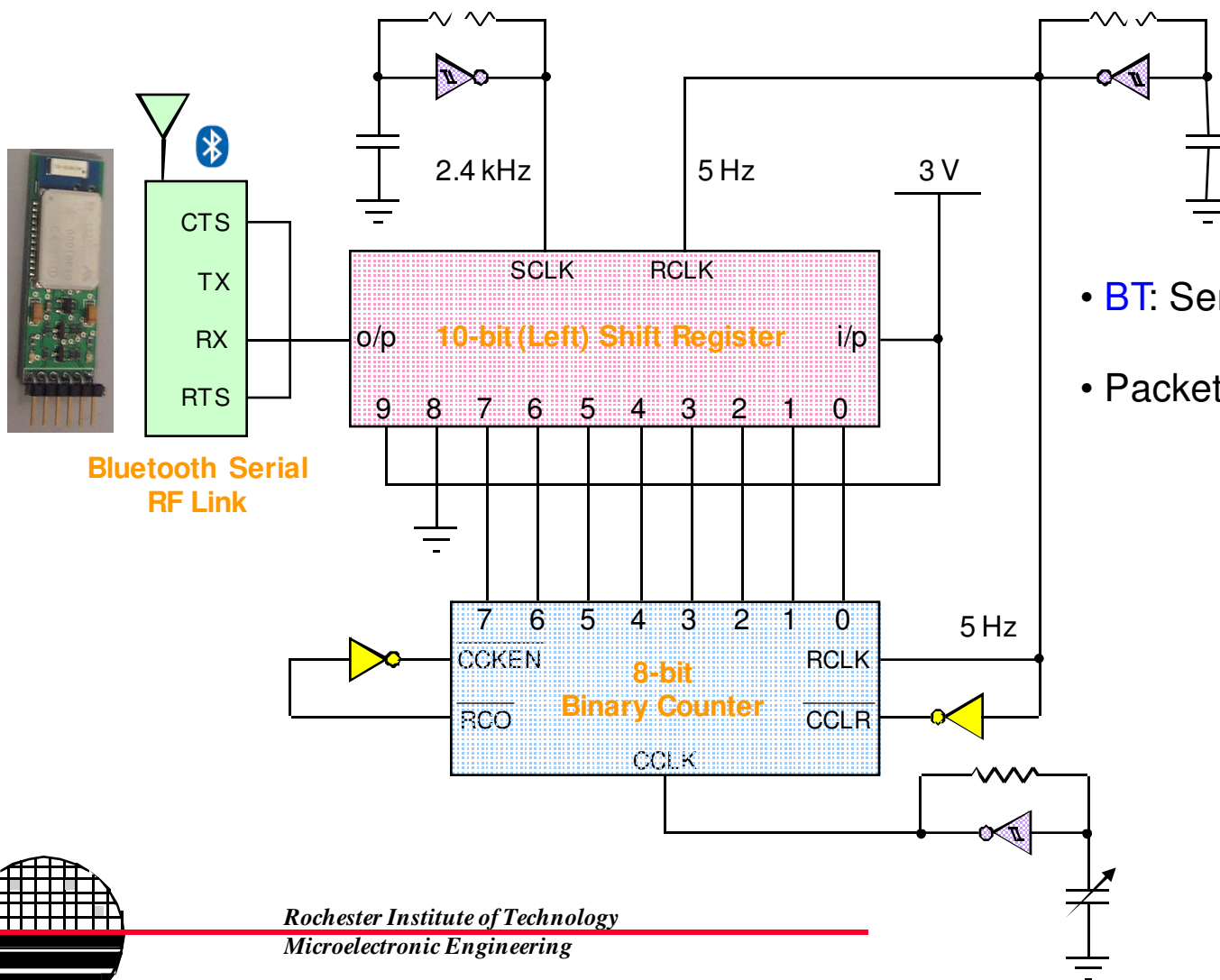

Bluetooth Serial
RF Link

- BT: Serial Port Profile (RS232)

- Packet Specification :


Baud rate: 2400

Data bits: 8


Parity: None

Stop bits: 1

BLUETOOTH WIRELESS CAPACITOR SENSOR

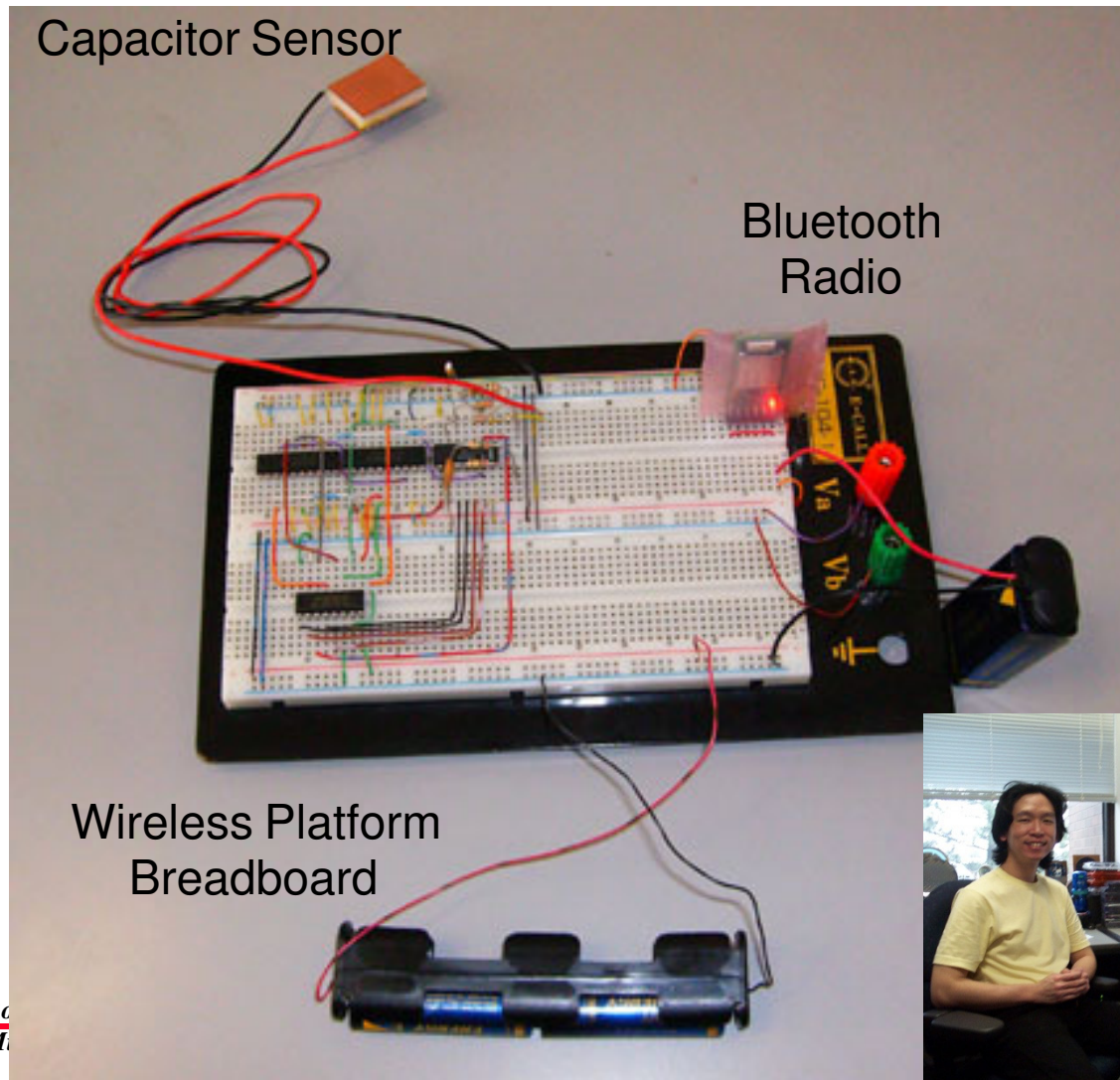


Ro
M

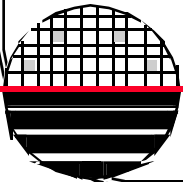


REFERENCES

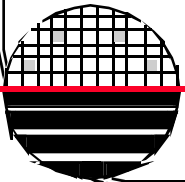1. Mechanics of Materials, by Ferdinand P. Beer, E. Russell Johnston, Jr., McGraw-Hill Book Co.1981, ISBN 0-07-004284-5
2. Electromagnetics, by John D Kraus, Keith R. Carver, McGraw-Hill Book Co.1981, ISBN 0-07-035396-4
3. Fundamentals of Microfabrication, M. Madou, CRC Press, New York, 1997
4. Mechanics of Materials, by Ferdinand P. Beer, E. Russell Johnston, Jr., McGraw-Hill Book Co.1981, ISBN 0-07-004284-5
5. Switched Capacitor Circuits, Phillip E. Allen and Edgar Sanchez-Sinencio, Van Nostrand Reinhold Publishers, 1984.



HOMEWORK - CAPACITOR SENSOR LAB

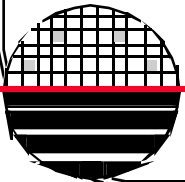1. Calculate the capacitance of the two parallel plate sensors with foam between the plates.
2. Calculate the change in capacitance for a capacitive analog oil level sensor.
3. Calculate the capacitance for a silicon diode at 25, 50, 75, and 100°C.



INSTRUCTORS NOTES: CAPACITOR SENSORS

1. Calculate the capacitance of a parallel plate capacitor.
2. Measure it.
3. Move the plate spacing, measure it.
4. Measure height of water.
5. Build RC Oscillator for measuring C.
6. Other ways to measure Capacitance
 - 6.1 Resonant Frequency
 - 6.2 Peak Detector
 - 6.3 Blue Tooth Wireless

