

**ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING**

Combinatorial and Sequential CMOS Circuits

Dr. Lynn Fuller

Webpage: <http://people.rit.edu/lffeee>

Microelectronic Engineering

Rochester Institute of Technology

82 Lomb Memorial Drive

Rochester, NY 14623-5604

Tel (585) 475-2035

Fax (585) 475-5041


Email: Lynn.Fuller@rit.edu

Department webpage: <http://www.microe.rit.edu>

10-31-2014 Combinational_Sequential_Circuits.ppt


ADOBE PRESENTER

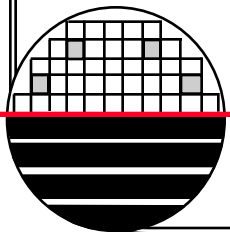This PowerPoint module has been published using Adobe Presenter. Please click on the **Notes** tab in the left panel to read the instructors comments for each slide. Manually advance the slide by clicking on the **play** arrow or pressing the **page down** key.




OUTLINE

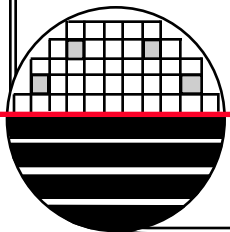Inntroduction
VTC of NAND and NOR
CMOS AND-OR-INVERT Gate
XOR and XNOR
Encoder, Decoder, Multiplexer, Demultiplexer
Set-Reset Latch
Flip-Flop
Power Dissipation
Energy and Delay
References
Homework





INTRODUCTION

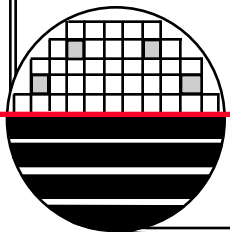In this module we want to look at combining transistors to make CMOS logic gates. In general we want the logic gate to function correctly for static operation, we want the noise margin to be similar to that of the CMOS inverter and the speed at which the gate operates to be similar to that of the CMOS inverter.





CMOS NOR AND NAND

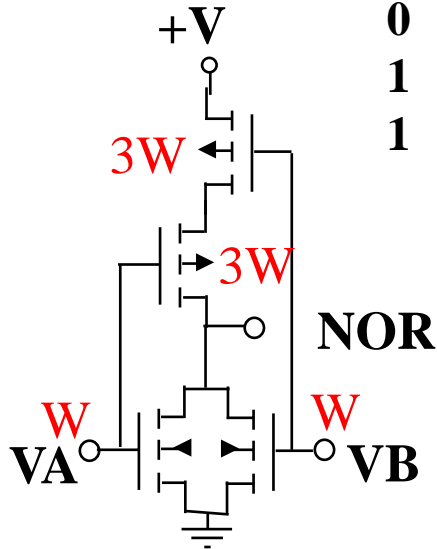
 
The design guideline is that the logic gate under consideration should have the same rise time and fall time as the inverter (after we adjusted the inverter for equal rise time and fall time. Assume L 's are the same. $(W/L)_{\text{pullup}} = \sim 1.5 (W/L)_{\text{pulldown}}$ based on mobility only



VA	VB	NOR	NAND
0	0	1	1
0	1	0	1
1	0	0	1
1	1	0	0

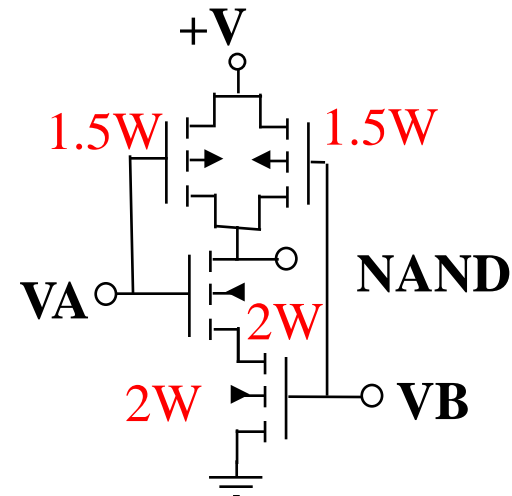 

VTC FOR CMOS NOR AND NAND

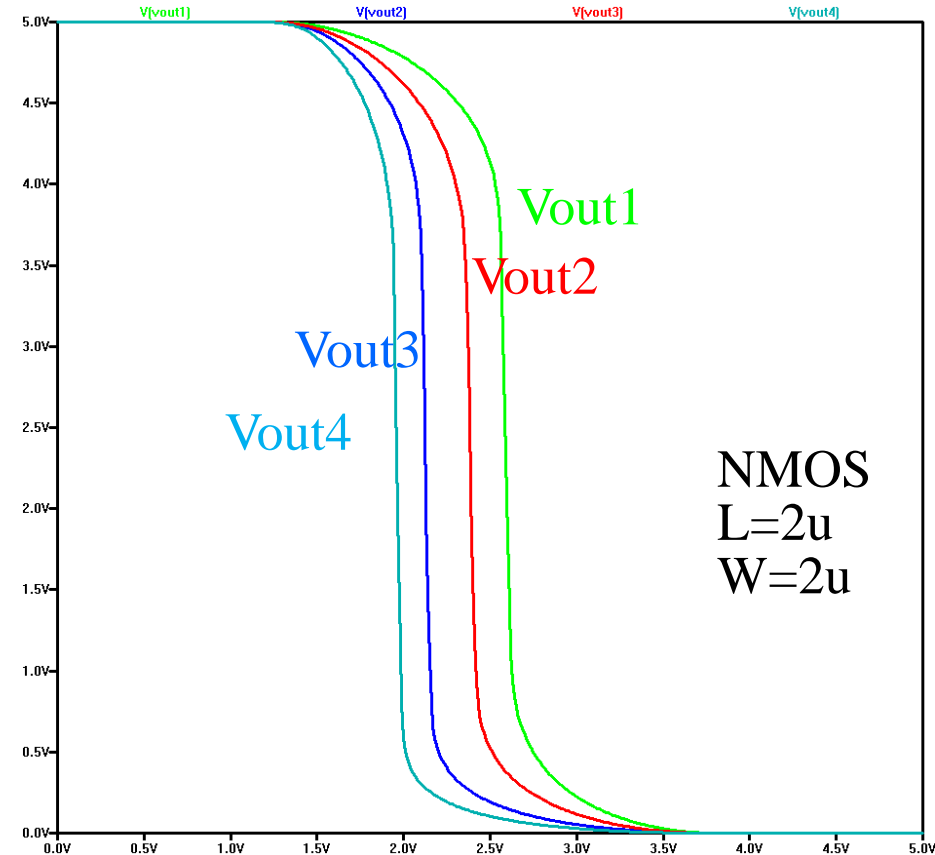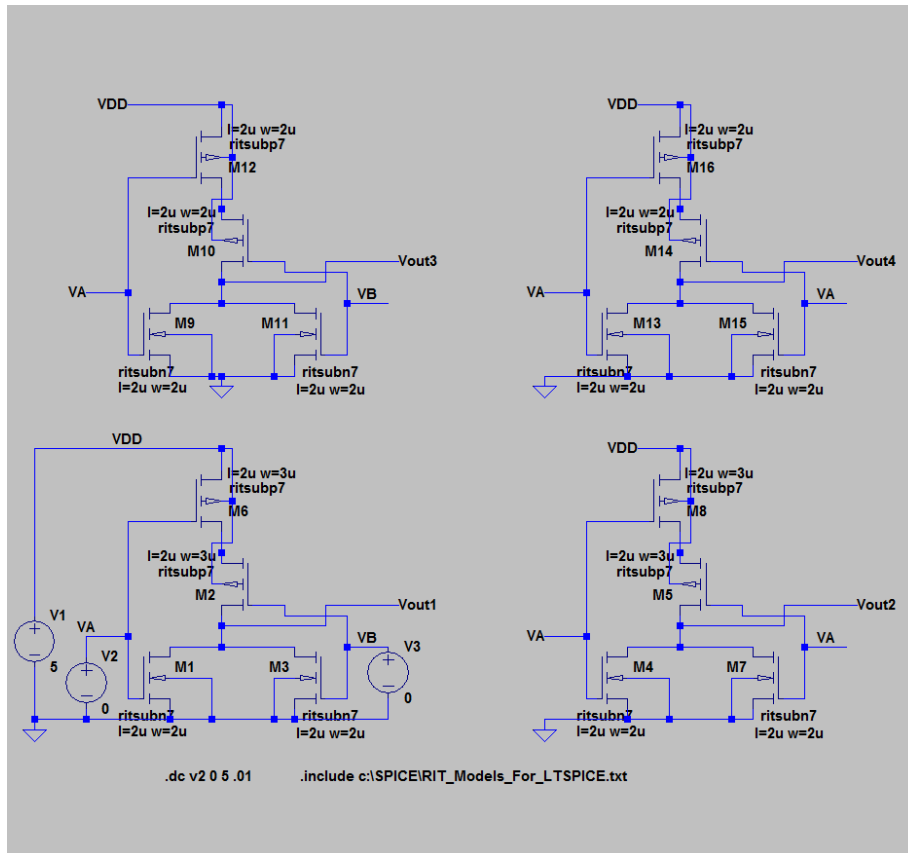

Vout1 PMOS $L=2\mu, W=3\mu$, VA Sweep 0 to 5, VB=zero

Vout2 PMOS $L=2\mu, W=3\mu$, VA Sweep 0 to 5, VB=VA




Vout3 PMOS $L=2\mu, W=2\mu$, VA Sweep 0 to 5, VB=zero

Vout4 PMOS $L=2\mu, W=2\mu$, VA Sweep 0 to 5, VB=VA

VTC FOR 3-INPUT NAND

The three NMOS transistors each have different source to substrate voltages which will change the threshold voltage of those transistors and as a result will change the VTC depending on which transistors are switching. This causes a horizontal shift in the VTC.

VA	VB	VC	NAND
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

  
 


3-INPUT NAND

3-Input NAND - Body Effect

```
.dc v4 0 5 .01
```
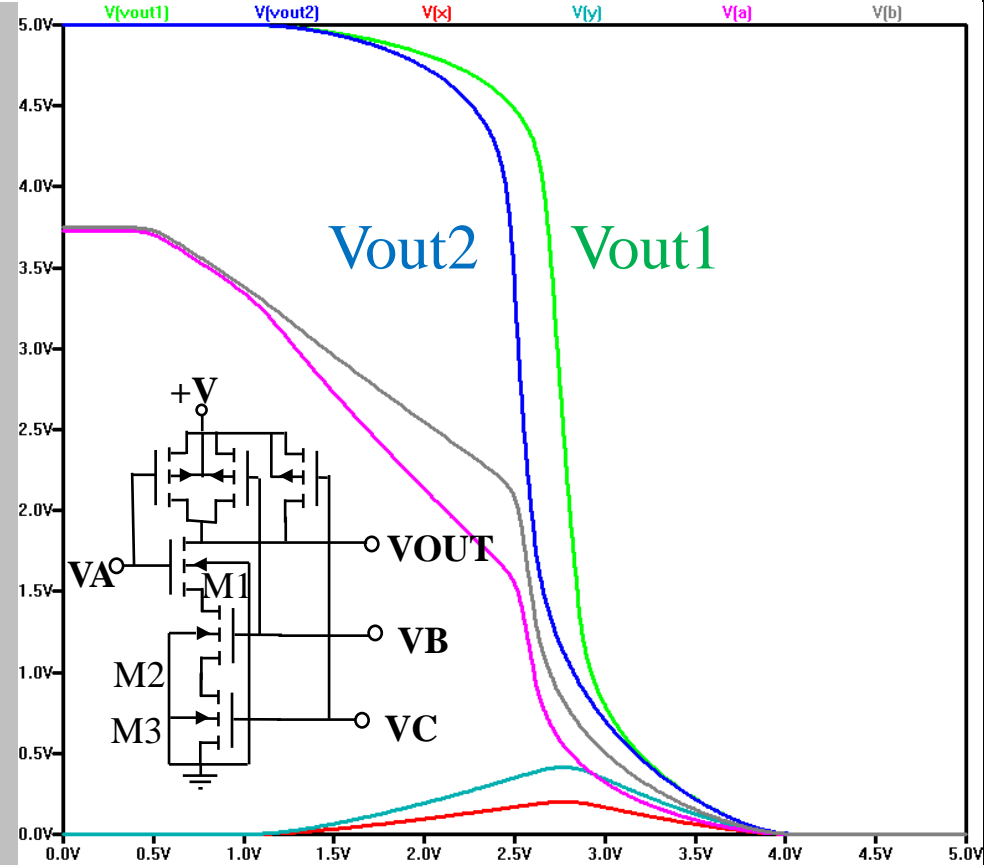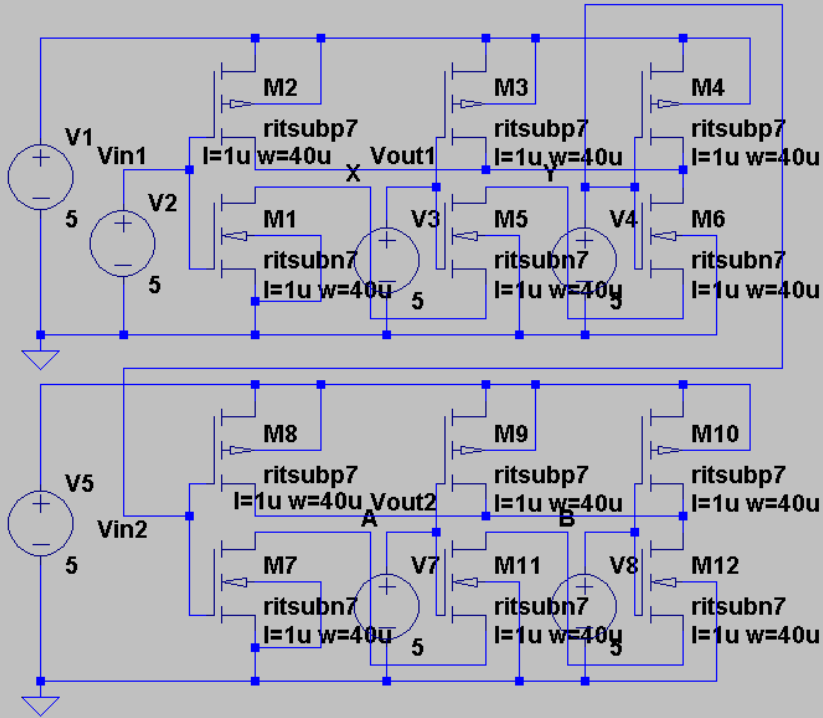
```
.include c:\SPICE\RIT_Models_For_LTSPICE.txt
```




Vout1 has M2 and M3 NMOS on and M1 NMOS switching
Vout2 has M1 and M2 NMOS on and M3 NMOS switching
 Other combinations are also possible.

FAN IN AND FAN OUT CONSIDERATIONS

Fan in refers to the number of inputs to a gate. It is common to have up to 8 inputs. In CMOS this implies that there are 8 transistors in parallel and 8 transistors in series. The 8 in parallel is not necessarily a problem but the 8 in series is because of the body effect on the threshold voltage of some of the transistors if they are all in the same well (at V_{ss} or V_{dd} for p-well or n-well respectively)


Fan-In = 6

 

FAN OUT CONSIDERATIONS




Fan out refers to the number of gates connected to the output of a gate. Each gate adds more capacitance to be charged or discharged during switching which has implications on rise time, fall time and gate delay. The size (W and L) of the MOSFETS can be made to keep the gate delay small.

Fan-Out = 6

 


PSEUDO – CMOS

   There are situations where we want a large number of inputs. Rather than have CMOS where there will be many transistors in series (which will not work) we can use a single PMOS/NMOS transistor that is always on.




OTHER BASIC LOGIC GATES


AND

 


VA	VB	VOUT
0	0	0
0	1	0
1	0	0
1	1	1

 


OR

 

VA	VB	VOUT
0	0	0
0	1	1
1	0	1
1	1	1

 


3 INPUT AND

 

VA	VB	VC	VOUT
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

3 INPUT OR

 

VA	VB	VC	VOUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

OTHER BASIC LOGIC GATE REALIZATIONS

Enhancement Load

V++ Gate Enhancement Load


Depletion Load

Pseudo CMOS NAND, NOR


CMOS AND-OR-INVERT Gate

Generalized Complex CMOS Gate

 
More Complex Gates, XOR, MUX,
Encoder, Decoder, etc.



CMOS AND-OR-INVERT GATE

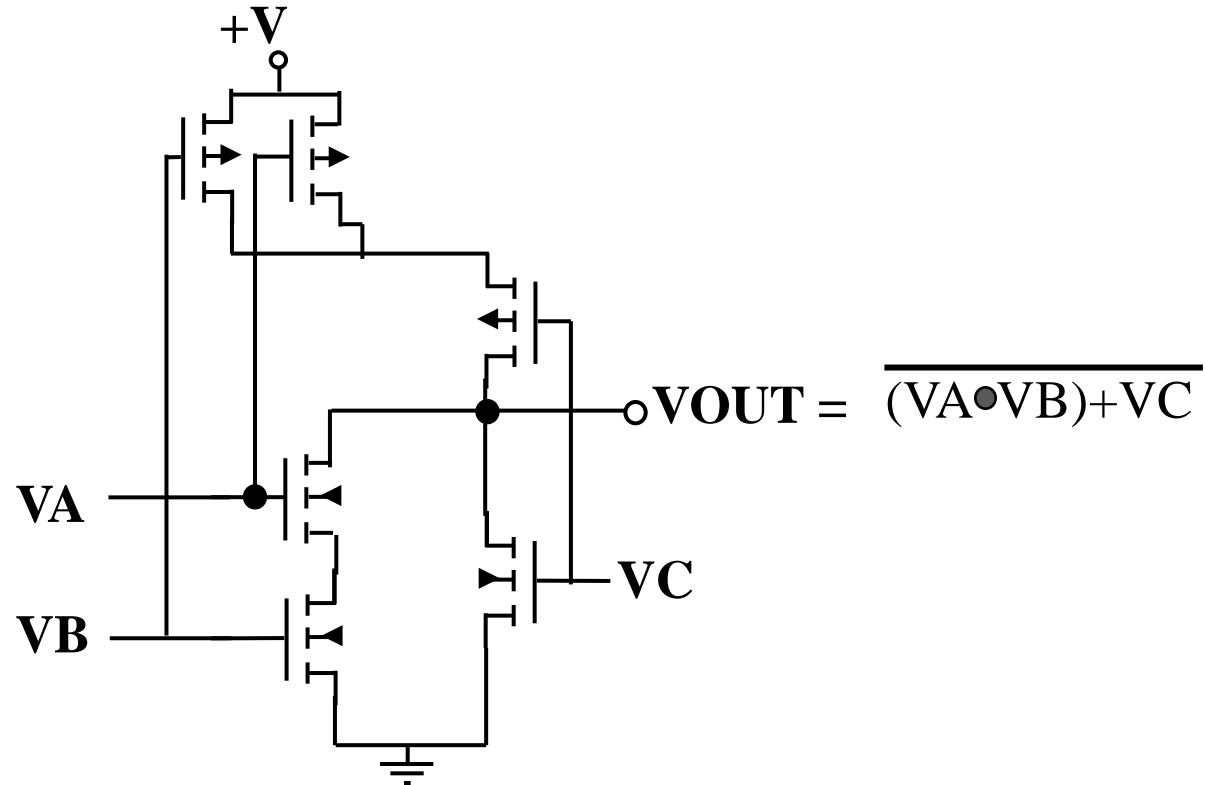


GENERALIZED COMPLEX GATE

 

$$F = \overline{(V_A + V_B)} \bullet V_C$$

Design a gate that provides this output

 


EXCLUSIVE OR (XOR) DESIGN EXAMPLE

Functional Description – This digital logic circuit returns a true (high) value when one of two inputs is high and returns a false (zero) otherwise.


Truth Table

Exclusive OR XOR	V_A	V_B	V_{OUT}
	0	0	0
	0	1	1
	1	0	1
	1	1	0


Gate Level Design

 

GATE LEVEL SIMULATION OF XOR – AND/OR

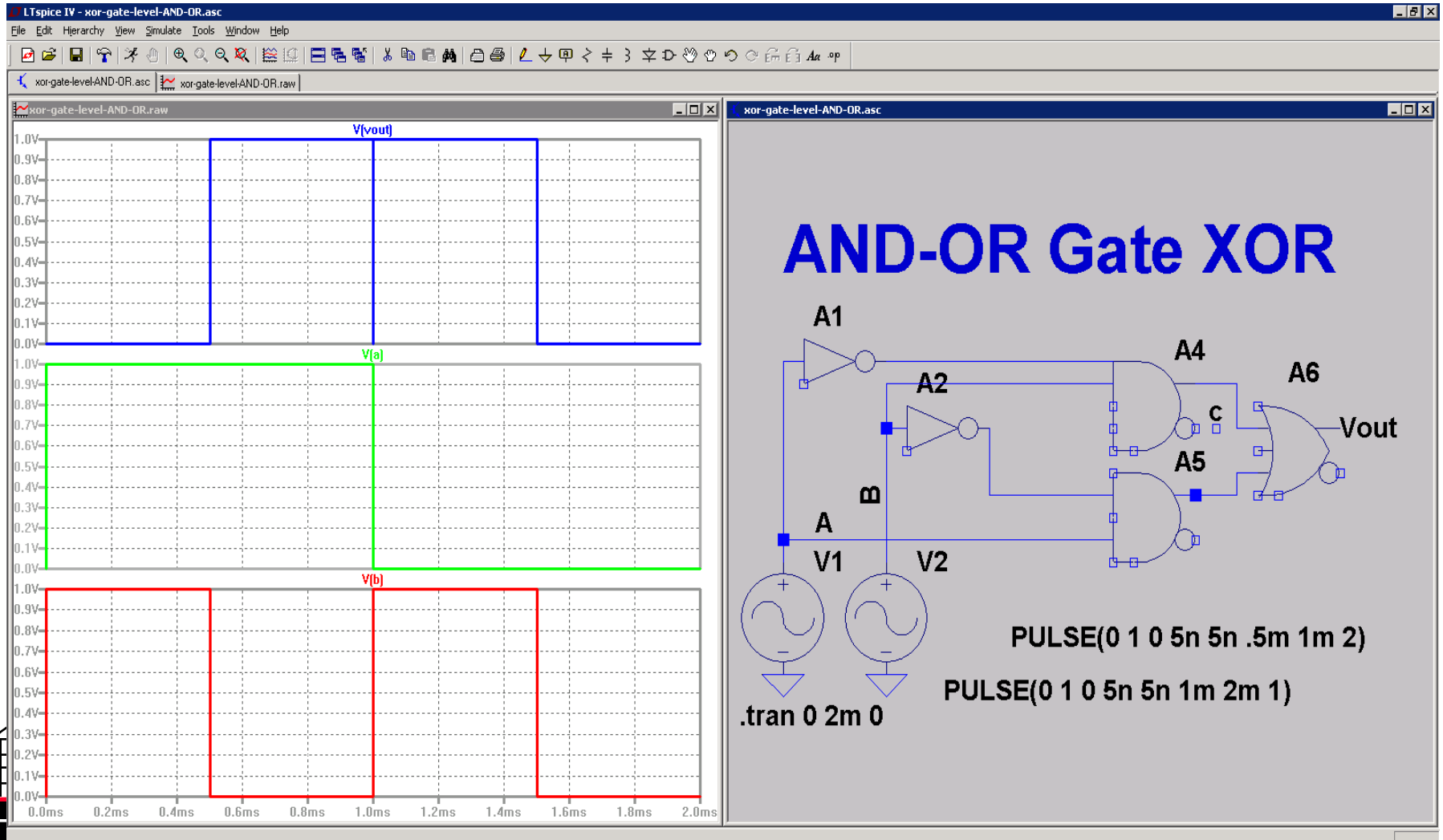


NOR CIRCUIT REALIZATION FOR XOR

 


Exclusive OR
XOR

V_A	V_B	V_{OUT}
0	0	0
0	1	1
1	0	1
1	1	0

GATE LEVEL SIMULATION OF XOR – ALL/NOR

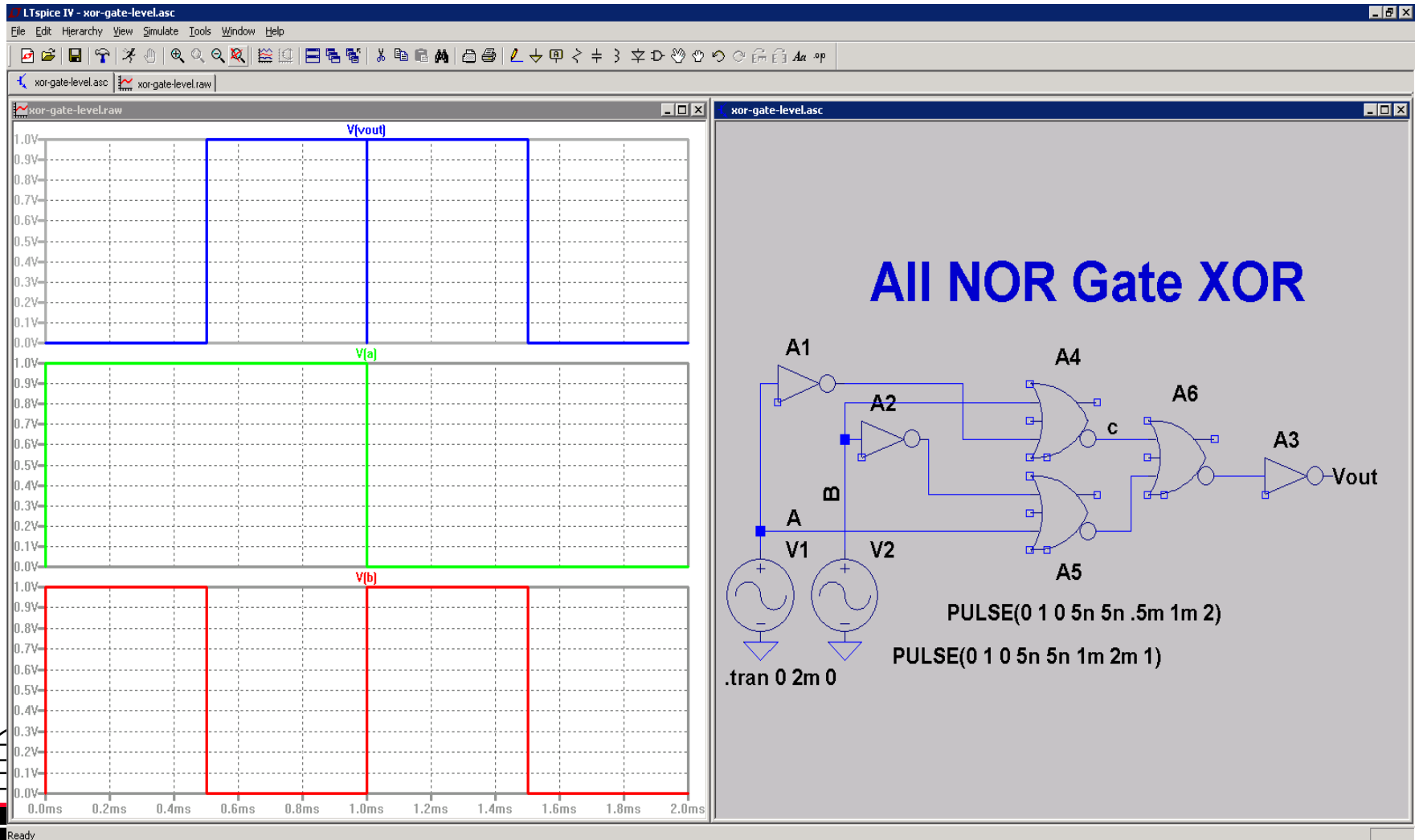


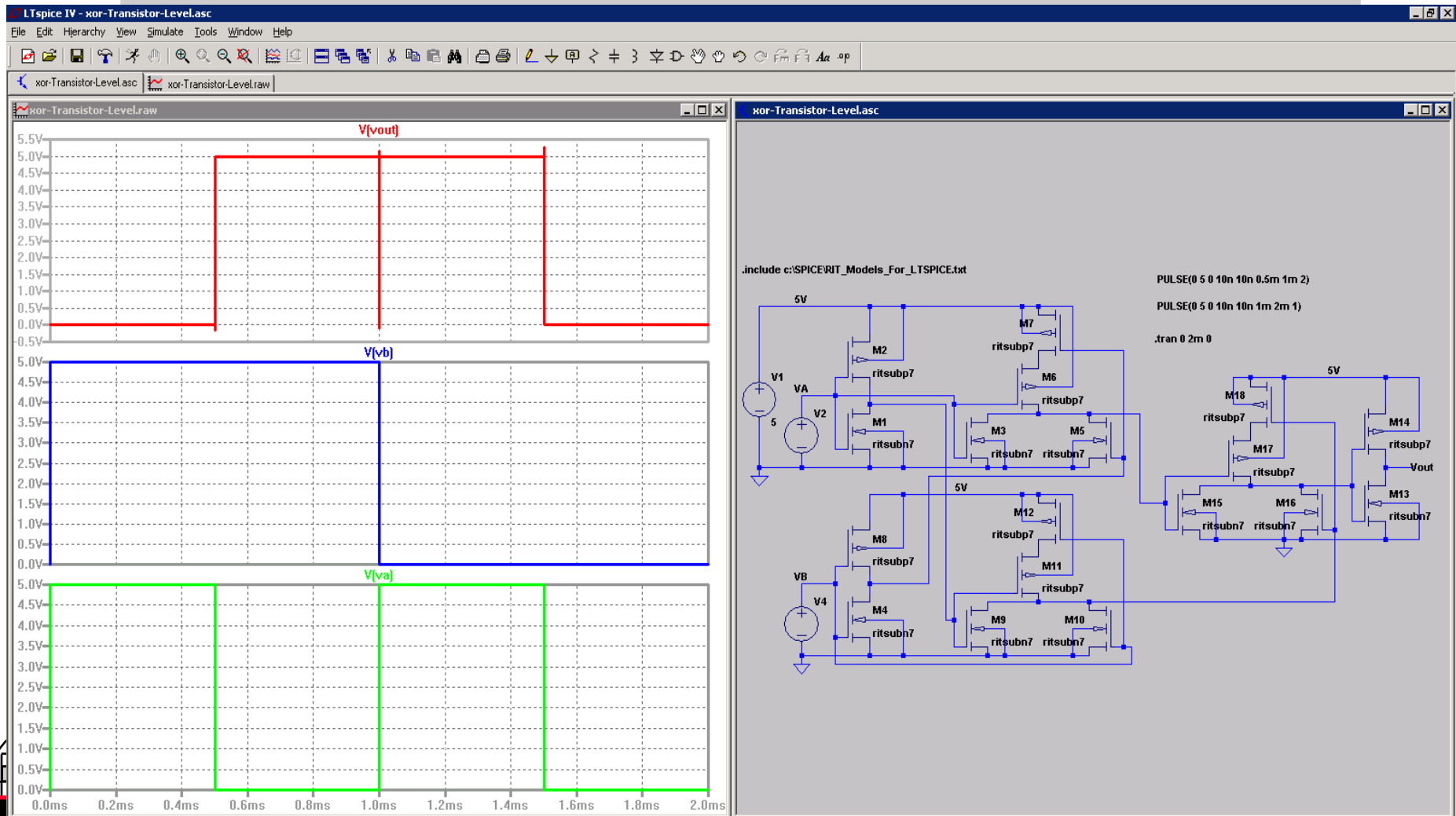TRANSISTOR LEVEL SIMULATION OF XOR – ALL/NOR




BASIC CELL XOR


Input A

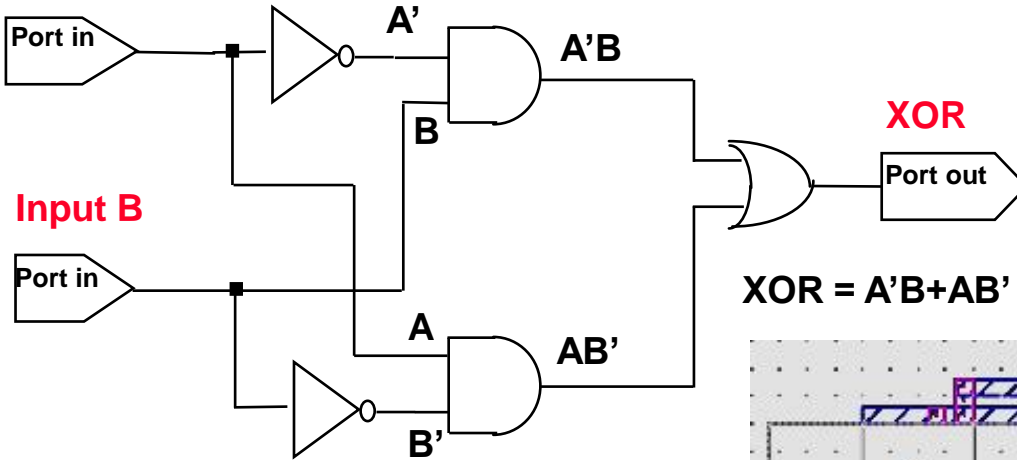


XOR

 

LAYOUT FOR XOR

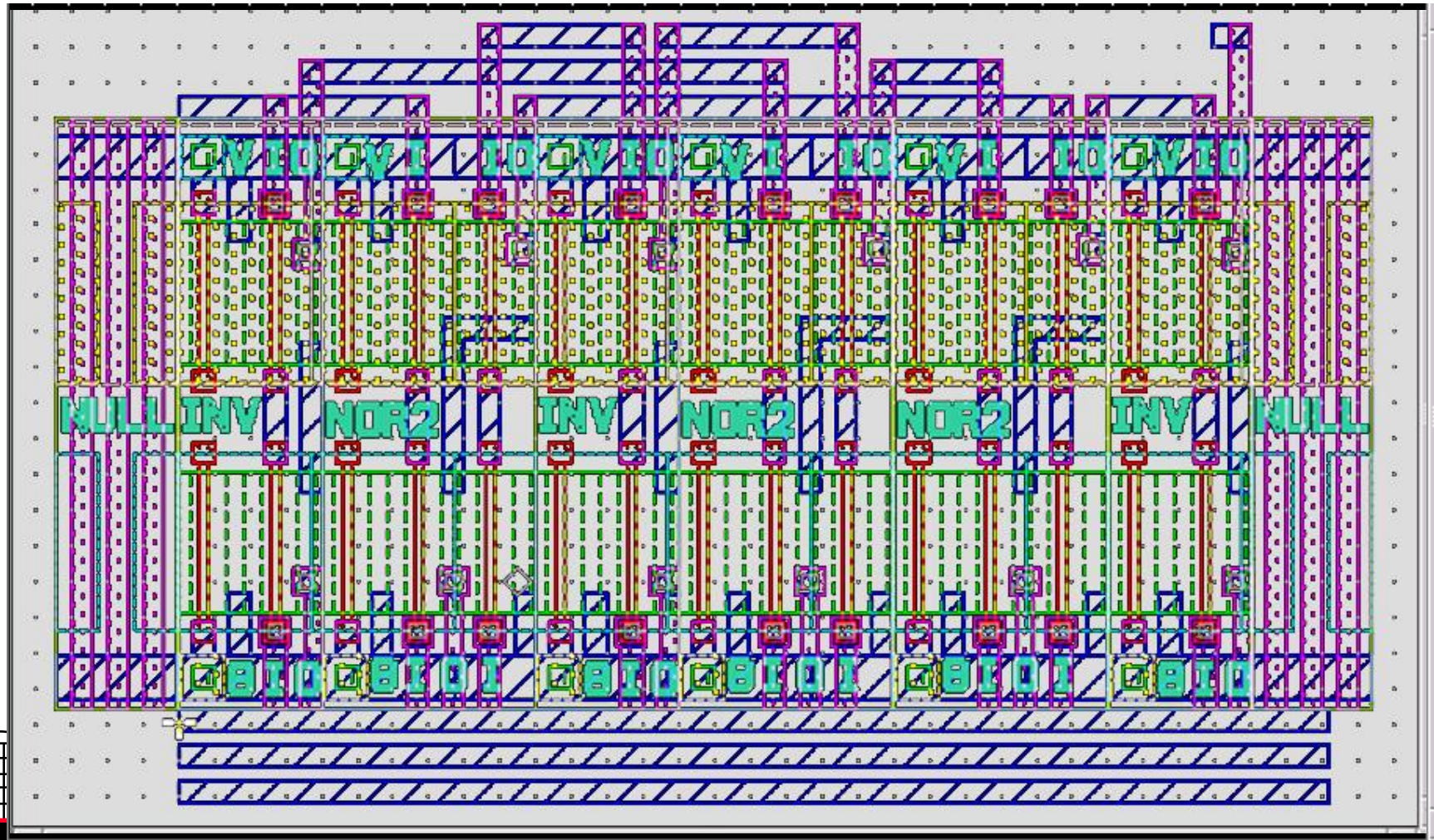

BASIC DIGITAL CELLS WITH PADS

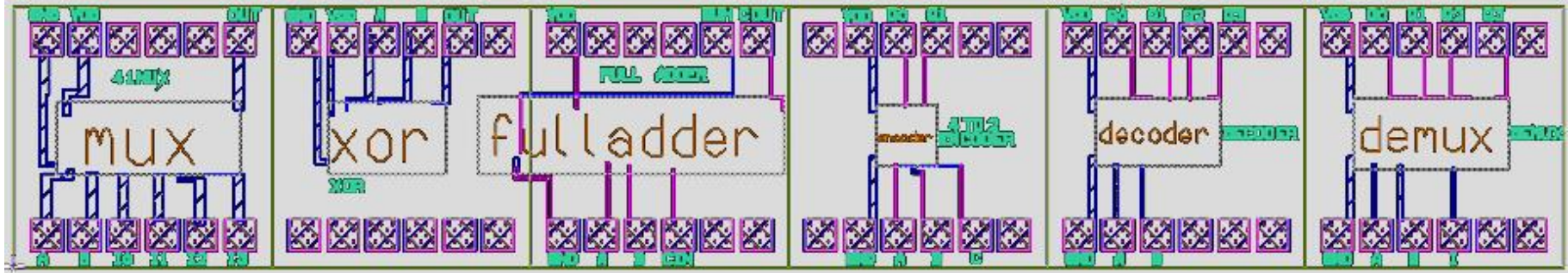

Multiplexer


XOR

Full Adder


Encoder

Decoder

Demux


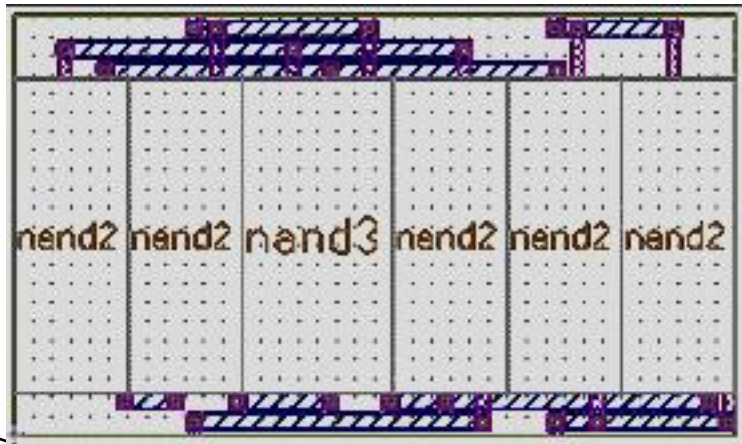


Edge Triggered D FF

 


JK FF

4 TO 1 MULTIPLEXER

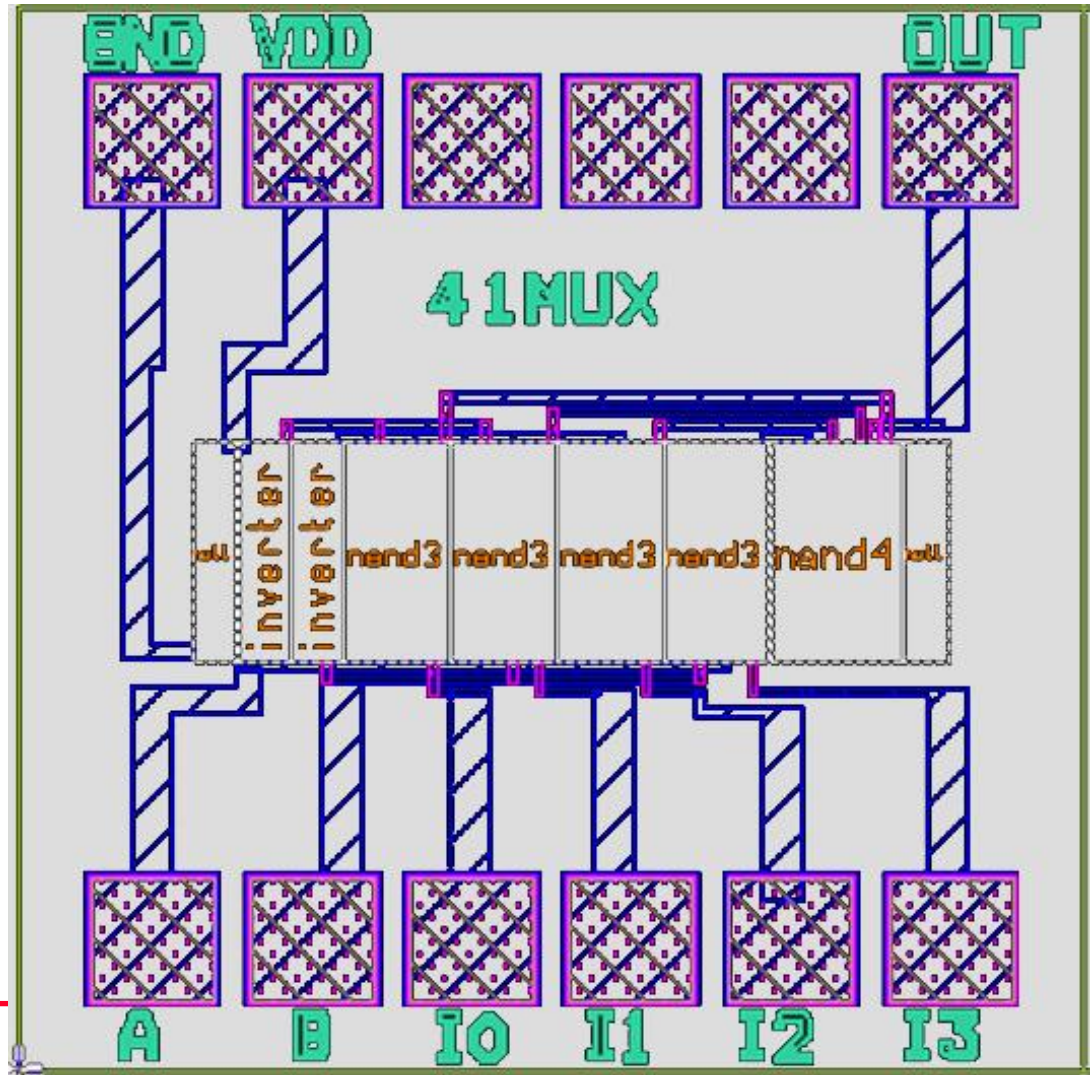 

4 TO 1 MUX - GATE LEVEL SIMULATION

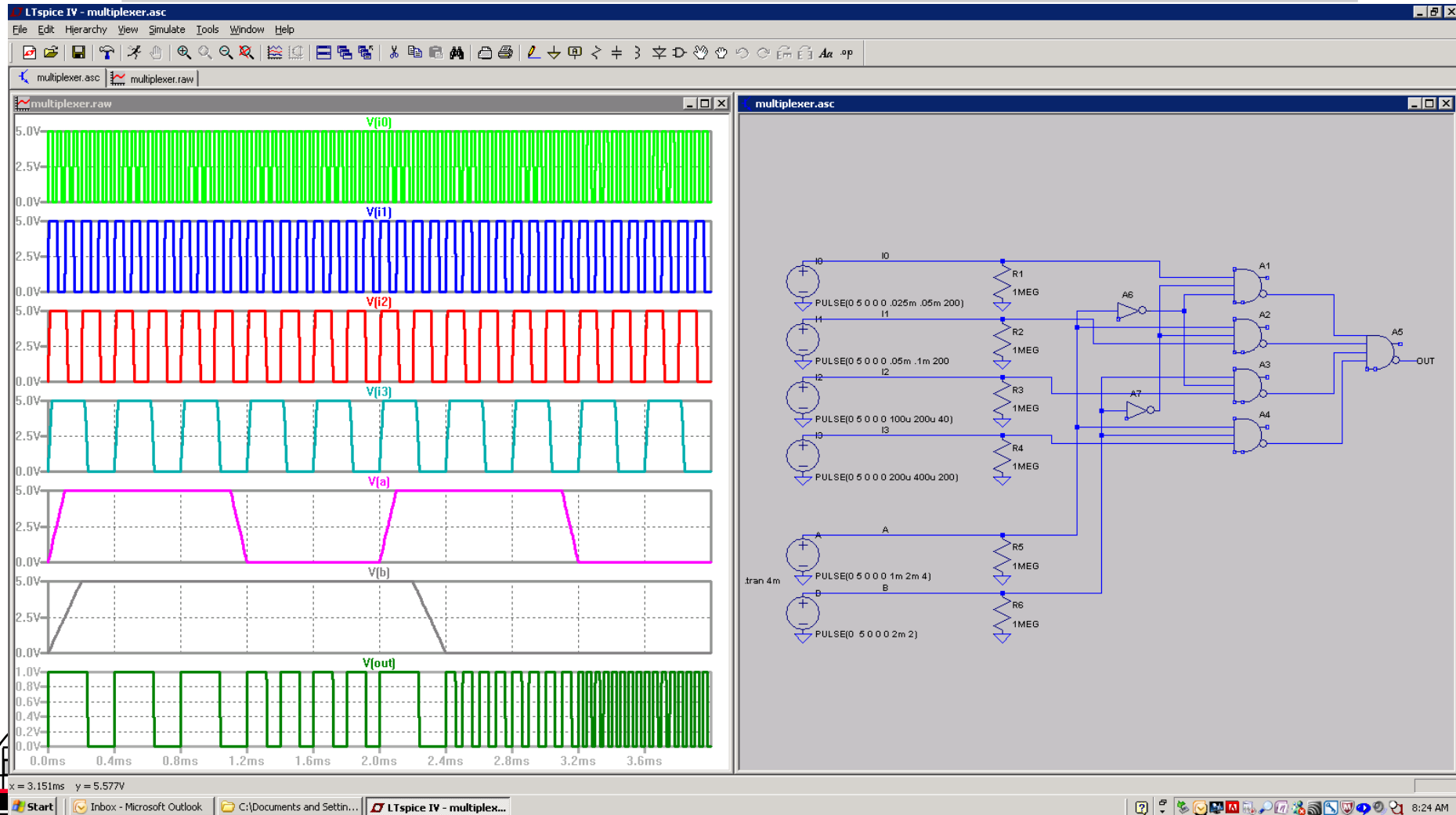

ADDITION IN BINARY

IN BASE 10

$$\begin{array}{r} 7 \\ +2 \\ \hline 9 \end{array}$$

IN BINARY


$$\begin{array}{r} 11 \quad \text{CARRY} \\ 0111 \\ 0010 \\ \hline 1001 \quad \text{SUM} \end{array}$$

0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

TRUTH TABLE
FOR ADDITION
RULES

A	B	CIN	SUM	COUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


AND-OR CIRCUIT REALIZATION OF SUM

 

TRUTH TABLE
FOR ADDITION
RULES

A	B	CIN	SUM	COU
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



CIRCUIT REALIZATION OF CARRY OUT (COUT)

 



TRUTH TABLE
FOR ADDITION
RULES

A	B	CIN	SUM	COUT
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



FULL ADDER

 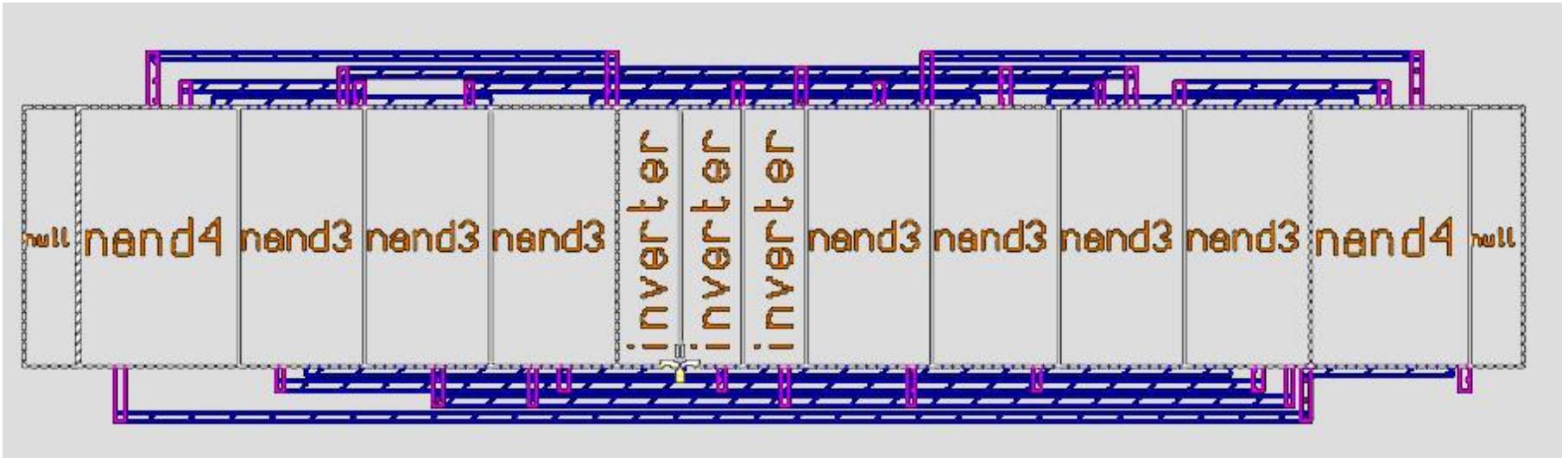


1 TO 4 DEMULTIPLEXER

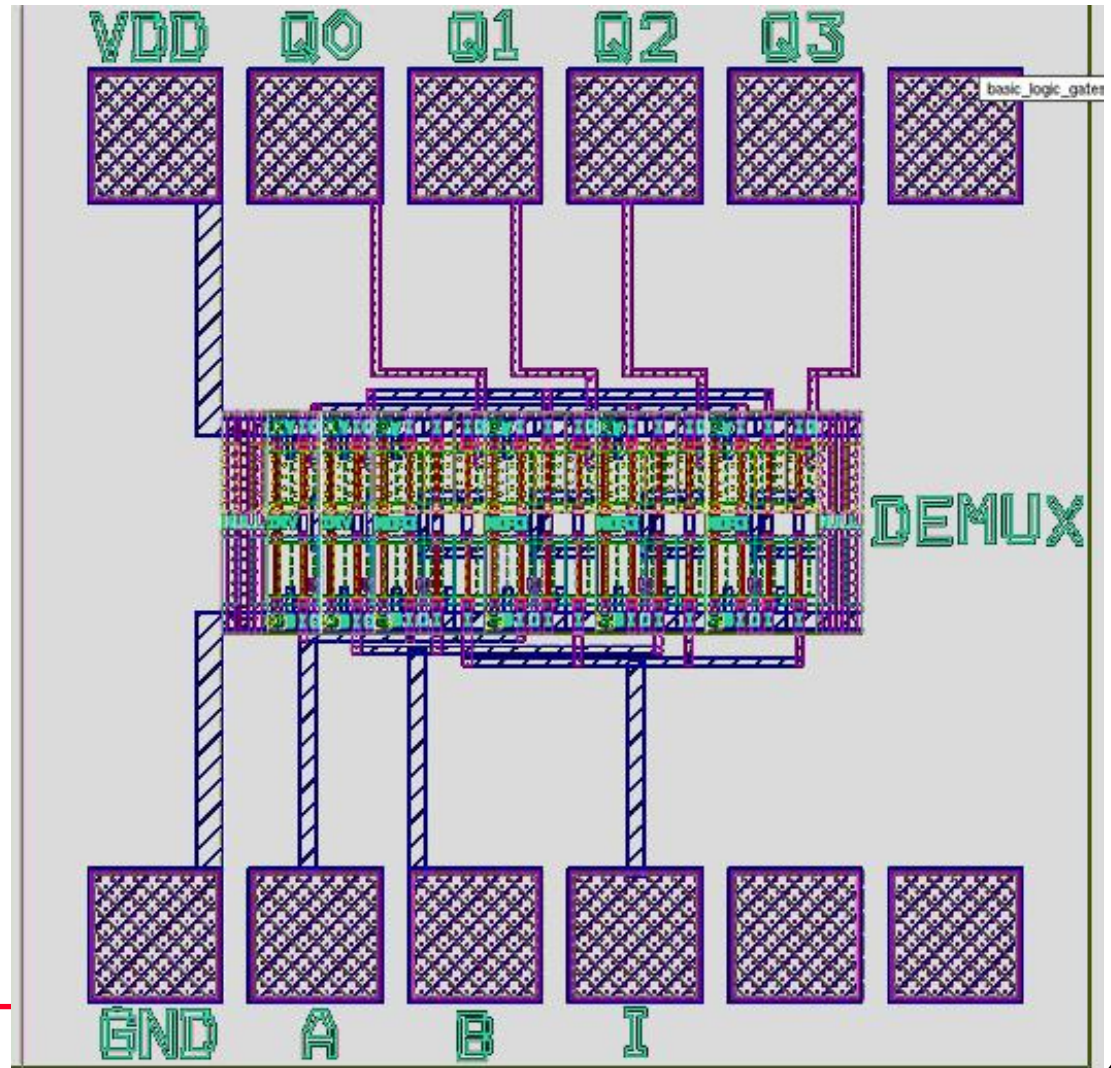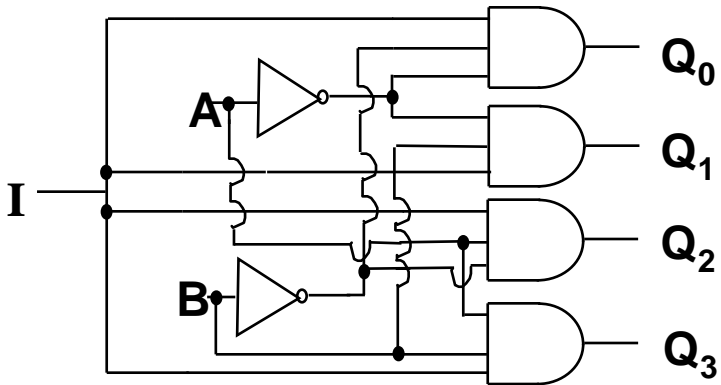

DECODER

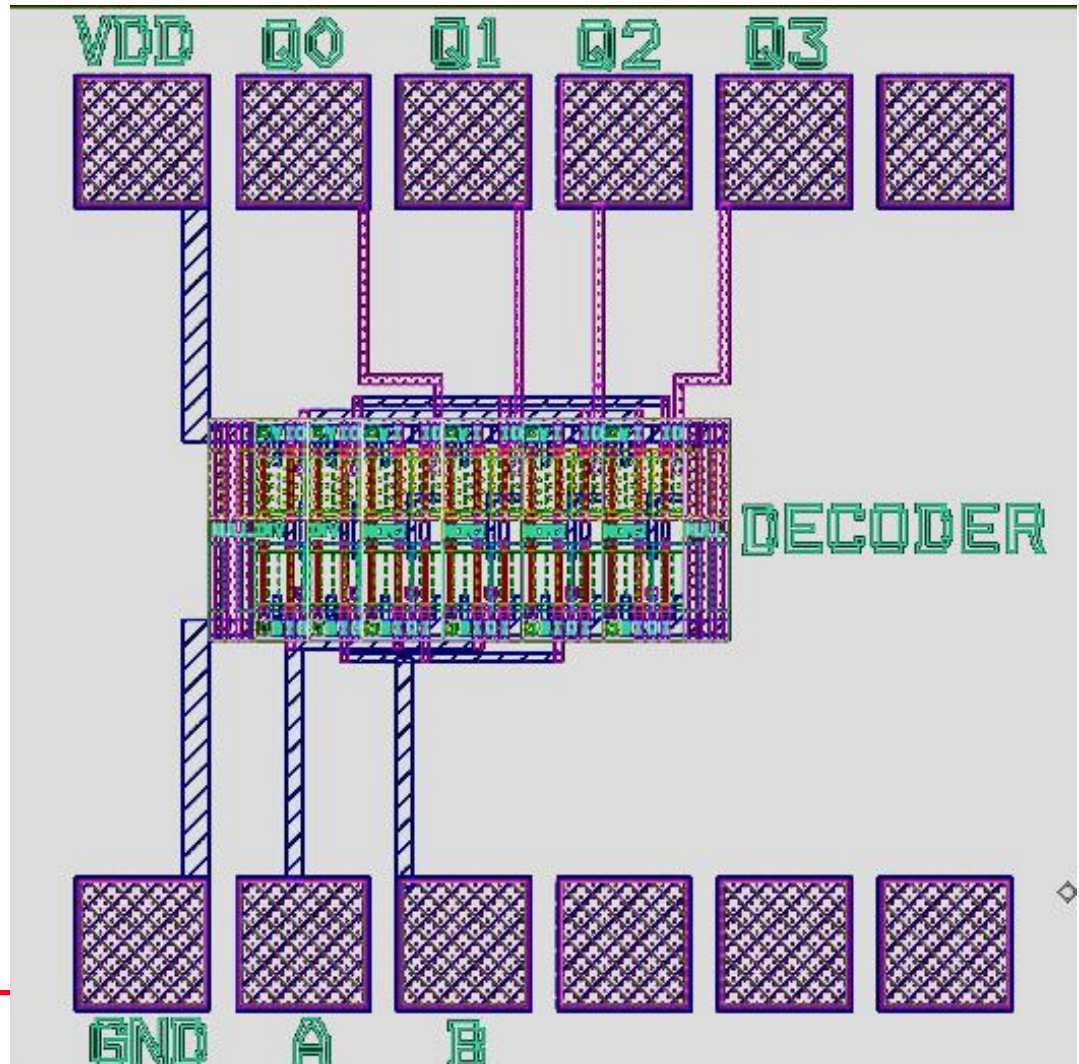 



ENCODER

 

Digital Encoder


512 inputs can be coded into 9 lines which is a more dramatic benefit

A	B	C	D	Q0	Q1
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

  


FILP-FLOPS

RS FLIP FLOP

 

R	S	Q
0	0	Q_{n-1}
0	1	1
1	0	0
1	1	INDETERMINATE


D FLIP FLOP

 


Q=DATA IF CLOCK IS HIGH

IF CLOCK IS LOW Q=PREVIOUS DATA VALUE

MASTER-SLAVE D FLIP FLOP

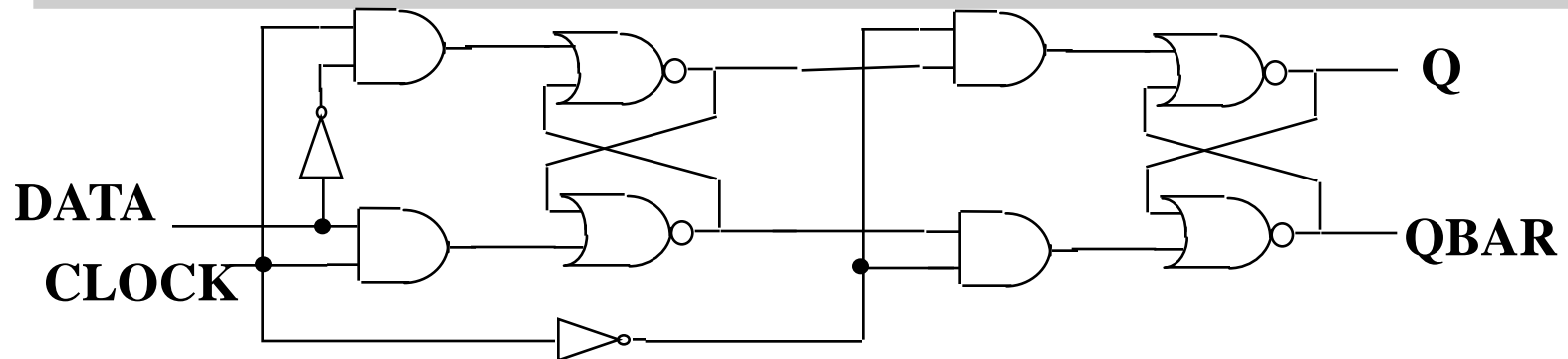


NEGATED INPUT NOR IS EQUAL TO AND


 


A	B	\bar{A}	\bar{B}	$\overline{\bar{A}\bar{B}}$	OUT
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1



ALL NOR MASTER SLAVE D FLIP FLOP

 


CMOS CLOCKED DATA LATCH USING AND-OR-INV

  



EDGE TRIGGERED D TYPE FLIP FLOP

 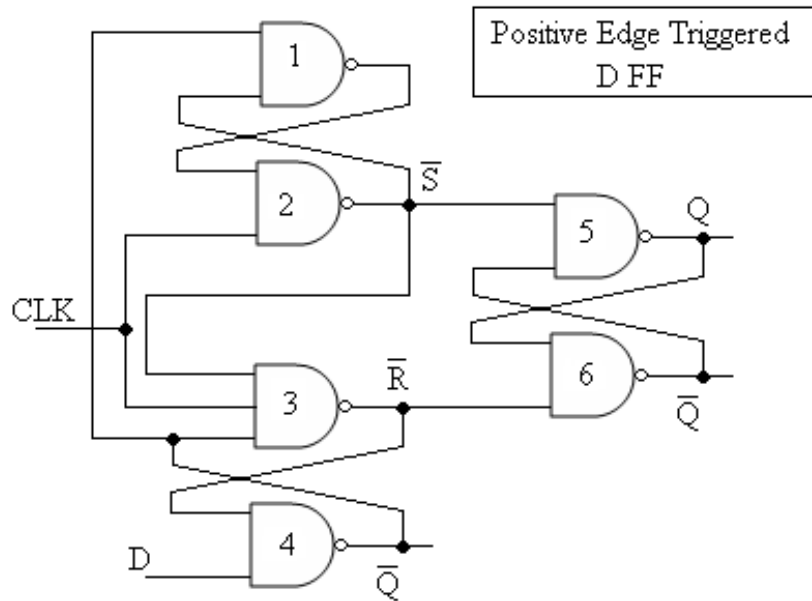


Inputs		Outputs	
D	C	Q^+	$Q^{\bar{}}$
0	\uparrow	0	1
1	\uparrow	1	0
X	0	Q	$Q^{\bar{}}$
X	1	Q	$Q^{\bar{}}$

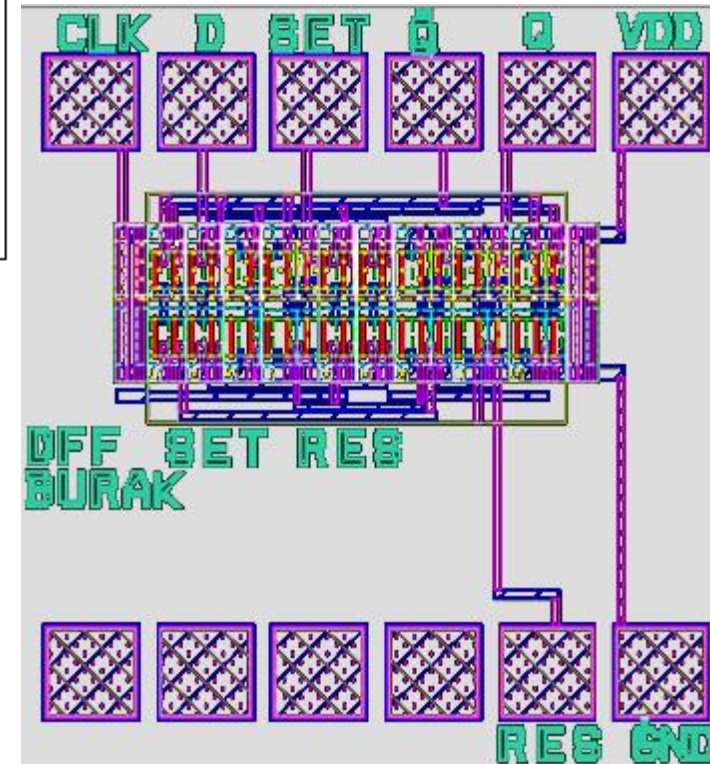

JK FLIP FLOP

  


Positive Edge Triggered
JK FF

 

Inputs			Outputs	
J	K	C	Q^+	Q^-
0	0	↑	Q	\overline{Q}
0	1	↑	0	1
1	0	↑	1	0
1	1	↑	\overline{Q}	Q
X	X	0	Q	Q
X	X	1	Q	Q


T-TYPE FLIP-FLOP

TOGGLE FLIP FLOP

 


Q: Toggles High and Low with Each Input

T	Q _{n-1}	Q
0	0	0
0	1	1
1	0	1
1	1	0

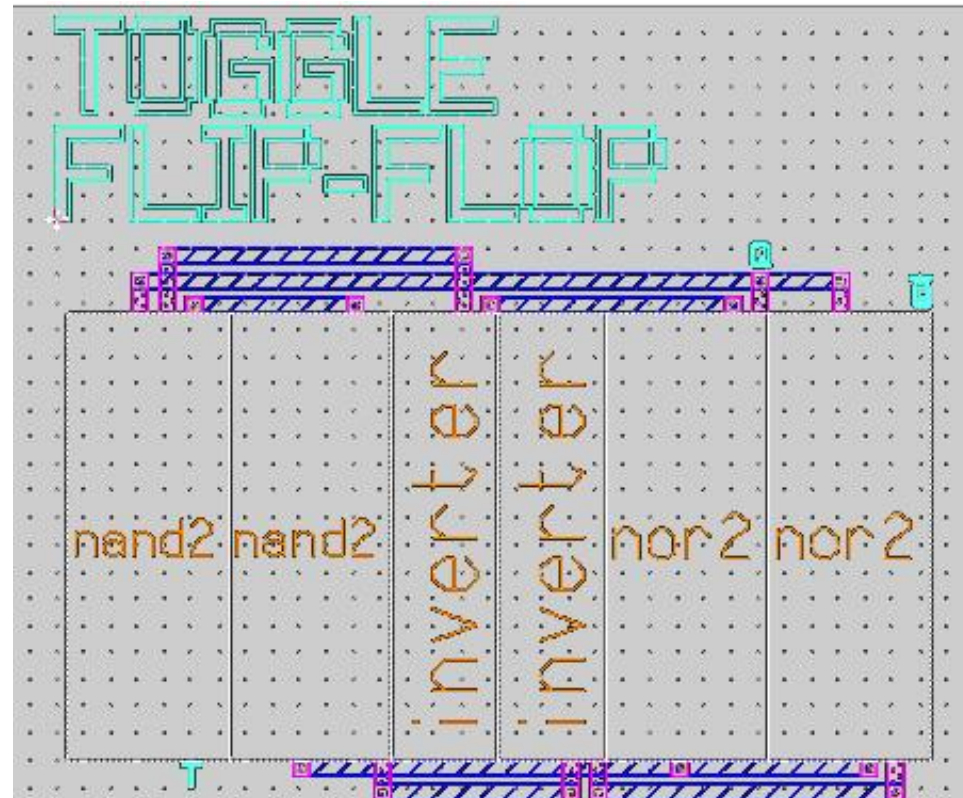

BINARY COUNTER USING T TYPE FLIP FLOPS

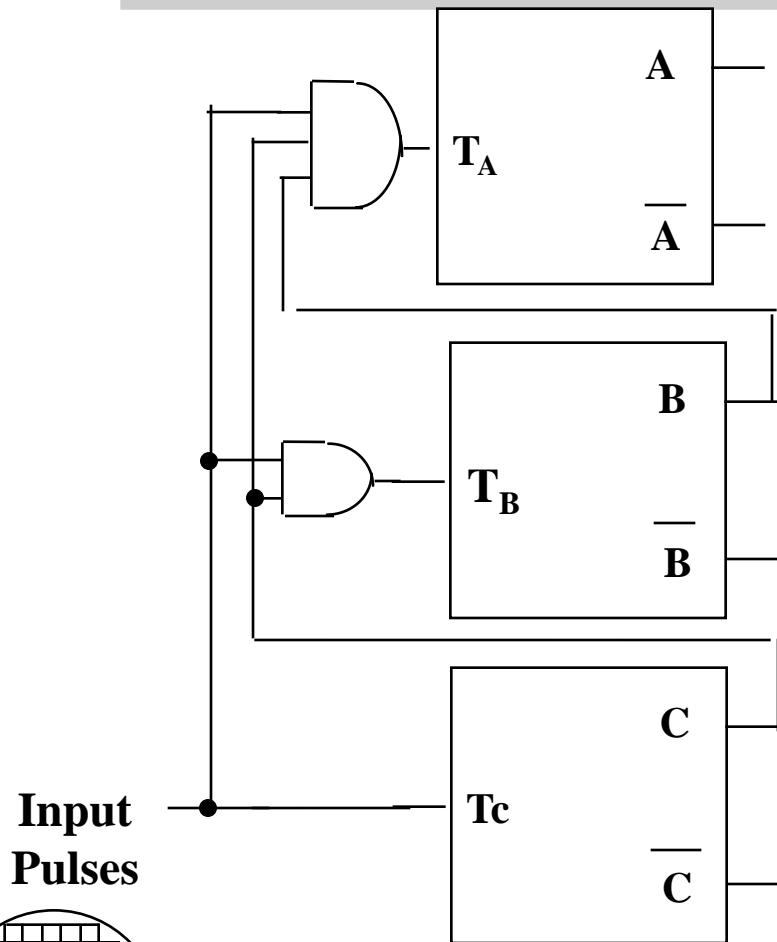

State Table for Binary Counter

Present State			Next State			F-F Inputs		
A	B	C	A	B	C	T _A	T _B	T _C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

T	Q _{n-1}	Q
0	0	0
0	1	1
1	0	1
1	1	0

TOGGLE FLIP FLOP

BC \ A	0	1
00	0	0
01	0	0
11	1	1
10	0	0

T_A


BC \ A	0	1
00	0	0
01	1	1
11	1	1
10	0	0

T_B



BC \ A	0	1
00	1	1
01	1	1
11	1	1
10	1	1

T_C


3-BIT BINARY COUNTER WITH D FLIP FLOPS

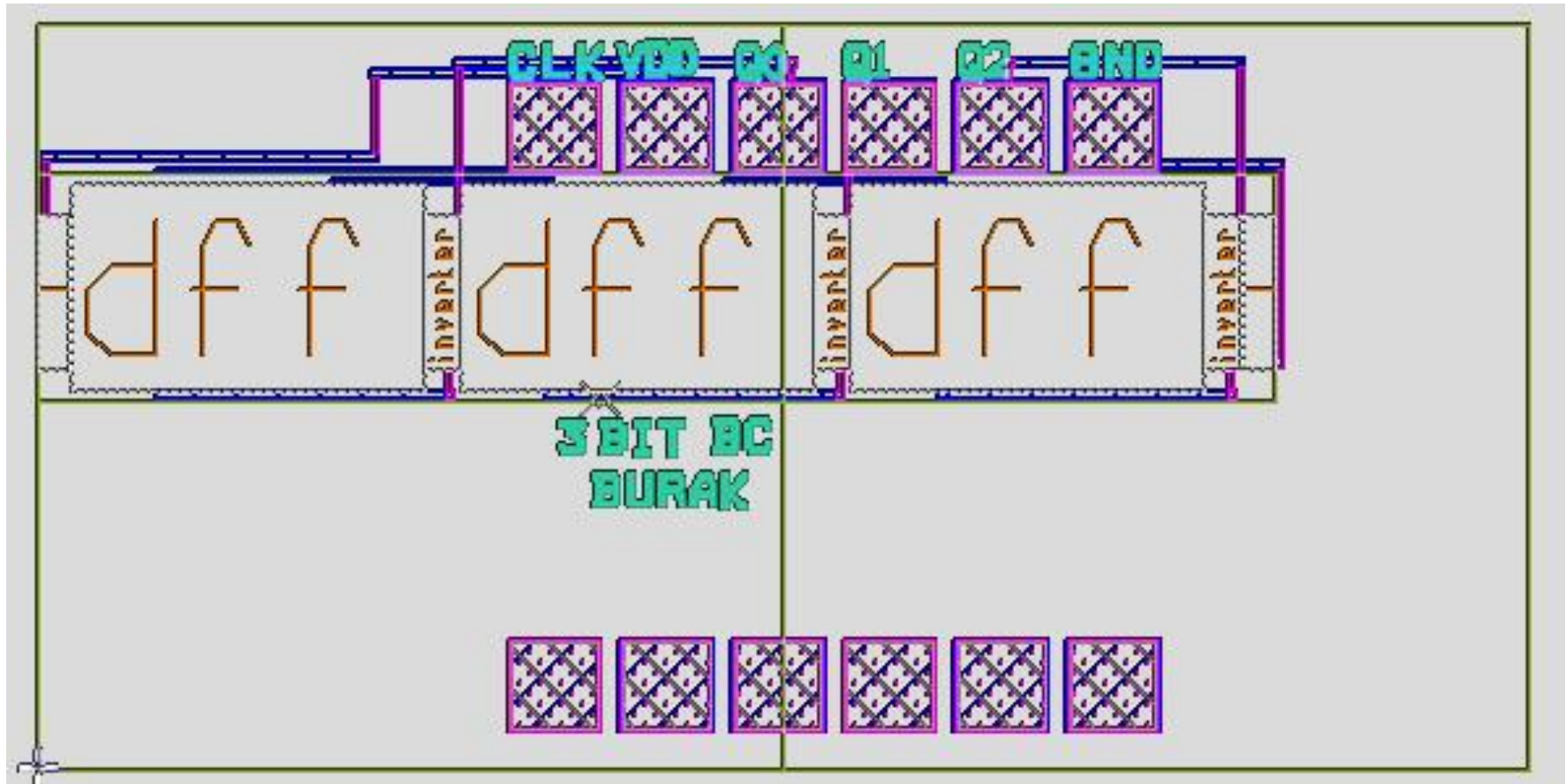

INVERTER WITH HYSTERESIS

  


Inverter with Hysteresis

 



The voltage on node 7 is different depending on if Vout is high or low. Changing the Voltage from source to substrate which changes the threshold voltage of M2

INVERTER WITH HYSTERESIS


 


SPICE shows inverter has hysteresis
 (Flip Blue output about the y-axis and superimpose on Red-Green Plot)

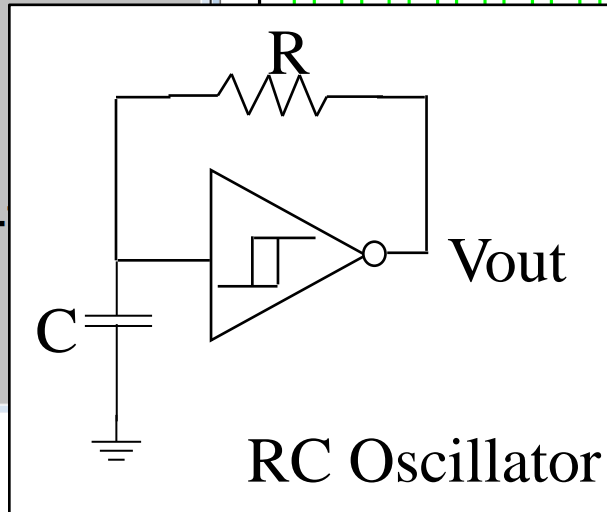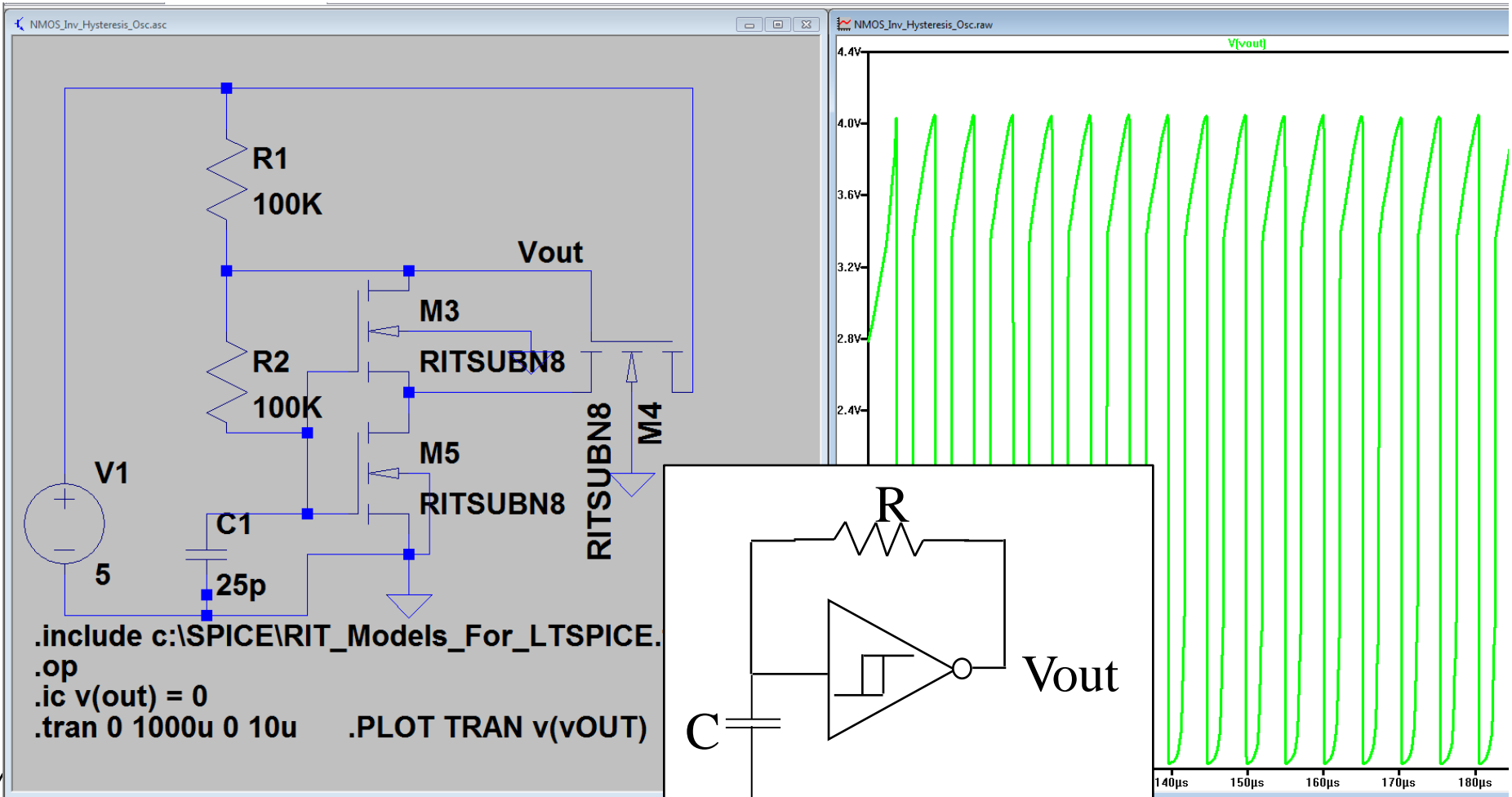
RC OSCILLATOR USING INVERTER WITH HYSTERESIS





BUFFERS

  

CMOS INVERTER WITH HYSTERESIS

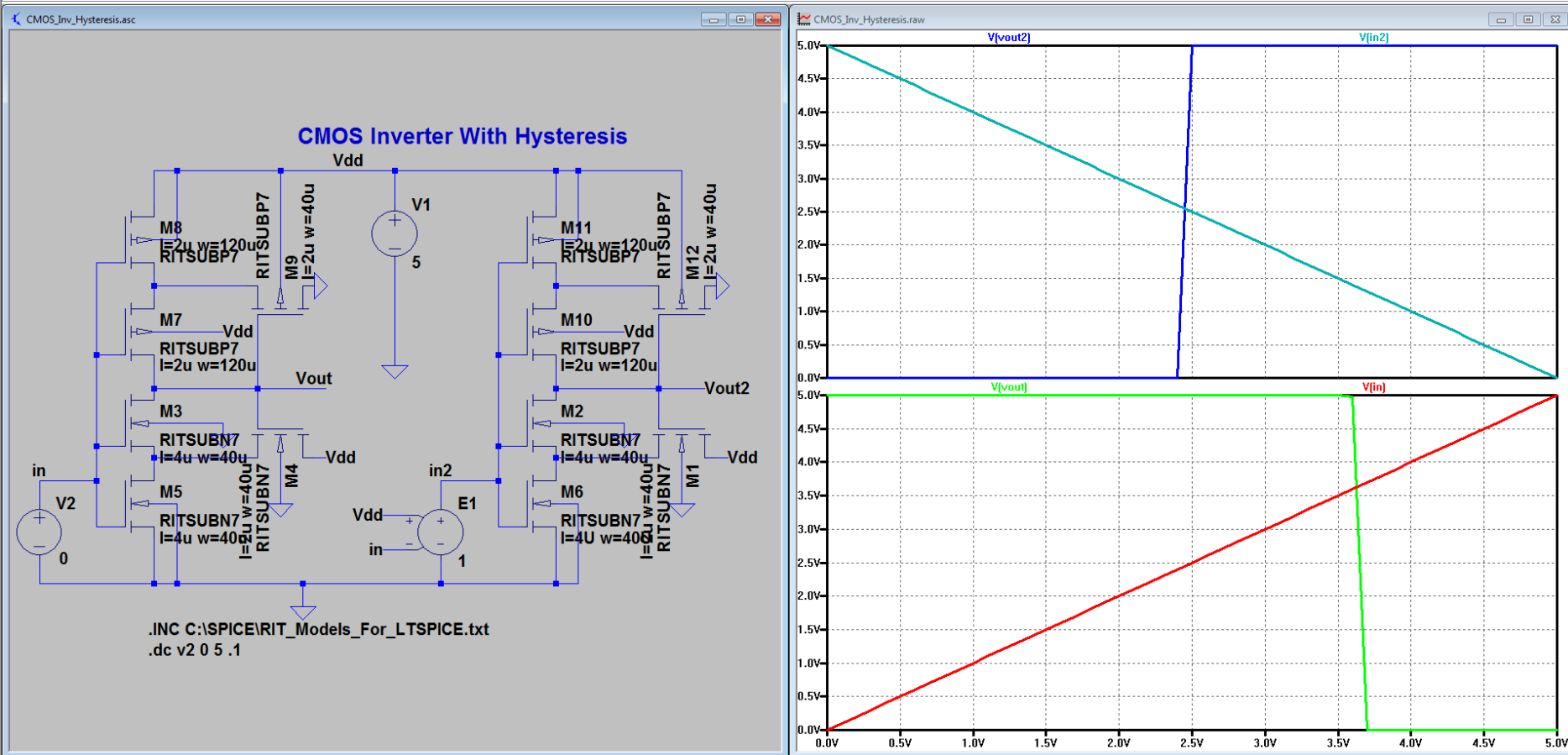


OSCILLATOR CMOS INVERTER WITH HYSTERESIS

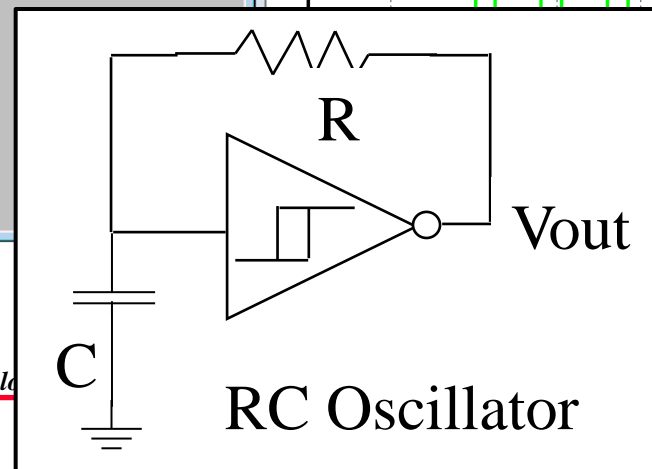 


REFERNCES

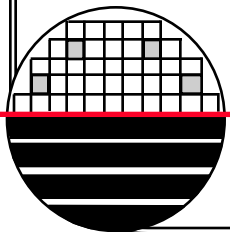1. Hodges Jackson and Saleh, Analysis and Design of Digital Integrated Circuits, Chapter 4.
2. Sedra and Smith, Microelectronic Circuits, Sixth Edition, Chapter 13.
3. Dr. Fuller's Lecture Notes, <http://people.rit.edu/lffeee>



HOMWORK – LOGIC

 1. Design a pseudo NMOS NAND gate. Use 1 μ m technology. Show it will work using SPICE.
2. Look up the data sheet for the MM74C14 CMOS inverter with hysteresis. Design a 10 KHz oscillator.
3. Use SPICE (transistor level) to simulate the 1 to 4 Demultiplexer.
4. Use SPICE (transistor level) to simulate the positive edge triggered D-type Flip-Flop.
5. Use SPICE to simulate a CMOS RC Oscillator with Buffers.



SPICE MODELS FOR MOSFETS

*SPICE MODELS FOR RIT DEVICES - DR. LYNN FULLER 4-10-2014

*LOCATION DR.FULLER'S WEBPAGE - <http://people.rit.edu/lffeee/CMOS.htm>

*

*Used in **Electronics II** for **CD4007 inverter chip**

*Note: Properties L=1u W=200u

.MODEL RIT4007N7 NMOS (LEVEL=7

+VERSION=3.1 CAPMOD=2 MOBMOD=1

+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8

+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7

+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95

+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5

+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)

*

*Used in **Electronics II** for **CD4007 inverter chip**

*Note: Properties L=1u W=200u

.MODEL RIT4007P7 PMOS (LEVEL=7

+VERSION=3.1 CAPMOD=2 MOBMOD=1


+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8

+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7

+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94

+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94

 +CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)



SPICE MODELS FOR MOSFETS

*Used for ALD1103 chips

*Note: Properties L=10u W=880u

.MODEL RITALDN3 NMOS (LEVEL=3

+TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7

+U0= 1215 VTO=0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5

+NSUB=1.57E16 XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11

+CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)

*

*Used for ALD1103 chips

*Note: Properties L=10u W=880u

.MODEL RITALDP3 PMOS (LEVEL=3

+TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7

+U0=550 VTO=-0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5

+NSUB=1.57E16 XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11

+CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)

SPICE MODELS FOR MOSFETS

*4-4-2013 LTSPICE uses Level=8

*For **RIT Sub-CMOS 150 process with L=2u**

.MODEL RITSUBN8 NMOS (LEVEL=8

+VERSION=3.1 CAPMOD=2 MOBMOD=1

+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8

+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7

+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95

+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5

+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)

*

*4-4-2013 LTSPICE uses Level=8

*For **RIT Sub-CMOS 150 process with L=2u**

.MODEL RITSUBP8 PMOS (LEVEL=8

+VERSION=3.1 CAPMOD=2 MOBMOD=1


+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8

+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7

+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94

+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94

 +CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)



SPICE MODELS FOR MOSFETS

* From **Sub-Micron CMOS Manufacturing Classes in MicroE ~ 1um Technology**

```
.MODEL RITSUBN7 NMOS (LEVEL=7  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8  
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7  
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*From **Sub-Micron CMOS Manufacturing Classes in MicroE ~ 1um Technology**

```
.MODEL RITSUBP7 PMOS (LEVEL=7  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8  
+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7  
+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94  
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94  
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```

SPICE MODELS FOR MOSFETS

*4-4-2013 LTSPICE uses Level=8

* From **Electronics II EEEE482 FOR ~100nm Technology**

```
.model EECMOSN NMOS (LEVEL=8
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*4-4-2013 LTSPICE uses Level=8

* From **Electronics II EEEE482 FOR ~100nm Technology**

```
.model EECMOSP PMOS (LEVEL=8
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```

*

Rochester Institute of Technology
Microelectronic Engineering