

**ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING**

Data Conversion Circuits

Dr. Lynn Fuller

Webpage: <http://people.rit.edu/lffeee>

Microelectronic Engineering

Rochester Institute of Technology


82 Lomb Memorial Drive

Rochester, NY 14623-5604

Tel (585) 475-2035

Email: Lynn.Fuller@rit.edu

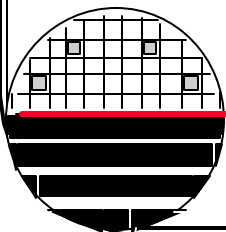
Department webpage: <http://www.microe.rit.edu>



INTRODUCTION


Analog electronic circuits are different from digital circuits in that the signals are expected to have any value rather than two discrete values. **Primitive** analog components include the diode, mosfet, BJT, resistor, capacitor, etc,. Analog circuit **building blocks** include single stage amplifiers, differential amplifiers, constant current sources, voltage references, etc. **Basic** analog electronic circuits include the operational amplifier, inverting amplifier, non-inverting amplifier, integrator, bistable multivibrator, peak detector, comparator, RC oscillator, etc. **Mixed-mode** analog integrated circuits include D-to-A, A-to-D, etc.

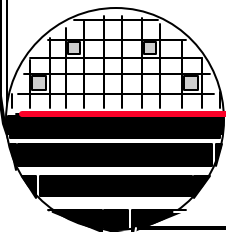This document will introduce some **mixed-mode** analog/digital electronic circuits.




OUTLINE

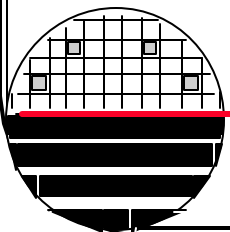
- Analog Multiplexer
- D to A
- A to D
- Binary Counter A to D
- Flip Flops
- Shift Registers/Counters
- Design Examples
- Blue Tooth
- References
- Homework




3 BIT ANALOG MULTIPLEXER

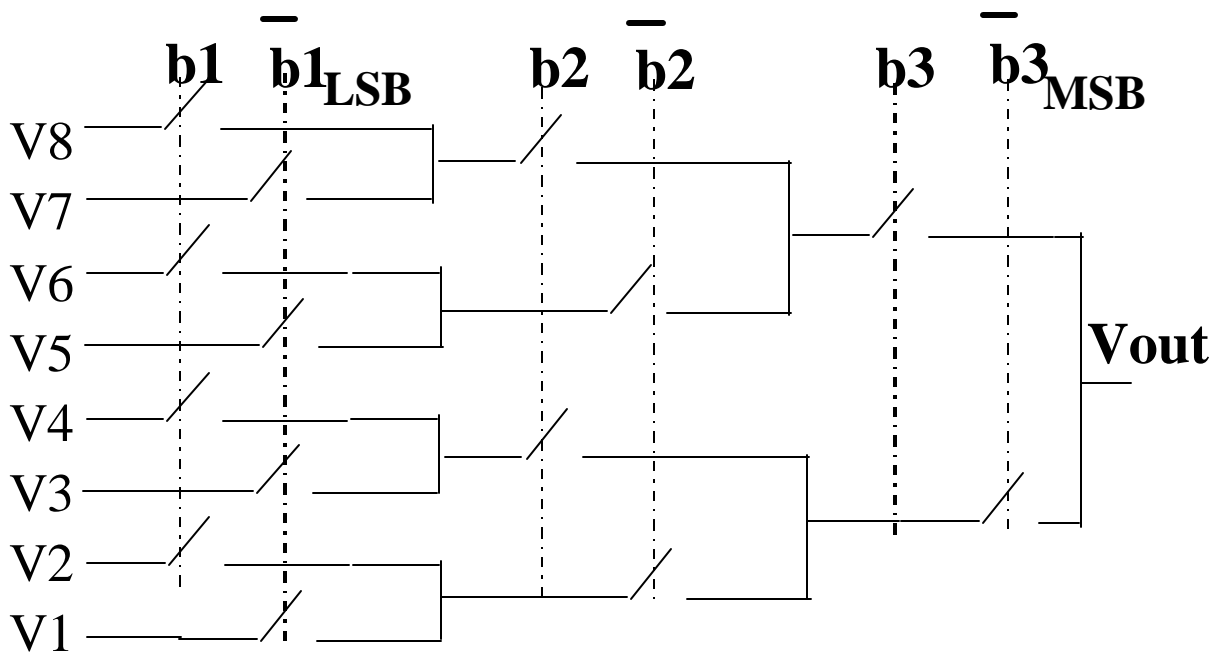

MSB		LSB		Vout
b3	b2	b1		
0	0	0		V1
0	0	1		V2
0	1	0		V3
0	1	1		V4
1	0	0		V5
1	0	1		V6
1	1	0		V7
1	1	1		V8

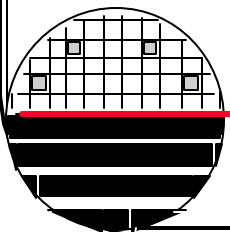


ANALOG MULTIPLEXER APPLICATION

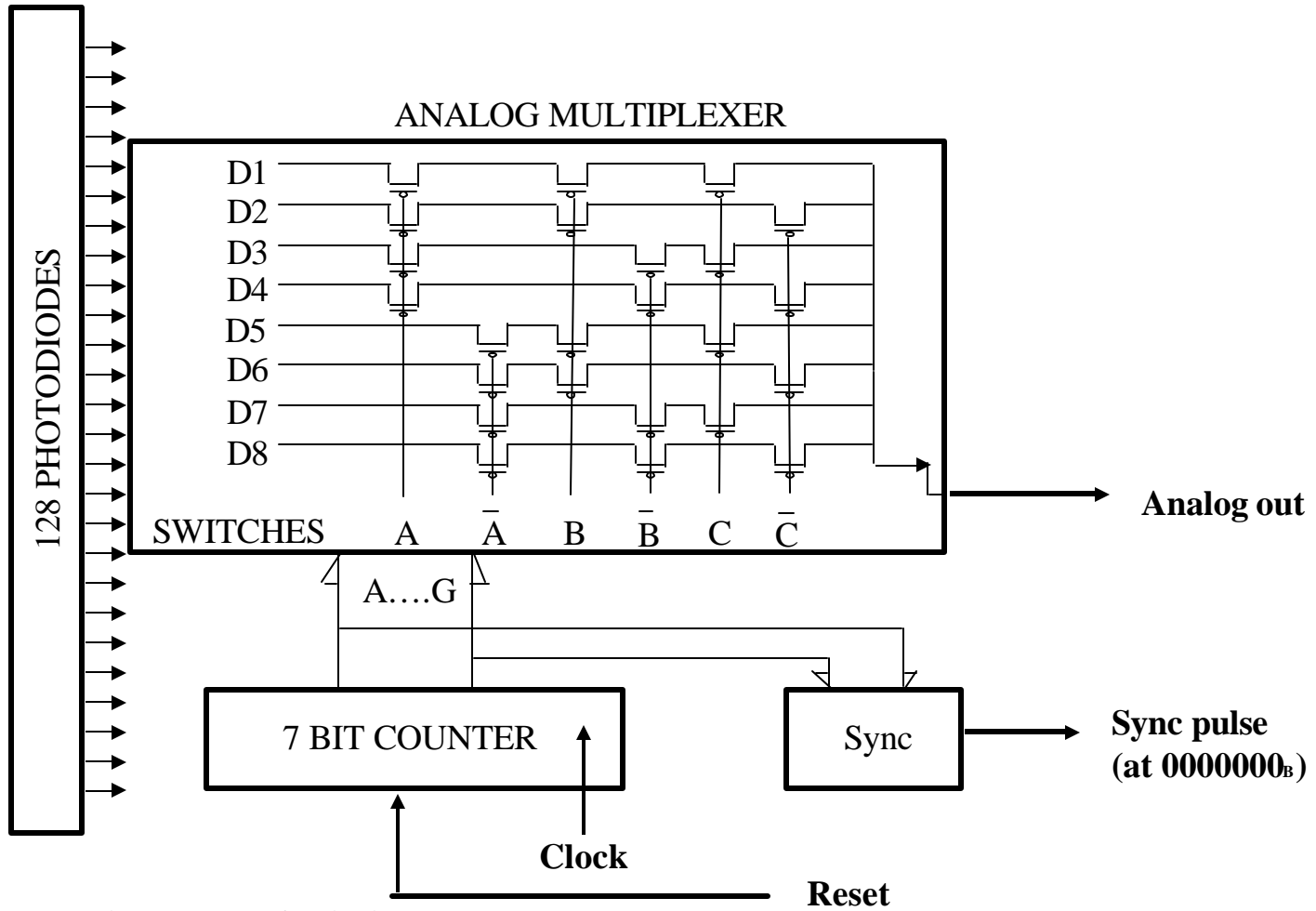


Rochester Institute of Technology
Microelectronic Engineering

CMOS ANALOG MULTIPLEXER LAYOUT


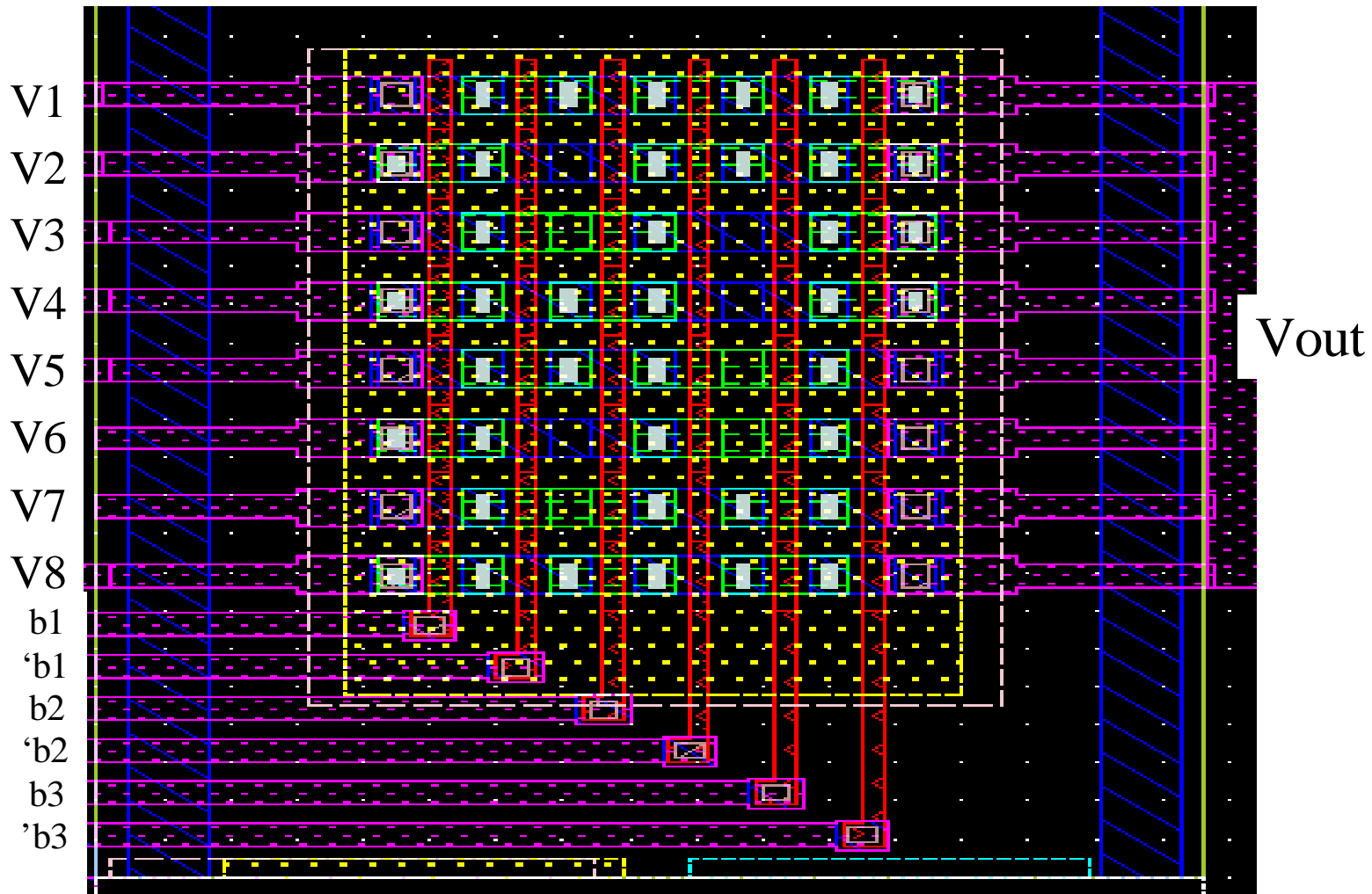


DIGITAL TO ANALOG CONVERSION

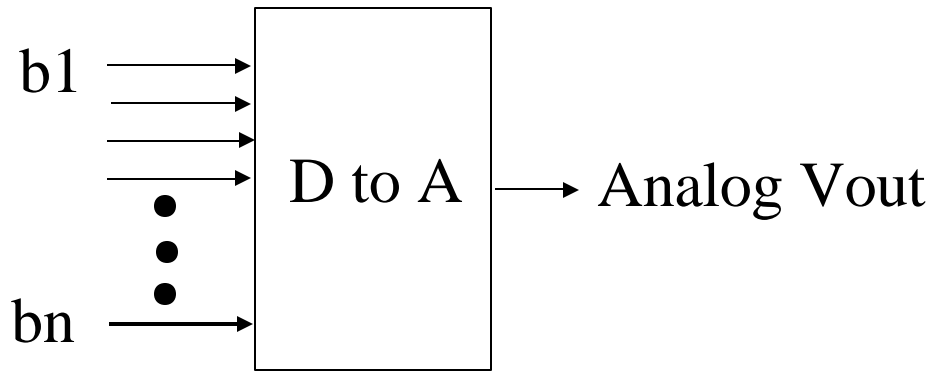
A digital word of n bits is converted to an analog voltage. If n = 3 then 2ⁿ or 8 different analog values are possible. If n=10 then 1024 different analog values are possible.



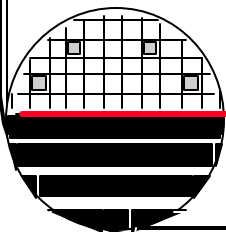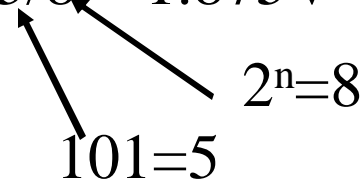
For example if the reference voltage is 3 volts and n = 3 and the digital word is 101 then the Analog Vout = 3V x 5/8 = 1.875V




3 BIT D TO A

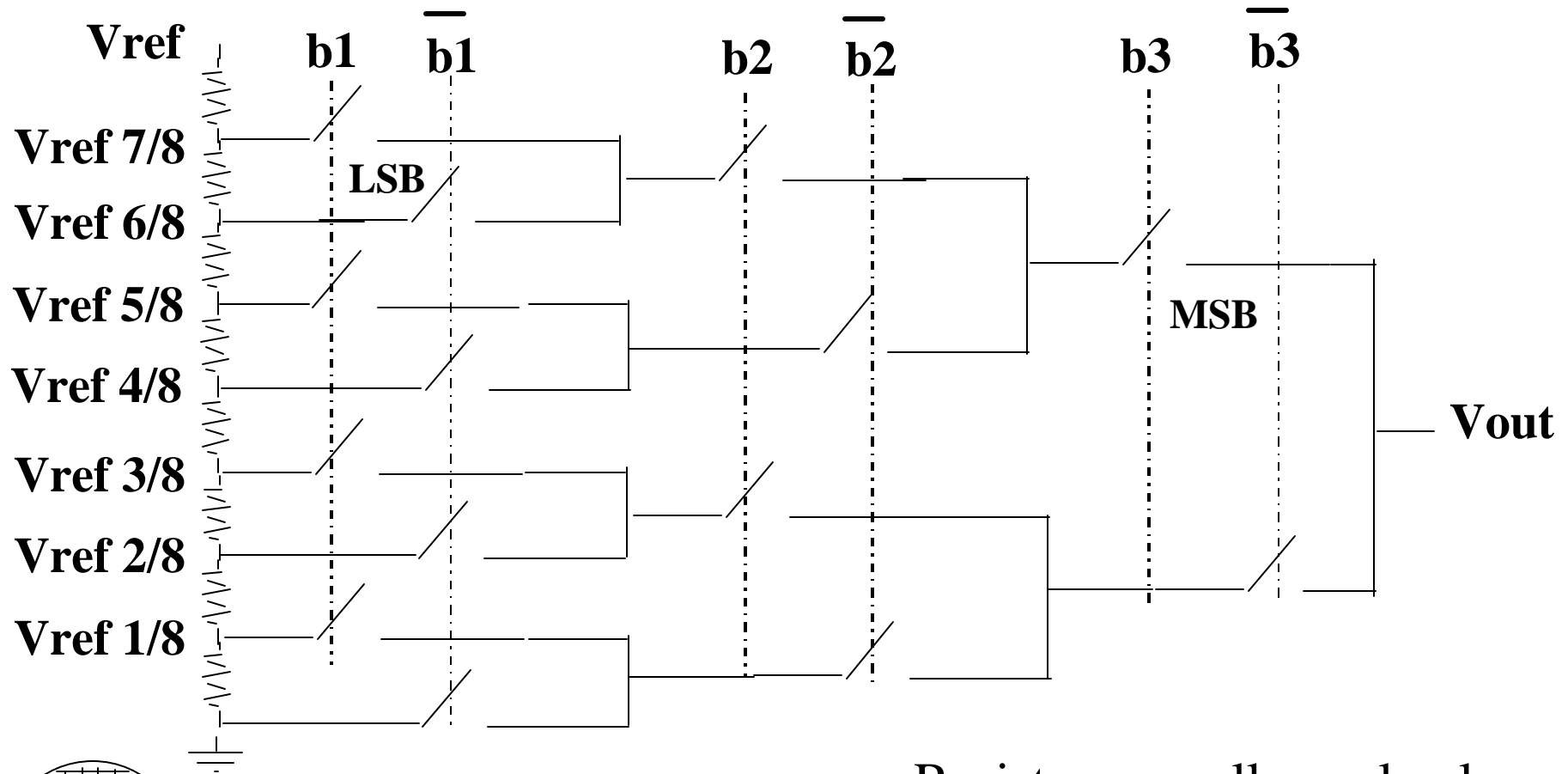

Resistors are all equal value

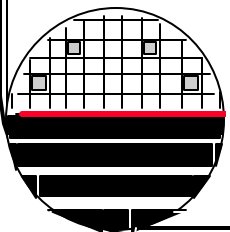


BINARY-WEIGHTED RESISTOR D TO A

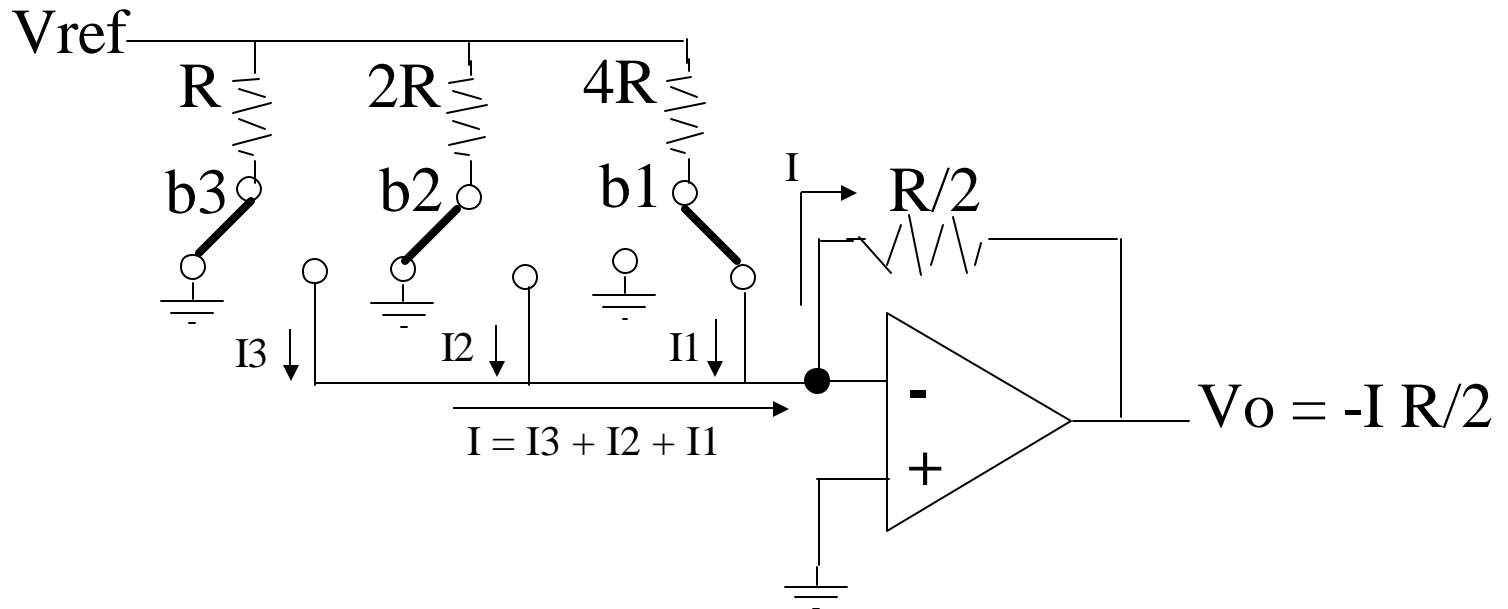


With the switches as shown $V_o = \frac{-V_{ref} R/2}{4R} = -V_{ref} / 8$

What is V_o for a 101 digital input?

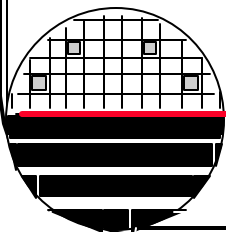How is this architecture extended to more bits?




R-2R RESISTOR LADDER D TO A

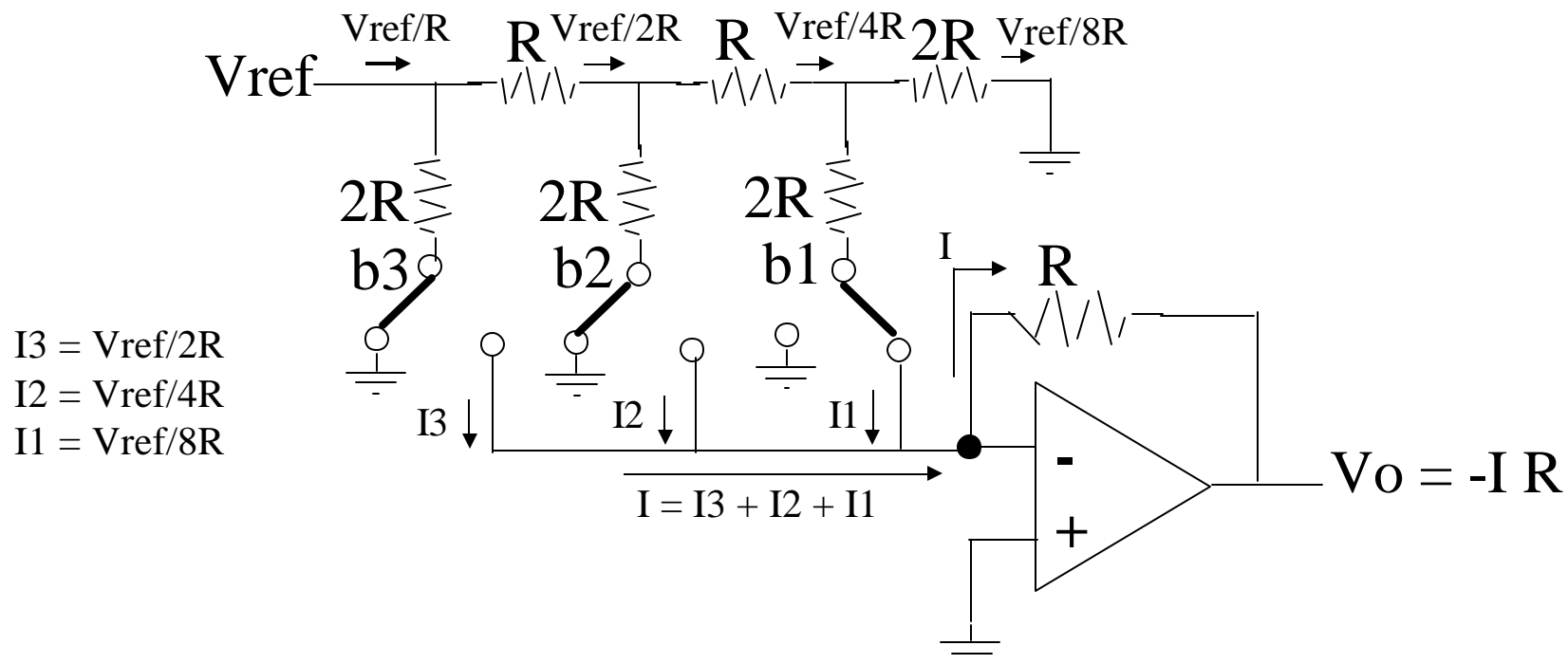



With the switches as shown $V_o = \frac{-V_{ref} R}{8R} = -V_{ref} / 8$

What is V_o for a 101 digital input?

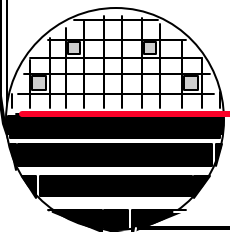How is this architecture extended to more bits?




DAC LAYOUT

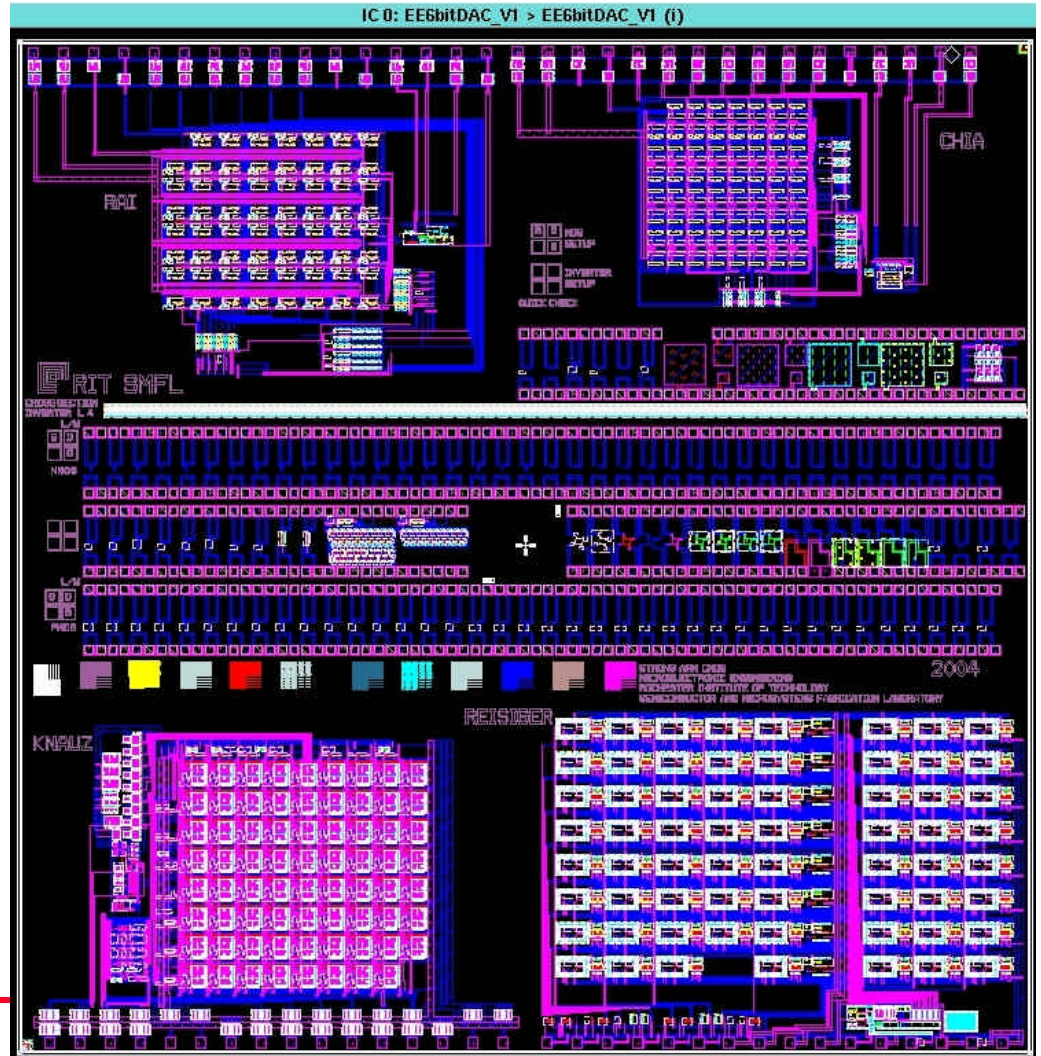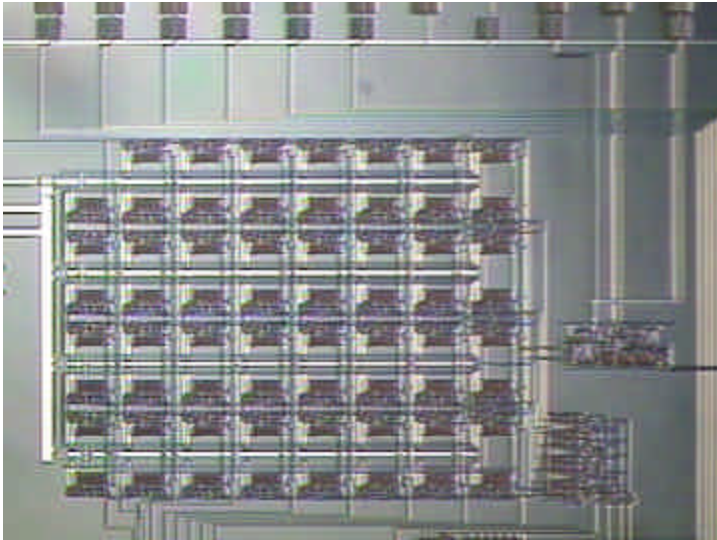

DAC1	DAC2
Rai	Chia
Test Devices	
Saxer	
DAC4	DAC3
Knauz	Reisiger


Rochester Institute of Technology
Microelectronic Engineering

FEEDBACK-COMPARATOR A TO D CONVERTER



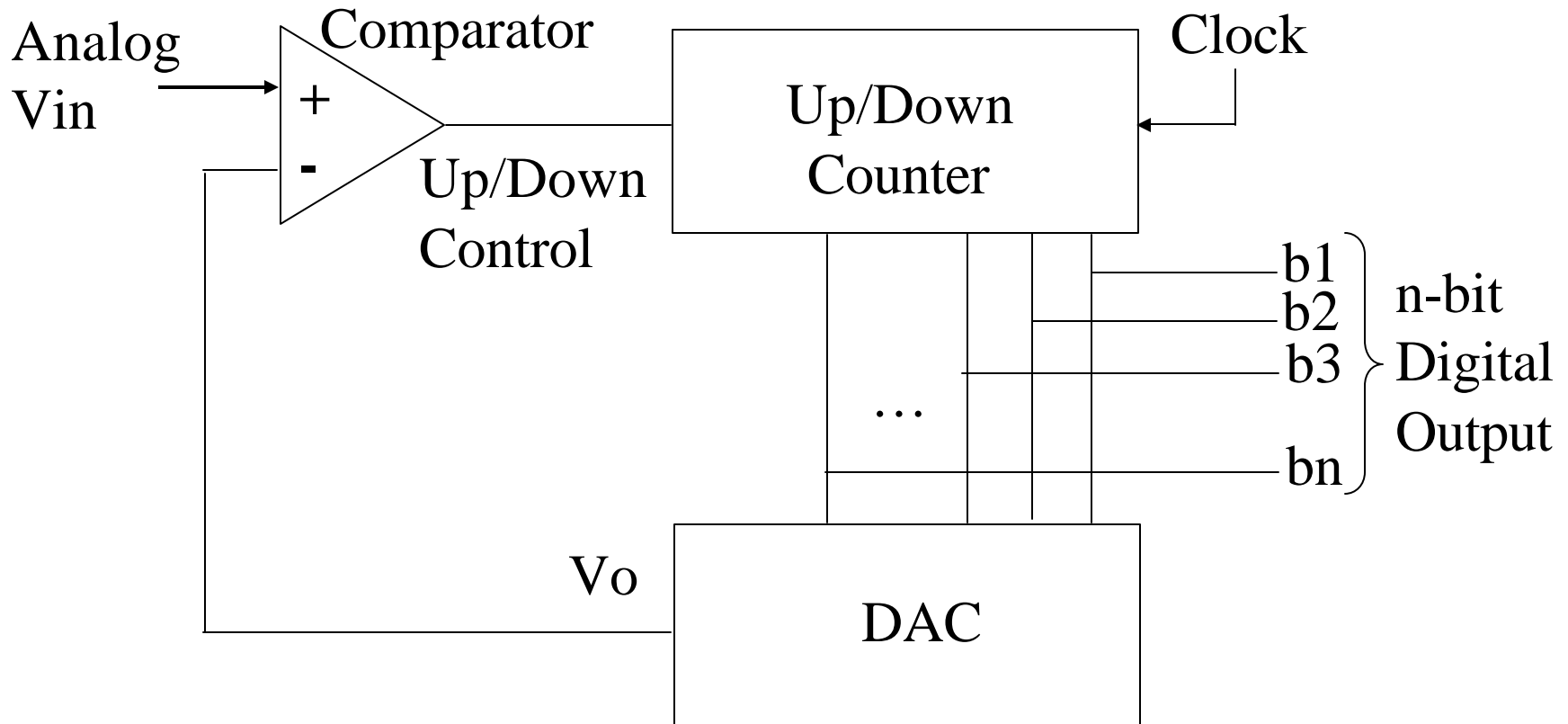


Analog V_{in} must be less than DAC V_{ref} .

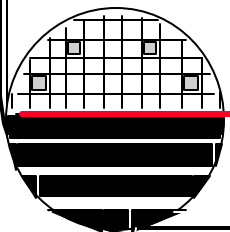
Could take a lot of clock cycles (time) for each conversion.



DUAL SLOPE A TO D CONVERTER

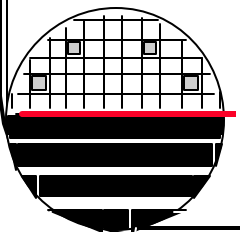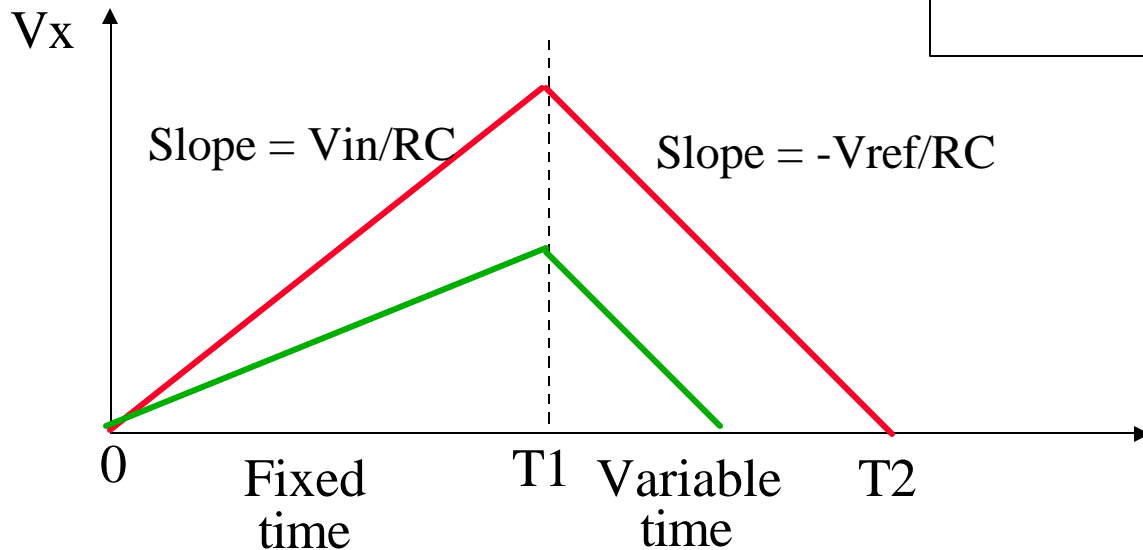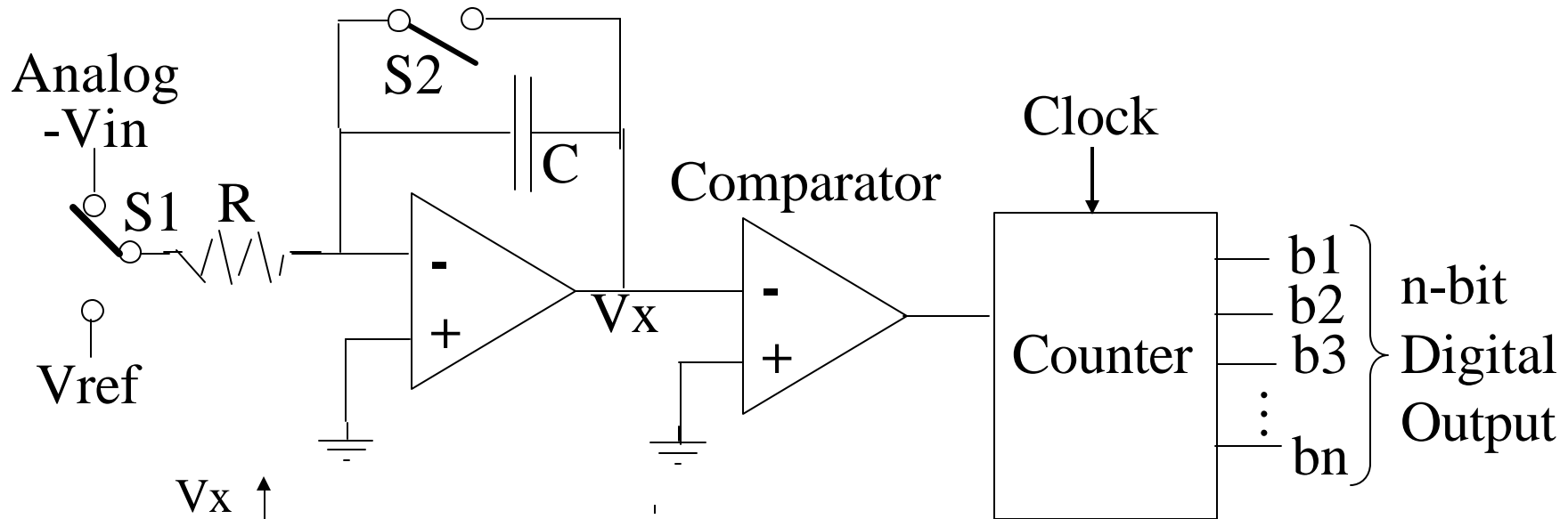


3 BIT FLASH ANALOG TO DIGITAL CONVERTER

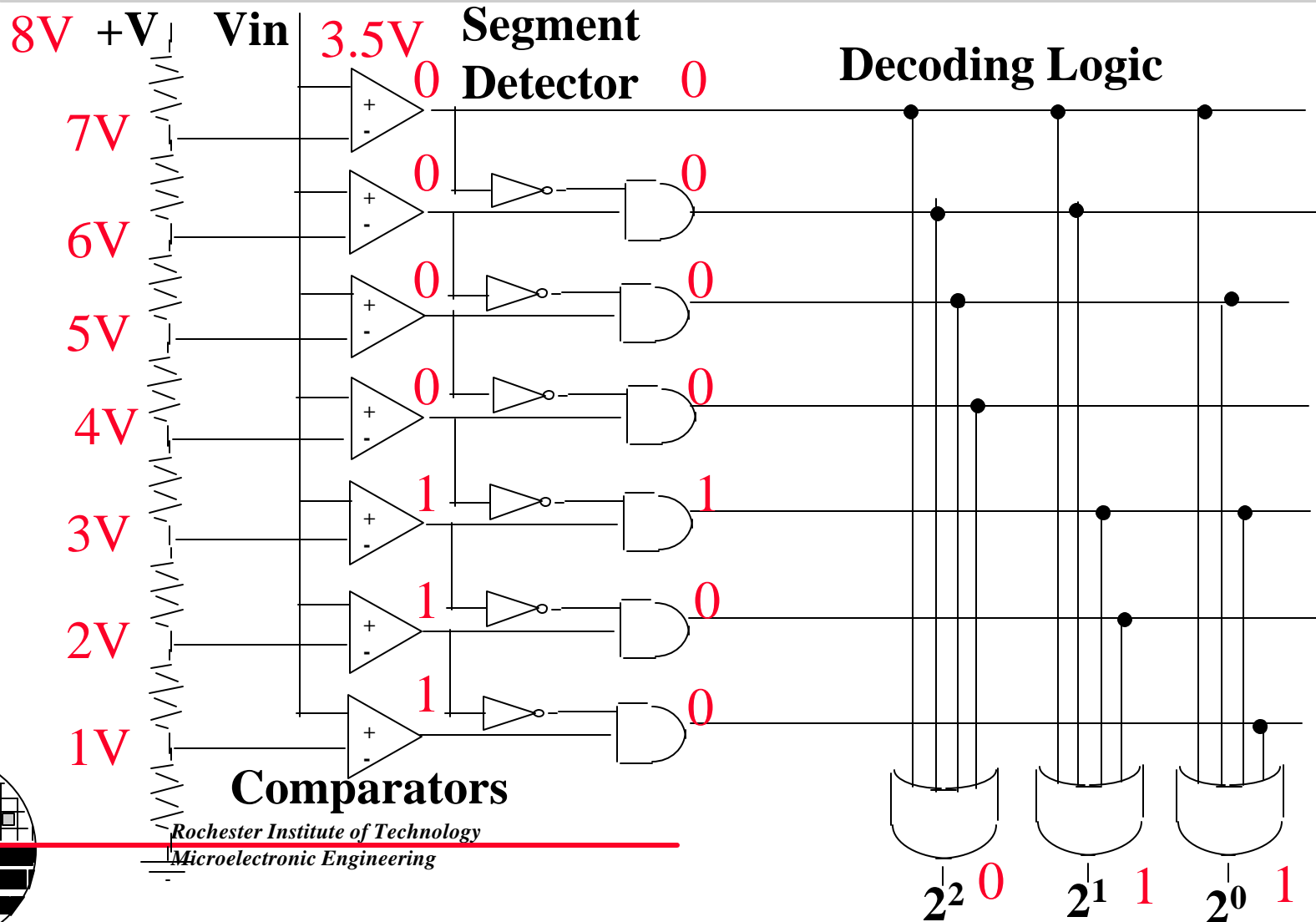


Rochester Institute of Technology
Microelectronic Engineering

LAYOUT OF FLASH A TO D

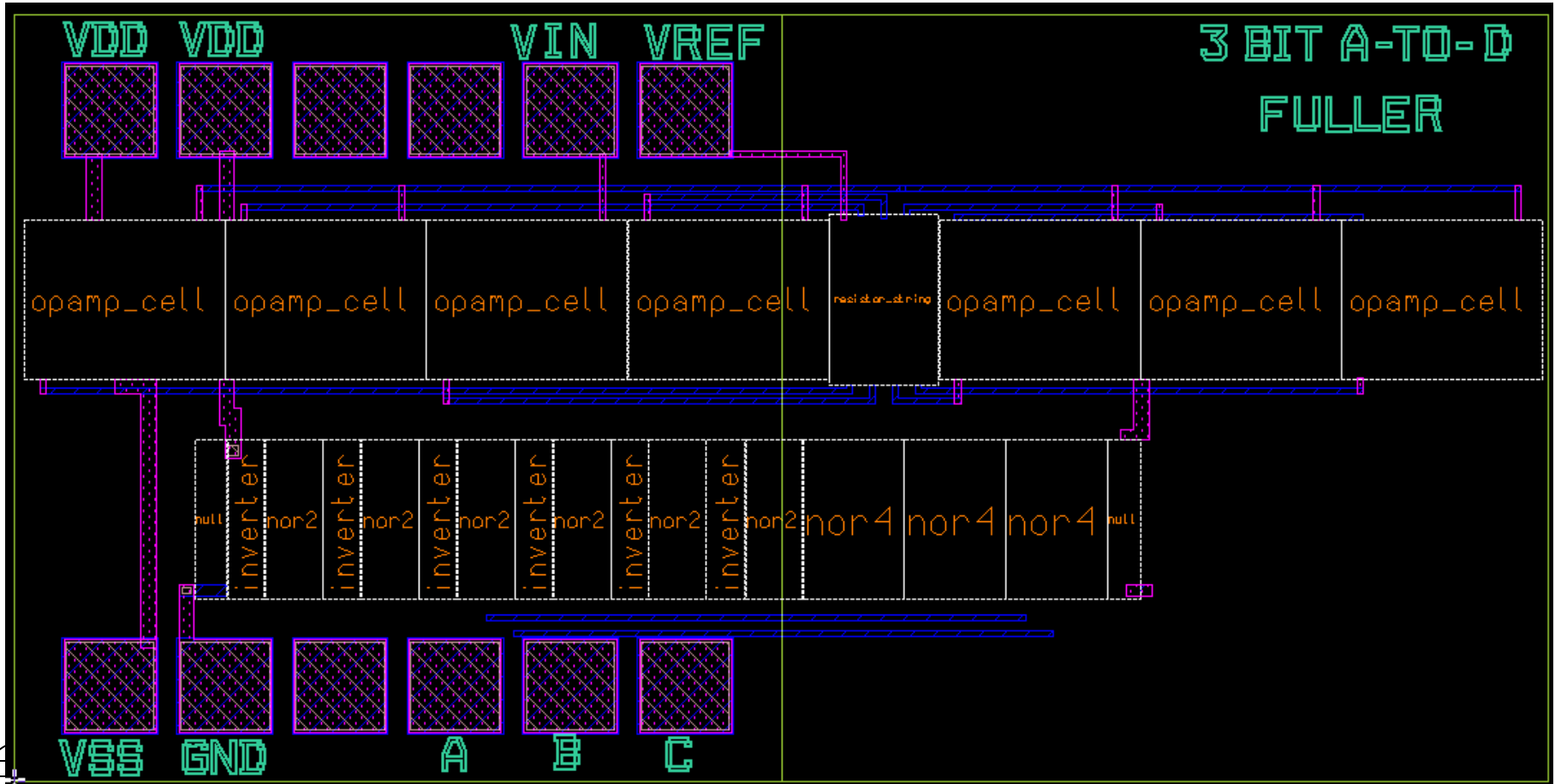


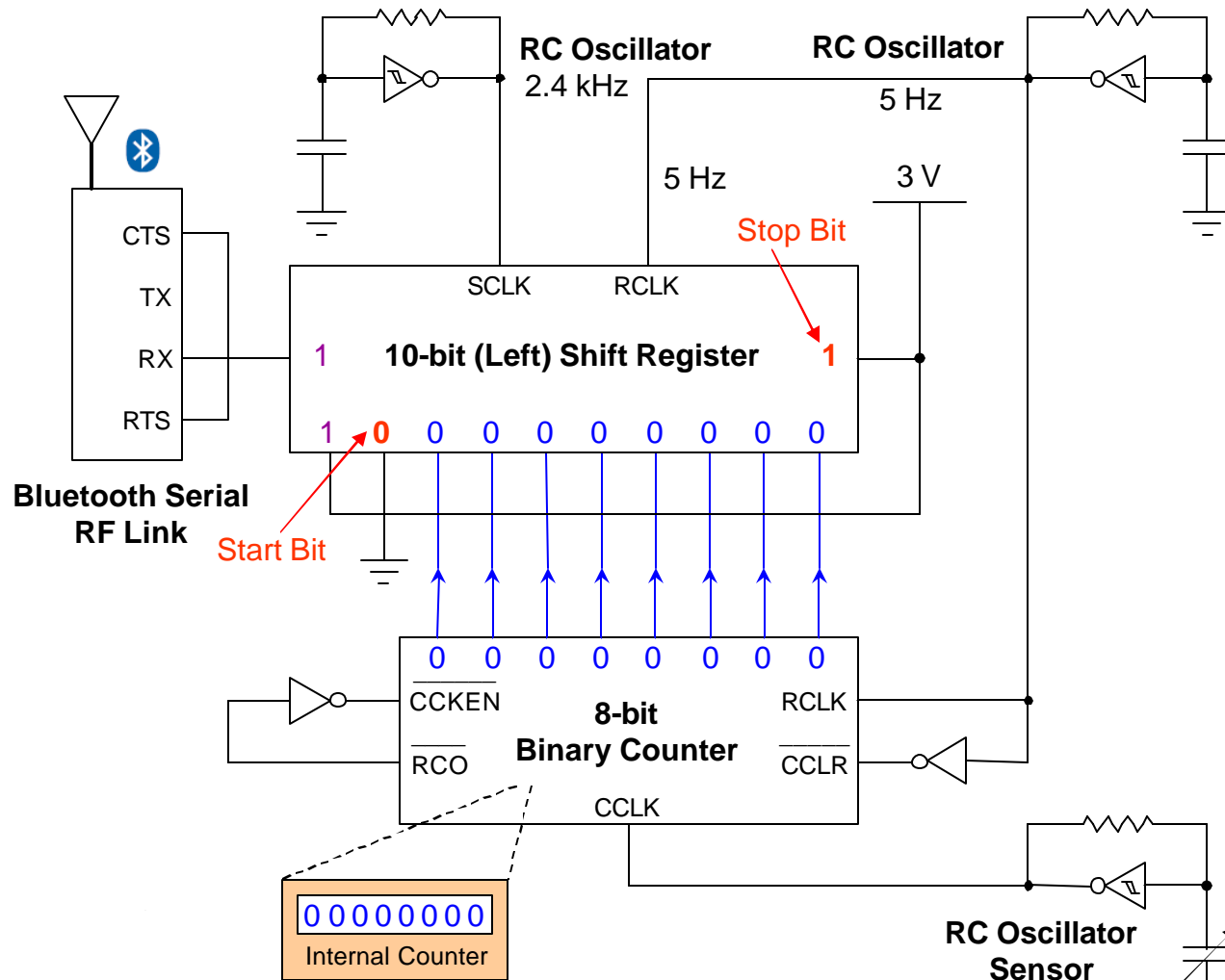WIRELESS CAPACITANCE TO DIGITAL CONVERTER



UP/DOWN COUNTER AND SHIFT REGISTERS


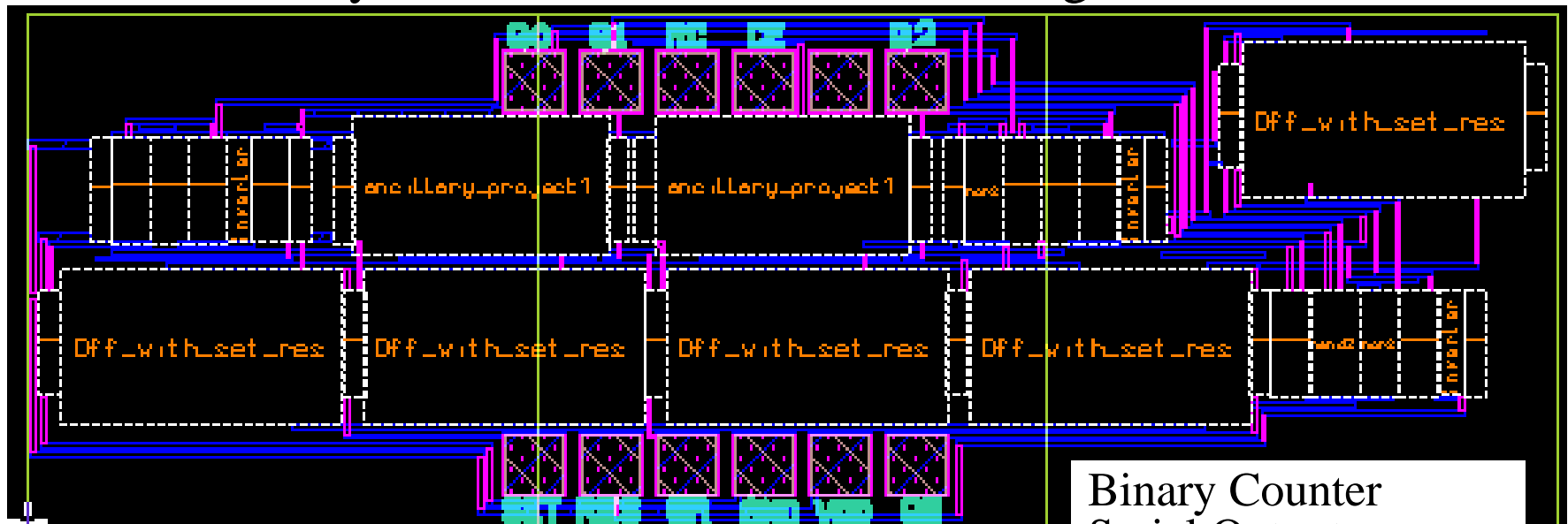
Many of these circuits need Up/Down counters and shift registers. In the next few pages we will look at one type of counter and see how to modify it to also function as a shift register.





Binary Counter
 Serial Output
 Asynchronous Reset
 Count Up Enable
 Shift Out Clock Input
 Count Up Clock Input
 Start Bit and Stop Bit

EDGE TRIGGERED D TYPE FLIP FLOP


Positive Edge Triggered D FF

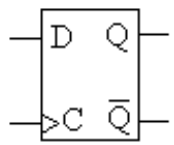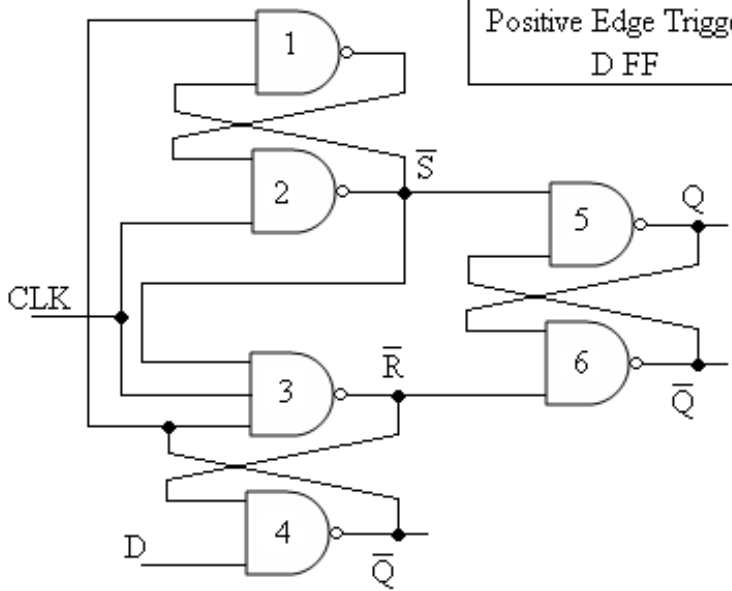

Inputs		Outputs	
D	C	Q	Q̄
0	↑	0	1
1	↑	1	0
X	0	Q	Q̄
X	1	Q	Q̄

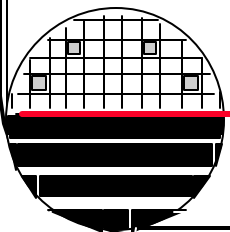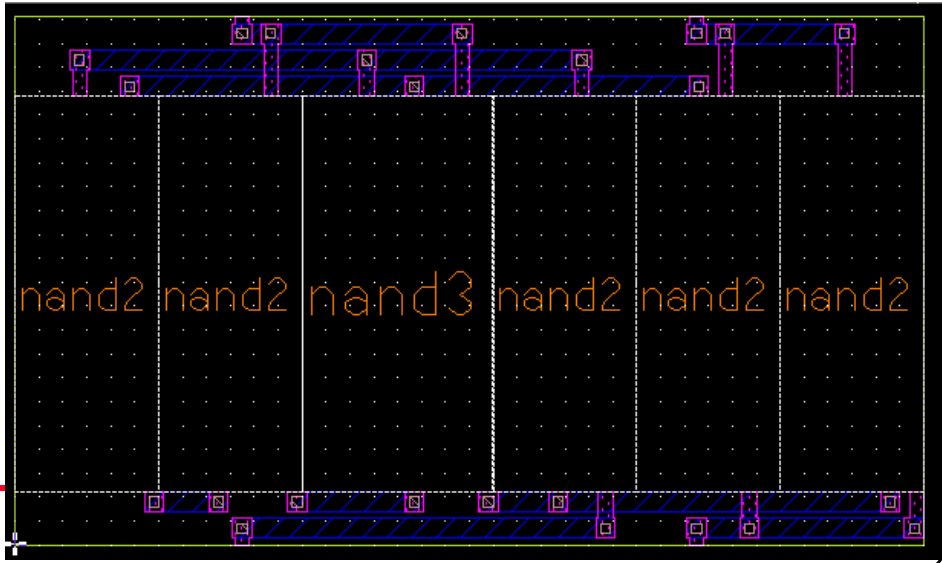


D (Edge Triggered) Flip Flop Realization

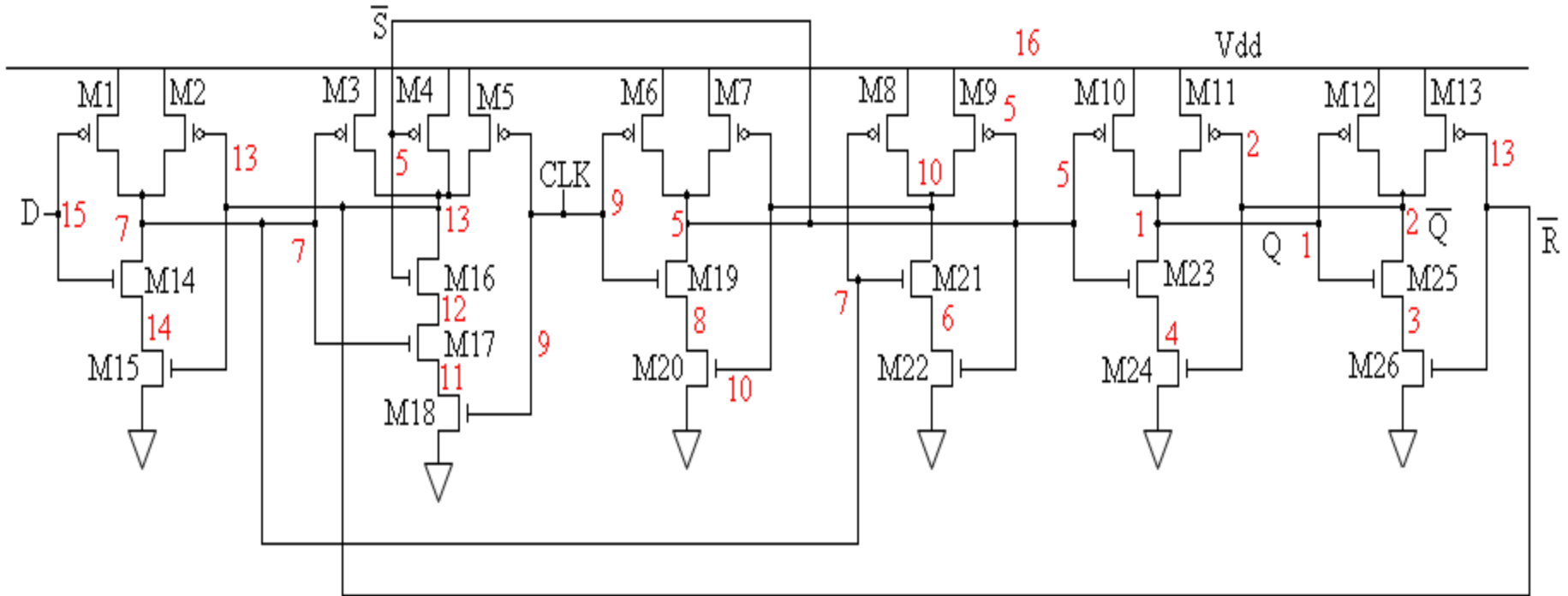


D FF (Edge Triggered) Input File:


```
.incl rit_sub_param.txt
m1 7 15 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m2 7 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m3 13 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m4 13 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m5 13 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m6 5 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m7 5 10 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m8 10 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m9 10 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m10 1 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m11 1 2 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m12 2 1 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m13 2 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m14 7 15 14 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m15 14 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m16 13 5 12 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m17 12 7 11 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m18 11 9 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m19 5 9 8 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m20 8 10 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m21 10 7 6 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m22 6 5 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m23 1 5 4 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m24 4 2 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m25 2 1 3 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m26 3 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
vdd 16 0 3
vd 15 0 PULSE(0 3 0NS 0NS 0NS 150NS 300NS)
vclock 9 0 PULSE(0 3 5NS 0NS 0NS 100NS 200NS)
*****transient*****
.tran 0.1n 0.5u
.end
```

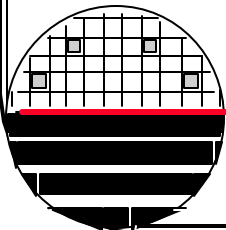



EDGE TRIGGERED D FF SIMULATION RESULTS

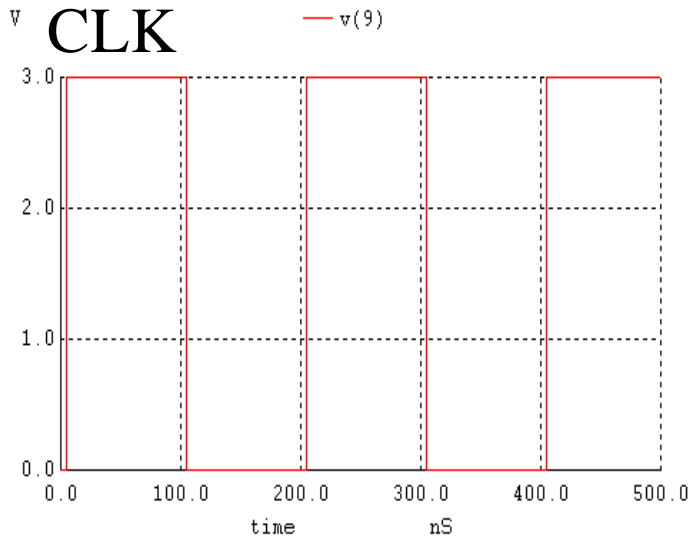


D

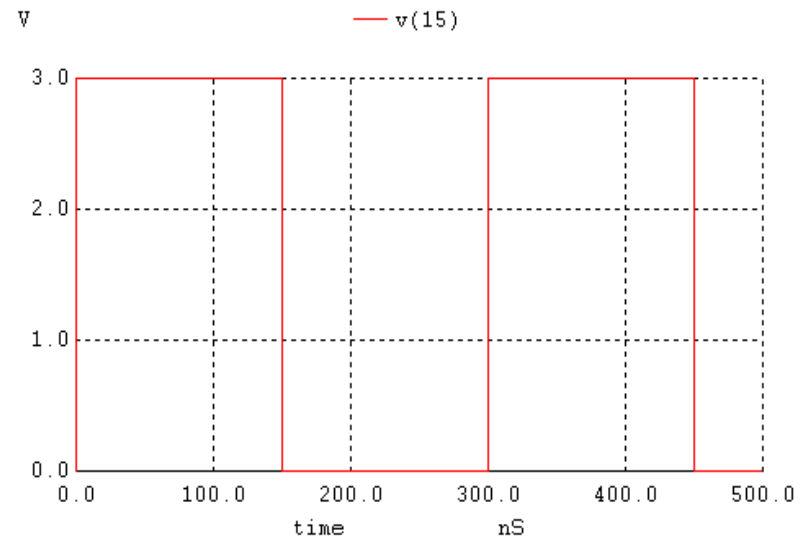


Q

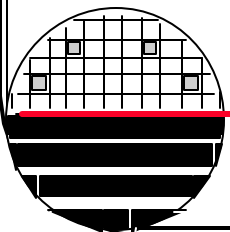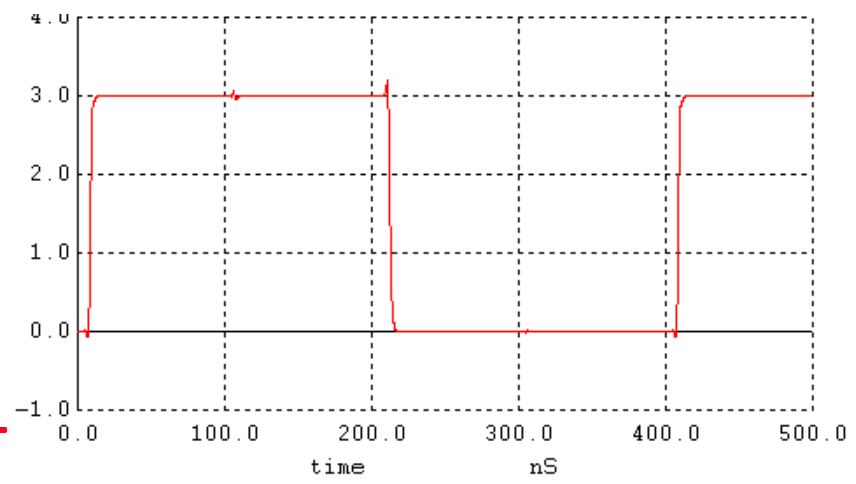


JK FLIP FLOP

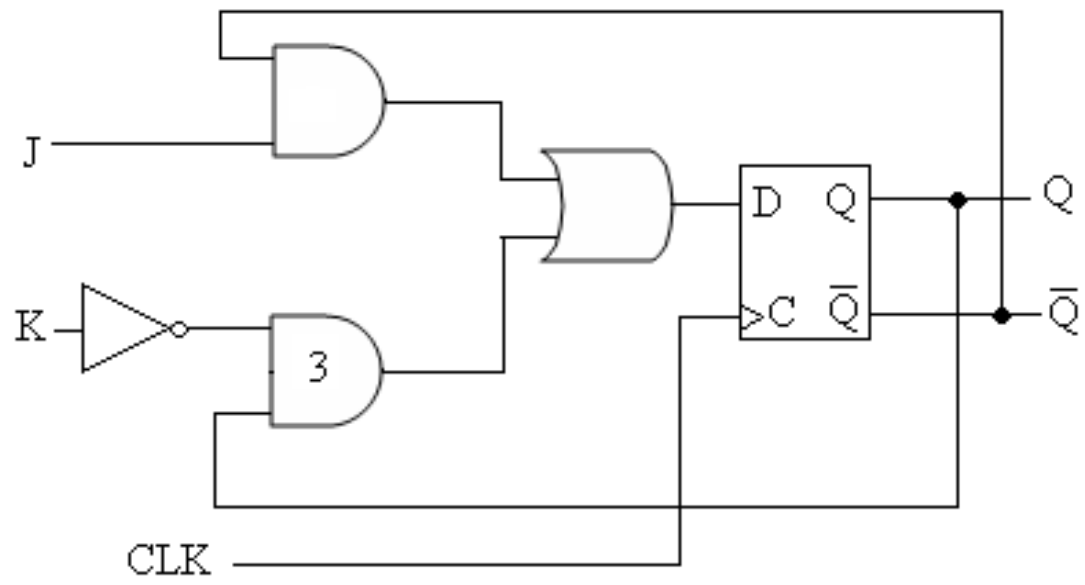



Positive Edge Triggered JK FF

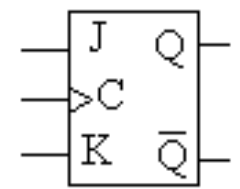

Inputs			Outputs	
J	K	C	Q^+	Q^+
0	0	↑	Q	\overline{Q}
0	1	↑	0	1
1	0	↑	1	0
1	1	↑	\overline{Q}	Q
X	X	0	Q	\overline{Q}
X	X	1	Q	\overline{Q}

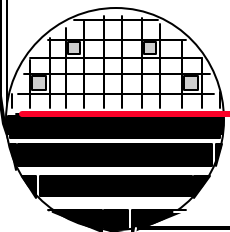

Modification to Convert D FF to JK FF

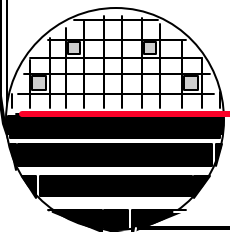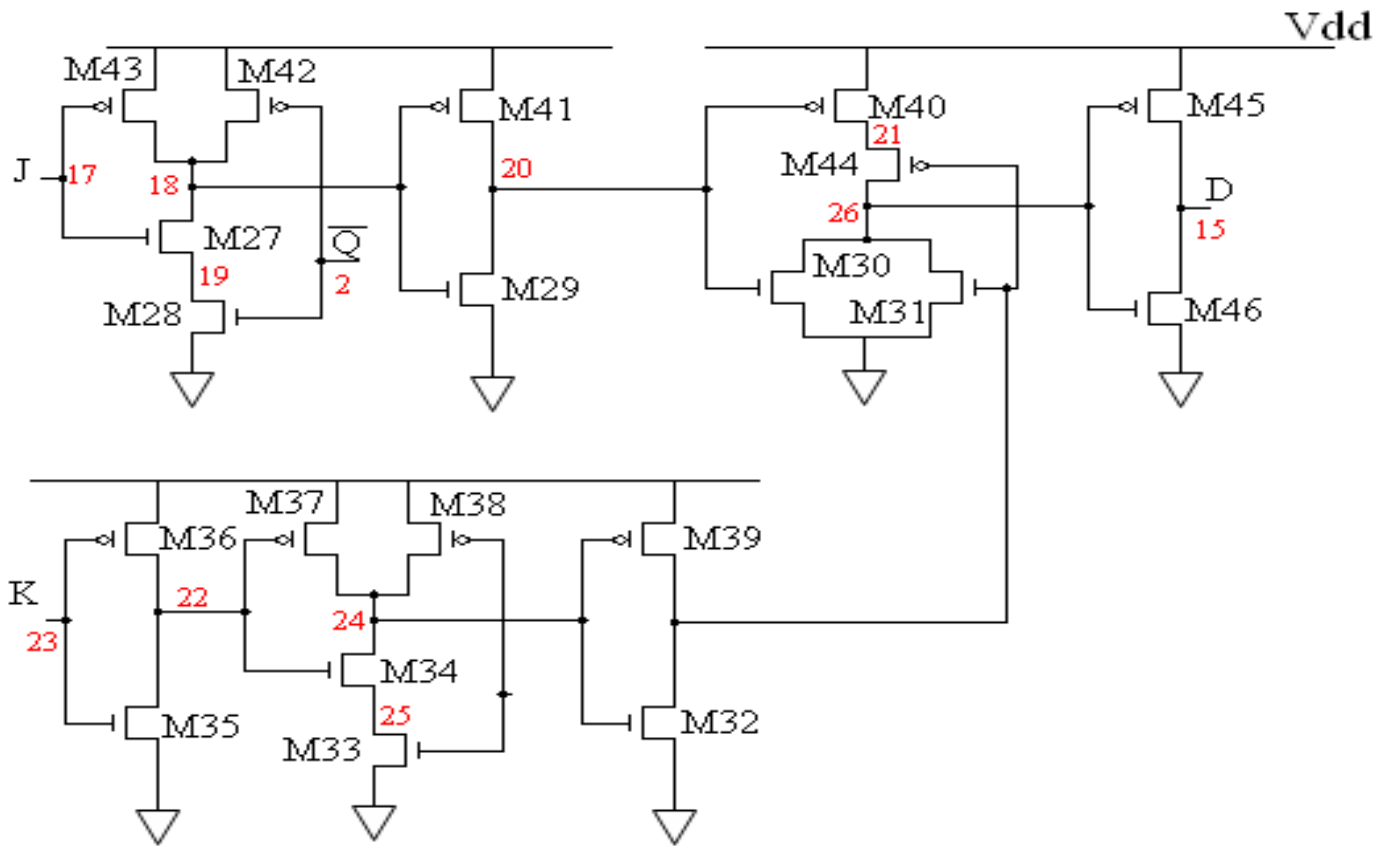

JK FF Input File:


```
.incl rit_sub_param.txt
m1 7 15 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m2 7 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m3 13 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m4 13 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m5 13 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m6 5 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m7 5 10 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m8 10 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m9 10 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m10 1 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m11 1 2 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m12 2 1 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m13 2 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m14 7 15 14 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m15 14 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m16 13 5 12 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m17 12 7 11 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m18 11 9 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m19 5 9 8 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m20 8 10 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m21 10 7 6 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m22 6 5 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m23 1 5 4 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m24 4 2 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m25 2 1 3 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m26 3 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
```

Transistors 27-46 on next page





JK FF Input File:

```
vdd 16 0 3
vj 17 0 PULSE(0 3 0NS 0NS 0NS 100NS 150NS)
vk 23 0 PULSE(0 3 0NS 0NS 0NS 50NS 100NS)
vclock 9 0 PULSE(0 3 50NS 0NS 0NS 50NS 150NS)
*****
m27 18 17 19 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m28 19 2 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m29 20 18 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m30 26 20 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m31 26 25 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m32 25 24 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m33 25 1 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m34 24 22 25 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m35 22 23 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m36 22 23 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m37 24 22 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m38 24 1 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m39 25 24 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m40 21 20 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m41 20 18 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m42 18 2 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m43 18 17 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m44 26 25 21 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m45 15 26 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m46 15 26 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
*****transient*****
.tran 0.1n 0.5u
.end
```

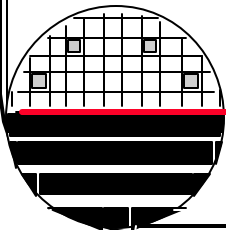
Rochester Institute of Technology
Microelectronic Engineering



JK FF Simulation Output:

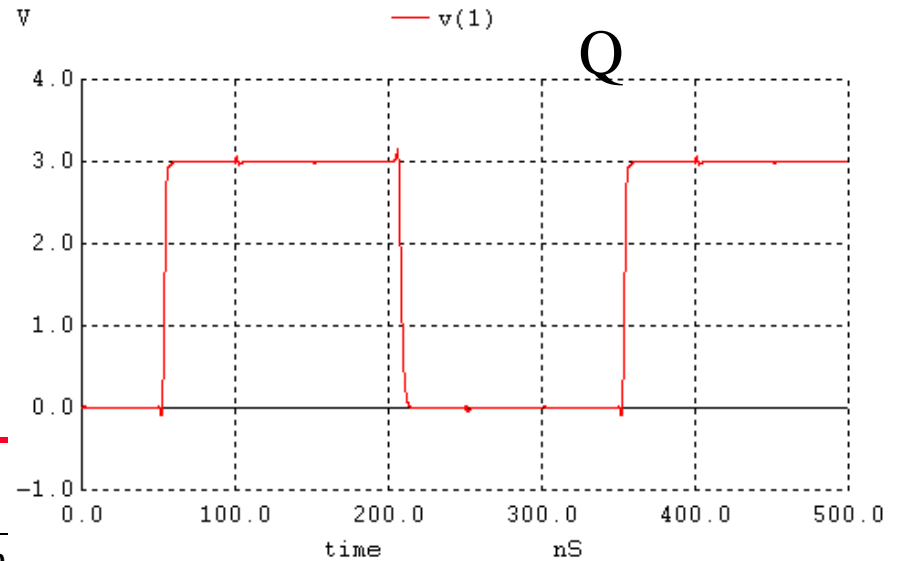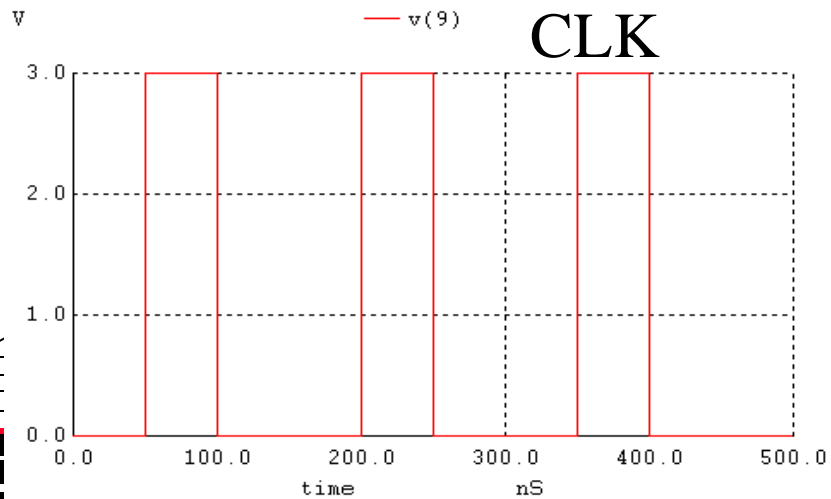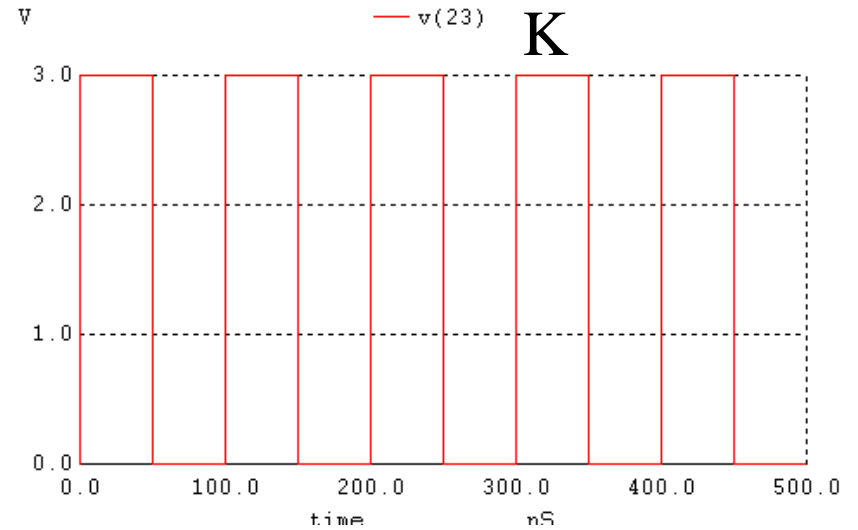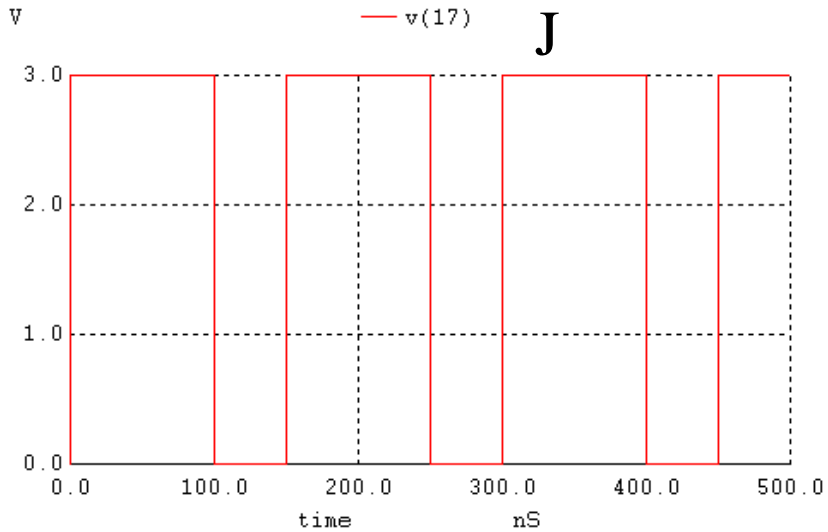

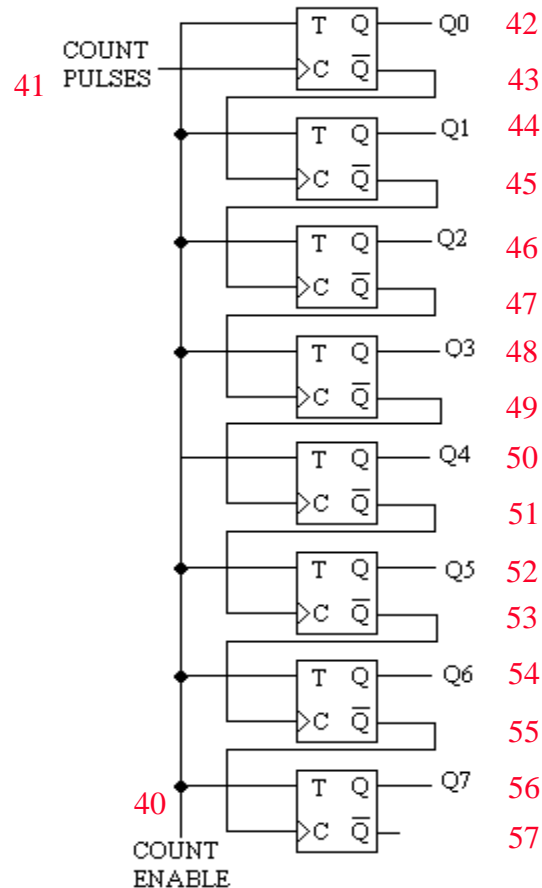Constructing 8 bit Binary Counter Using T FF



T Flip Flop is a JK FF
With J and K connected
together and labeled T

8 Bit Binary Counter Input File:

```
.incl rit_sub_param.txt
.subckt Tff 17 9 1 2
m1 7 15 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m2 7 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m3 13 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m4 13 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m5 13 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m6 5 9 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m7 5 10 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m8 10 7 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m9 10 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m10 1 5 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m11 1 2 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m12 2 1 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m13 2 13 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m14 7 15 14 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m15 14 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m16 13 5 12 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m17 12 7 11 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m18 11 9 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m19 5 9 8 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m20 8 10 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m21 10 7 6 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m22 6 5 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m23 1 5 4 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m24 4 2 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m25 2 1 3 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m26 3 13 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
vd 16 0 3
vjk 17 23 dc 0
*****
```



8 Bit Binary Counter Input File:

```


m27 18 17 19 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m28 19 2 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m29 20 18 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m30 26 20 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m31 26 25 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m32 25 24 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m33 25 1 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m34 24 22 25 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m35 22 23 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u
m36 22 23 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m37 24 22 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m38 24 1 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m39 25 24 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m40 21 20 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m41 20 18 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m42 18 2 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m43 18 17 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m44 26 25 21 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m45 15 26 16 16 cmosp w=7.5u l=2u ad=35p pd=25u as=35p ps=25u
m46 15 26 0 0 cmosn w=3u l=2u ad=15p pd=16u as=15p ps=16u

```





```

.ends
xB0 40 41 42 43 Tff
xB1 40 43 44 45 Tff
xB2 40 45 46 47 Tff
xB3 40 47 48 49 Tff
xB4 40 49 50 51 Tff
xB5 40 51 52 53 Tff
xB6 40 53 54 55 Tff
xB7 40 55 56 57 Tff
Vcountenable 40 0 3
vcount 41 0 PULSE(3 0 0NS 0NS 0NS 50NS 100NS)
.tran 0.1n 13u
.end





```

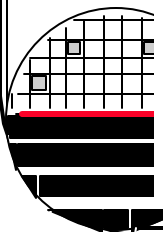




8 Bit Binary Counter Output:

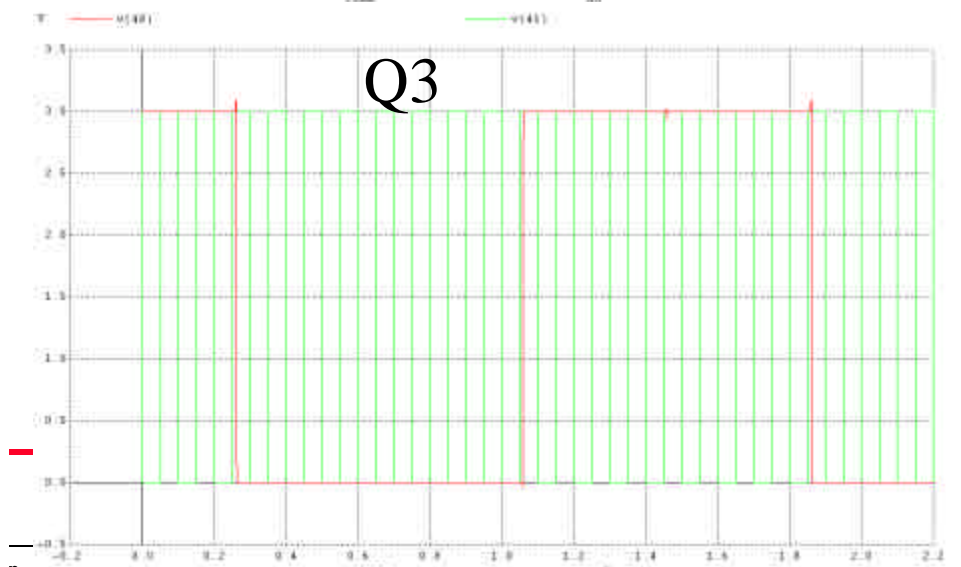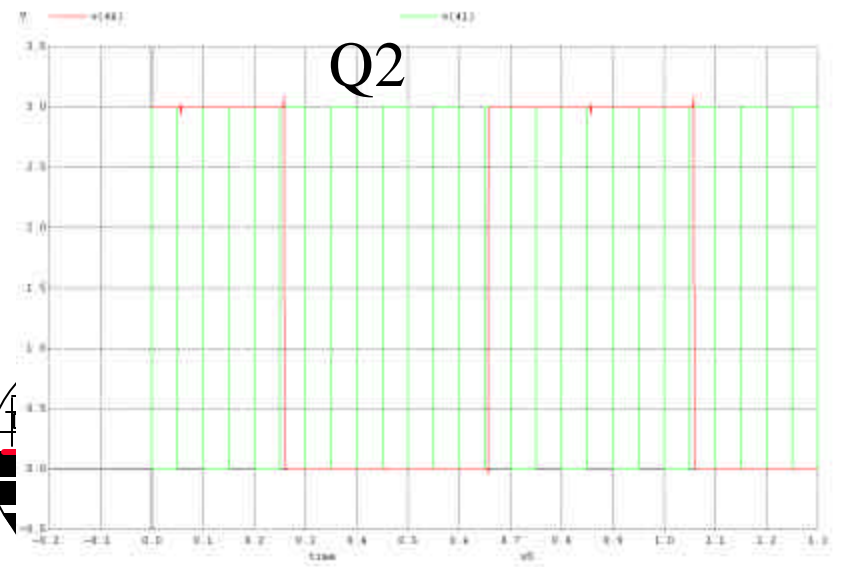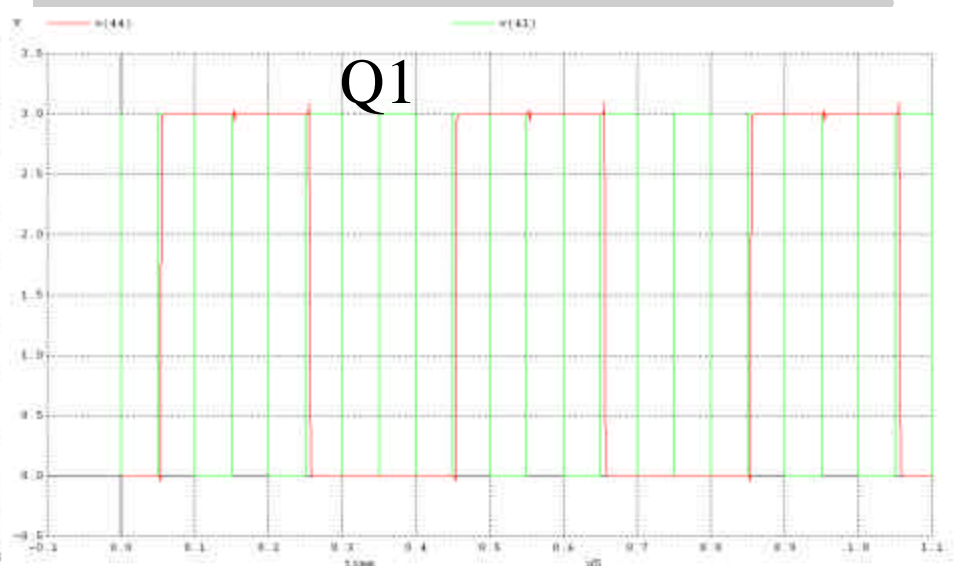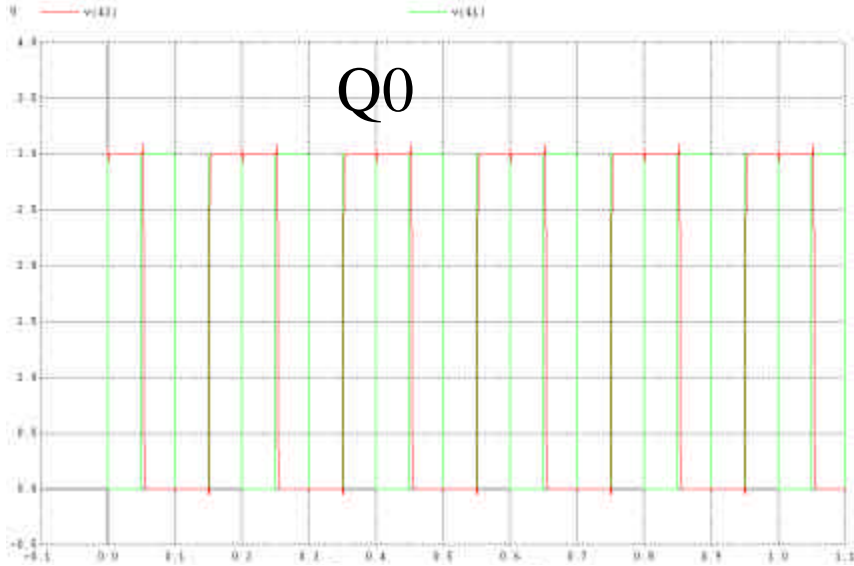



8 Bit Binary Counter Output:

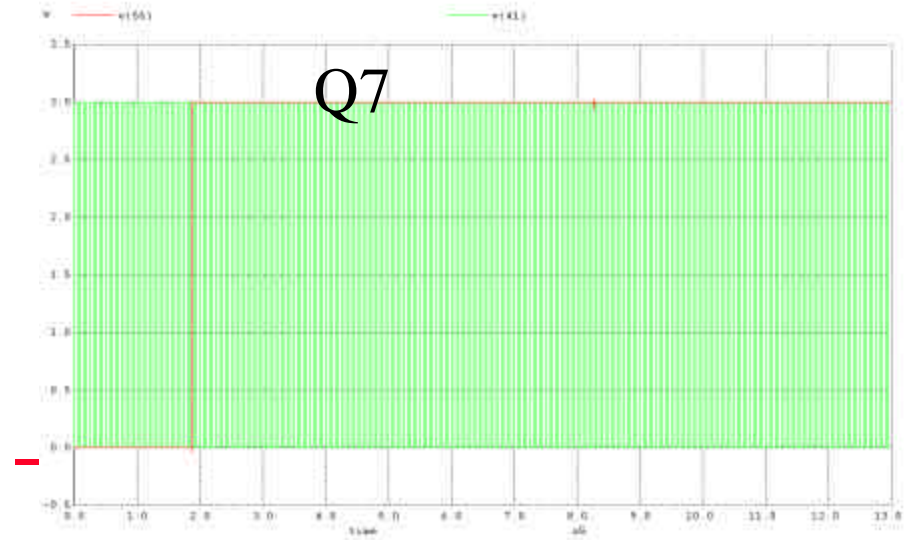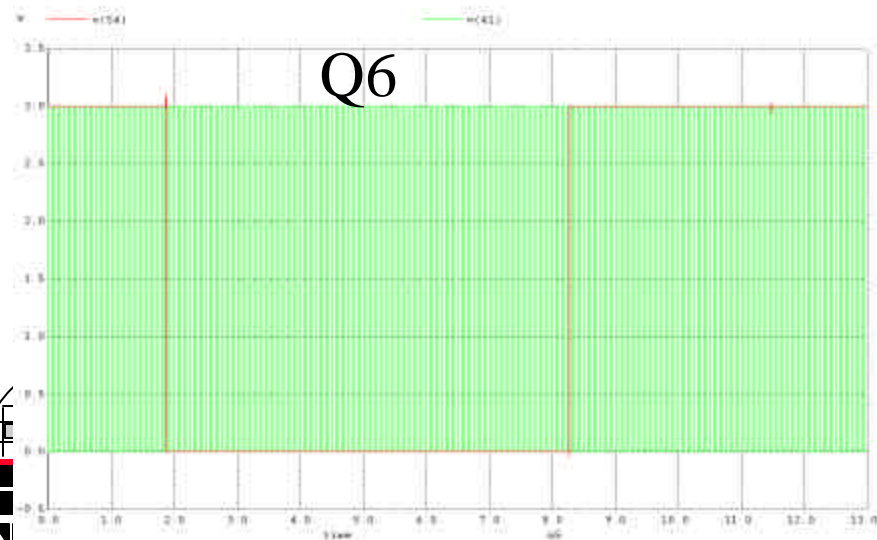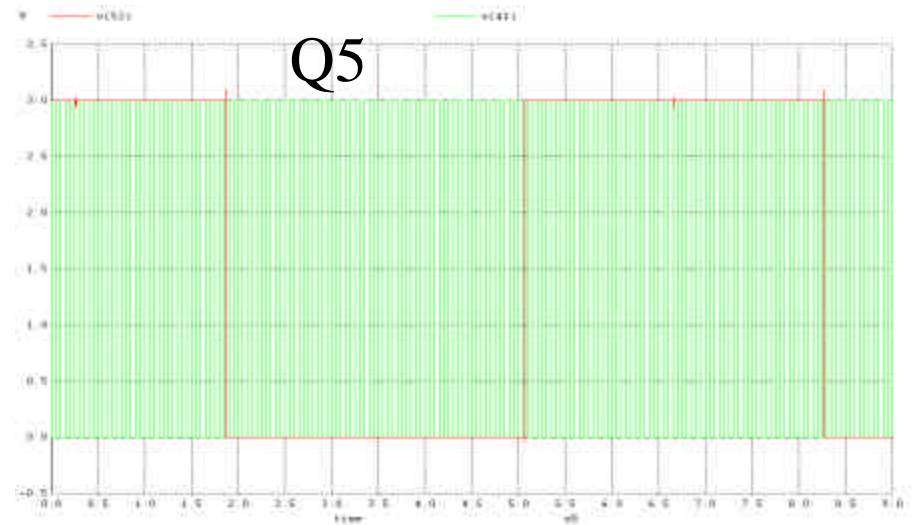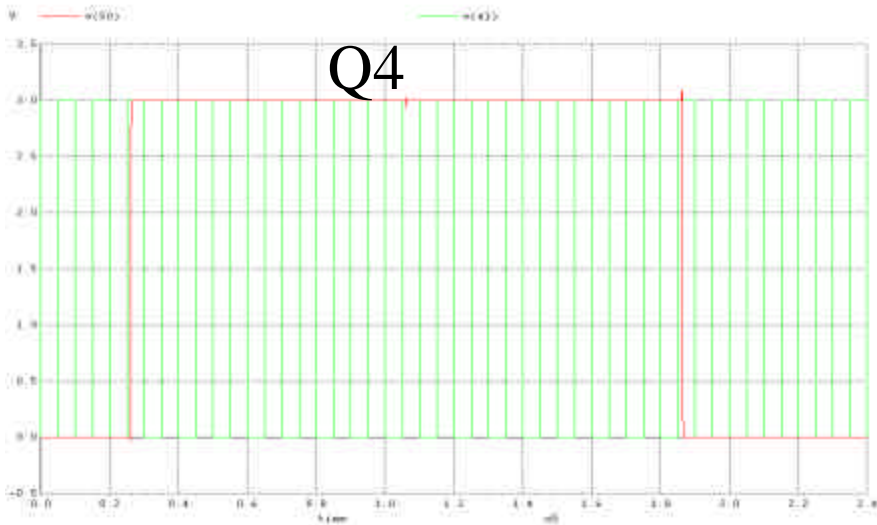



8-BIT BINARY COUNTER

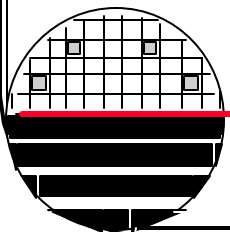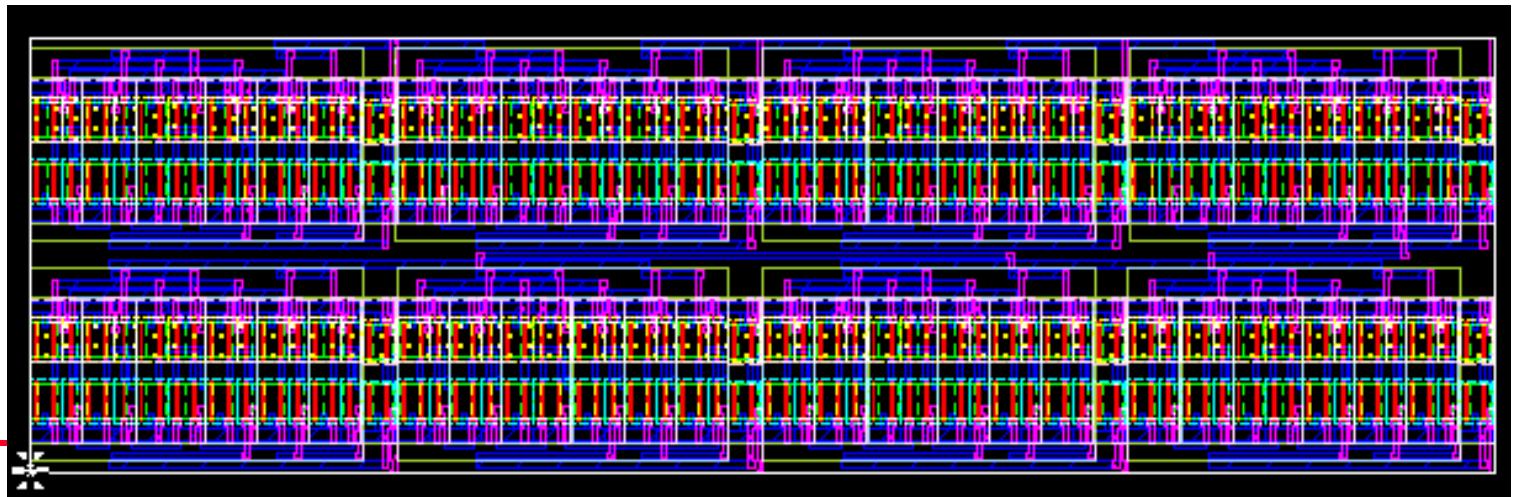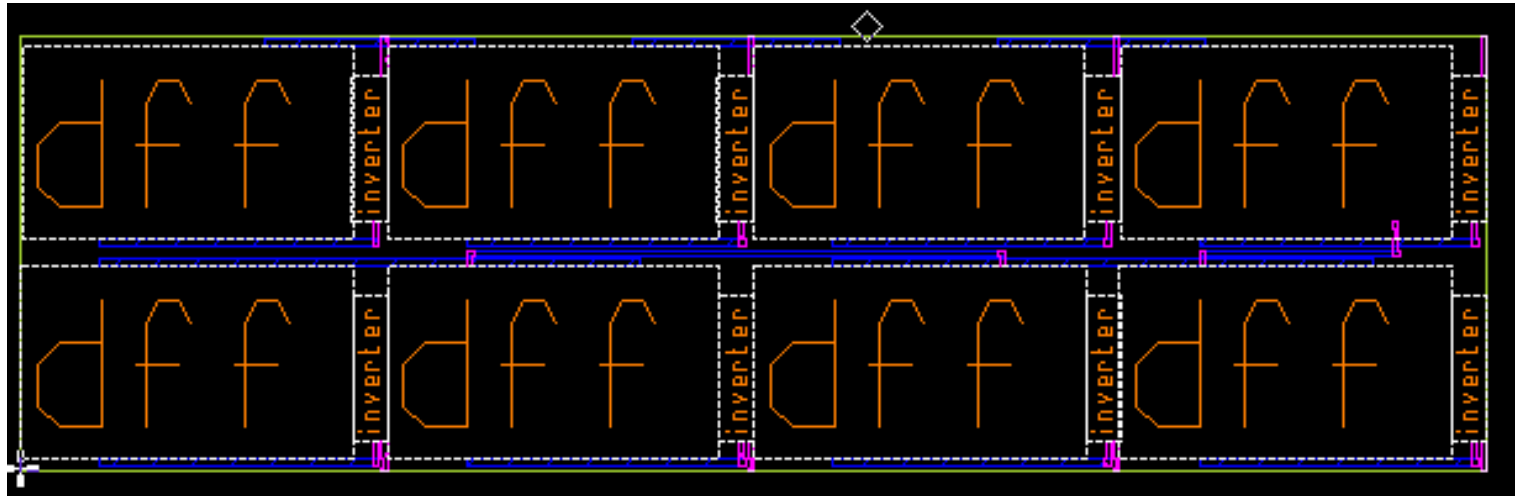

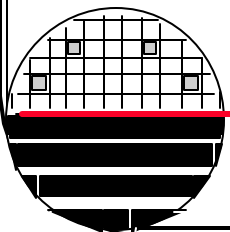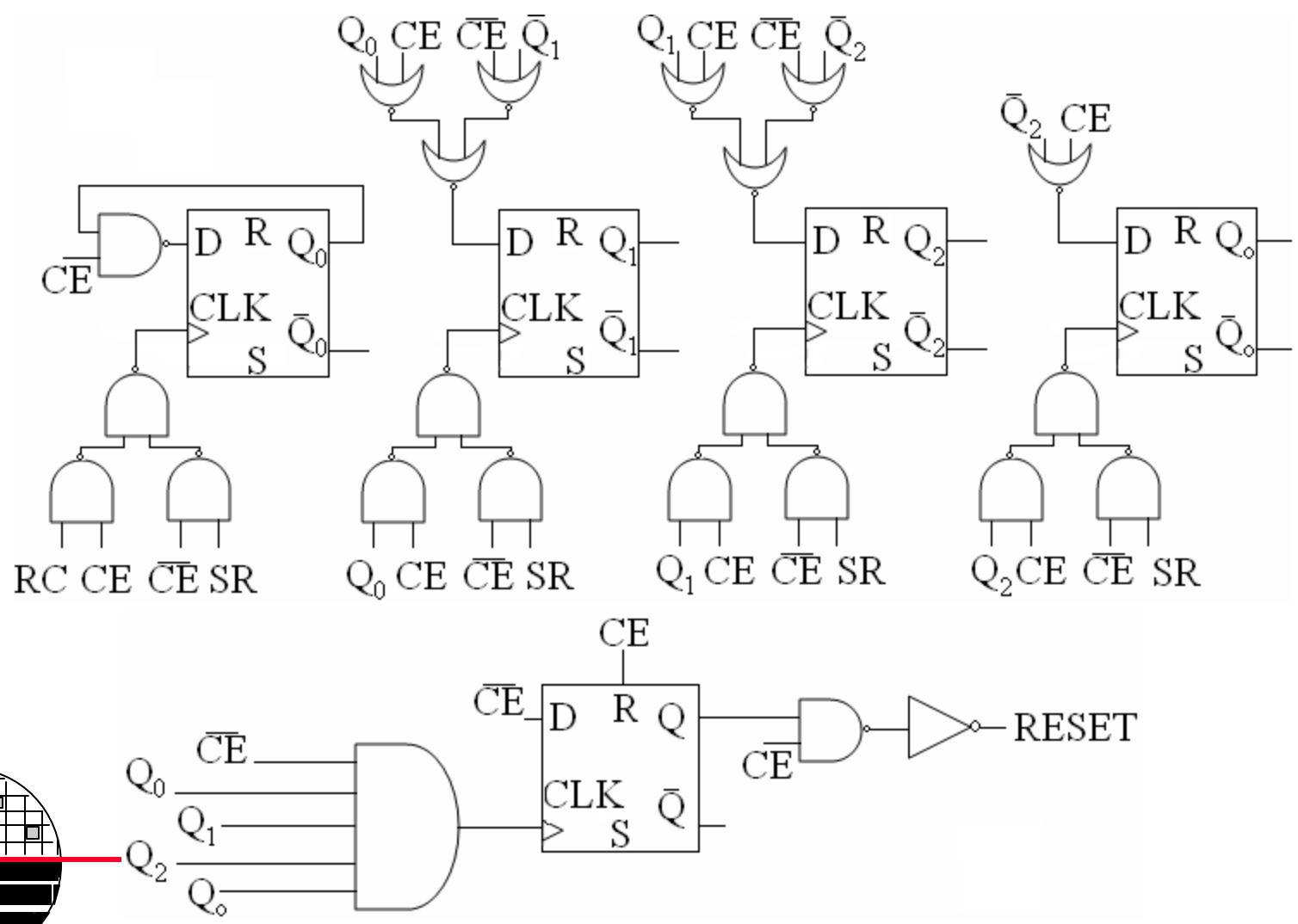
ADDITIONAL CIRCUITRY TO RESET, SHIFT, COUNT





UP/DOWN COUNTER AND SHIFT REGISTERS

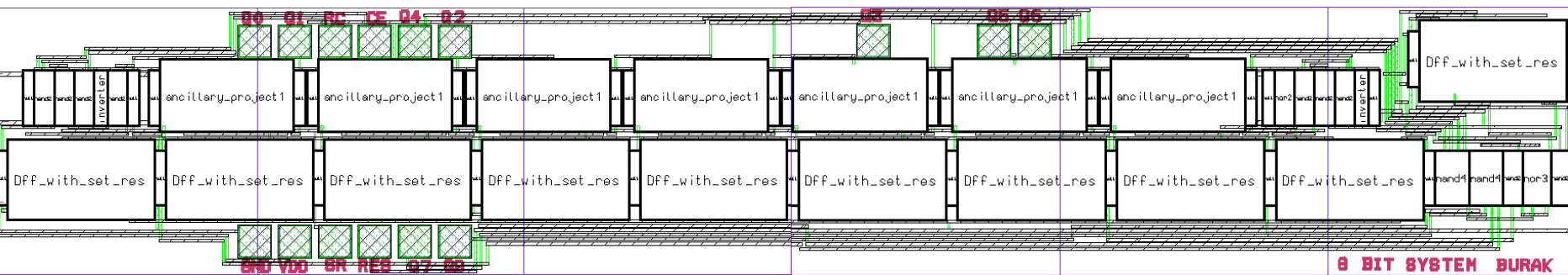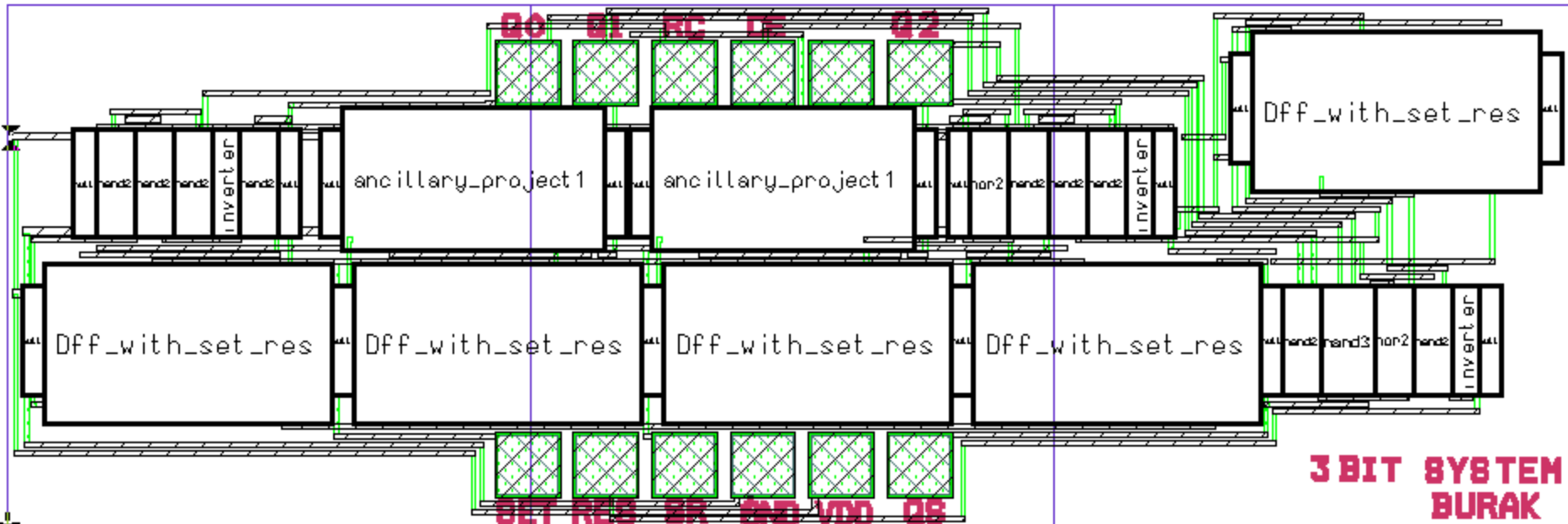

8-BIT BINARY COUNTER/SHIFT REGISTER

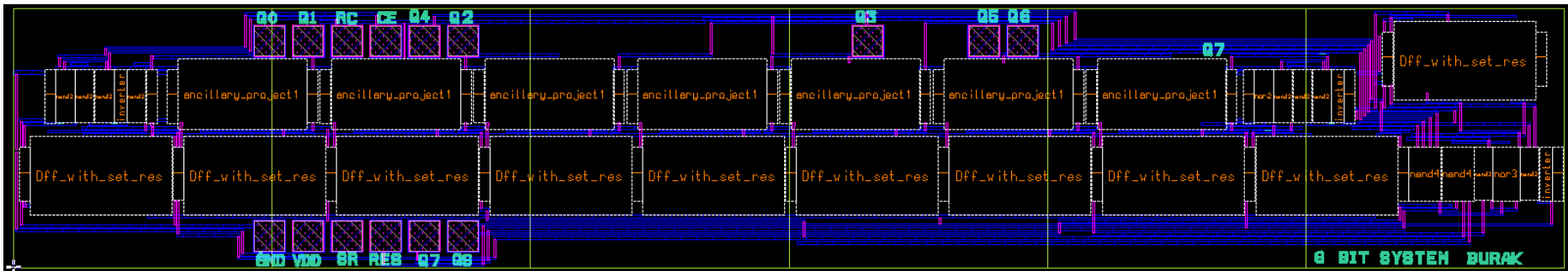

peek in 1 level

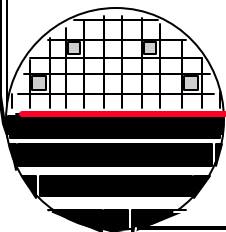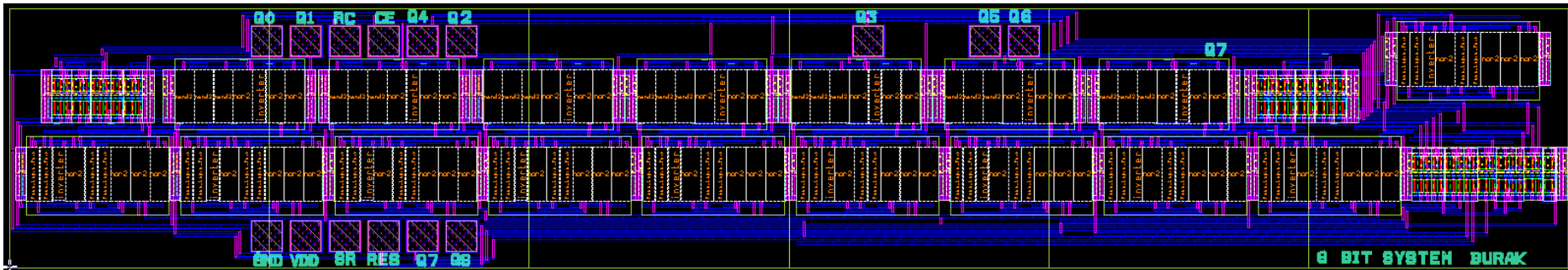

COUNTER AND SHIFT REGISTER



Data sheet acquired from Harris Semiconductor
SCHS037

CMOS 8-Stage Static Bidirectional Parallel/Serial Input/Output Bus Register

High-Voltage Types (20-Volt Rating)

■ CD4034B is a static eight-stage parallel-or serial-input parallel-output register. It can be used to:


1) bidirectionally transfer parallel information between two buses, 2) convert serial data to parallel form and direct the parallel data to either of two buses, 3) store (recirculate) parallel data, or 4) accept parallel data from either of two buses and convert that data to serial form. Inputs that control the operations include a single-phase CLOCK (CL), A DATA ENABLE (AE), ASYNCHRONOUS/SYNCHRONOUS (A/S), A-BUS-TO-B-BUS/B-BUS-TO-A-BUS (A/B), and PARALLEL/SERIAL (P/S).

Data inputs include 16 bidirectional parallel data lines of which the eight A data lines are

Applications:

- Parallel Input/Parallel Output, Serial Input/Parallel Output, Serial Input/Serial Output Register
- Shift right/shift left register
- Shift right/shift left with parallel loading
- Address register
- Buffer register
- Bus system register with enable parallel lines at bus side
- Double bus register system
- Up-Down Johnson or Ring counter
- Pseudo-random code generators
- Sample and hold register (storage, counting, display)
- Frequency and phase comparator

CD4034B Types

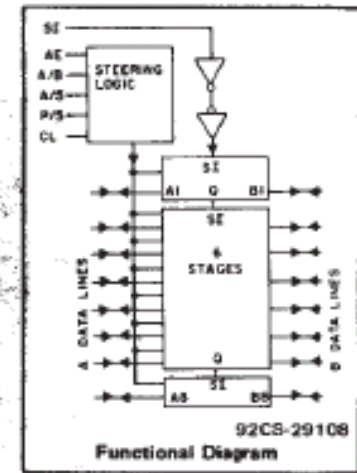


Features:

- Bidirectional parallel data input
- Parallel or serial inputs/parallel outputs
- Asynchronous or synchronous parallel data loading
- Parallel data-input enable on "A" data

REFERENCES

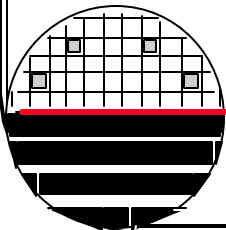1. Switched Capacitor Circuits, Phillip E. Allen and Edgar Sanchez-Sinencio, Van Nostrand Reinhold Publishers, 1984.
2. “Active Filter Design Using Operational Transconductance Amplifiers: A Tutorial,” Randall L. Geiger and Edgar Sanchez-Sinencio, IEEE Circuits and Devices Magazine, March 1985, pg. 20-32.
3. Microelectronic Circuits, 5th Edition, Sedra and Smith, Chapter 9 section 9.7-9.9



HOMWORK – DATA CONVERSION

1. Create two good homework problems and their solution related to the material covered in this document. (for next years students)
- 2.

