

**ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING**

Frequency Response of the CE Amplifier


Dr. Lynn Fuller

Webpage: <http://people.rit.edu/lffeee/>

Microelectronic Engineering
Rochester Institute of Technology
82 Lomb Memorial Drive
Rochester, NY 14623-5604
Tel (585) 475-2035

Email: Lynn.Fuller@rit.edu

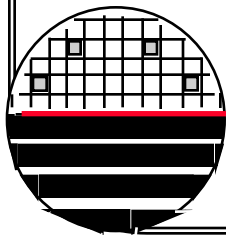MicroE webpage: <http://www.microe.rit.edu>



OUTLINE

Introduction

Gain Function and Bode Plots


Low Frequency Response of CE Amplifier

Millers Theorem

High Frequency Response of CE Amplifier


References

Homework Questions

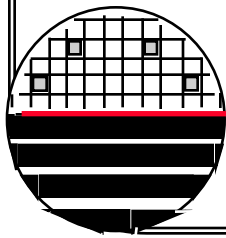

INTRODUCTION

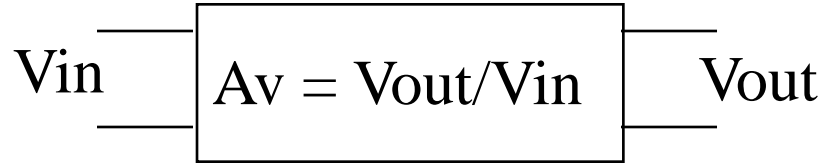We will be interested in the voltage gain of an electronic circuit as a function of frequency.



Decibel: the gain of some network can be expressed in logarithmic units. When this is done the overall gain of cascaded networks can be found by simple addition of the individual network gains.

The decibel is defined as:

$$A_p = 10 \log (P_o/P_{in}) \quad \text{dB}$$

where A_p is the power gain in decibels

P_o is the power out and P_{in} is the power in

The decibel has also been used as a unit for voltage gain.


$$P_o = V_{out}^2/RL \quad \text{and} \quad P_{in} = V_{in}^2/R_{in}$$

and if $R_{in}=RL$

$$A_p = 20 \log (V_{out}/V_{in}) \quad \text{dB}$$

INTRODUCTION

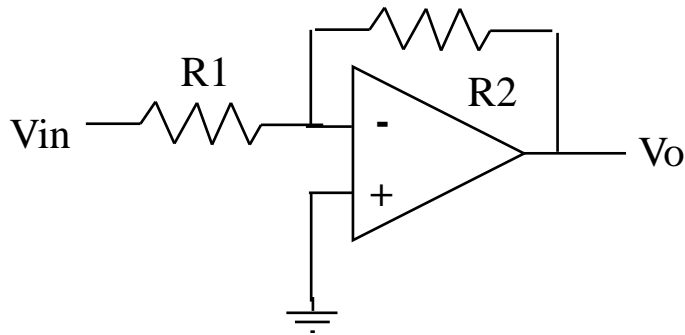
Thus the decibel is often used to express voltage gains. (Really only correct if $R_L = R_{in}$ but many people are not precise about this point)



If $R_1 = 2K$ and $R_2 = 47K$

$$V_o/V_{in} = -47K/2K = -23.5$$
$$|V_o/V_{in}| = 23.5 \text{ or } 27.4 \text{ dB}$$

Gain vs Frequency

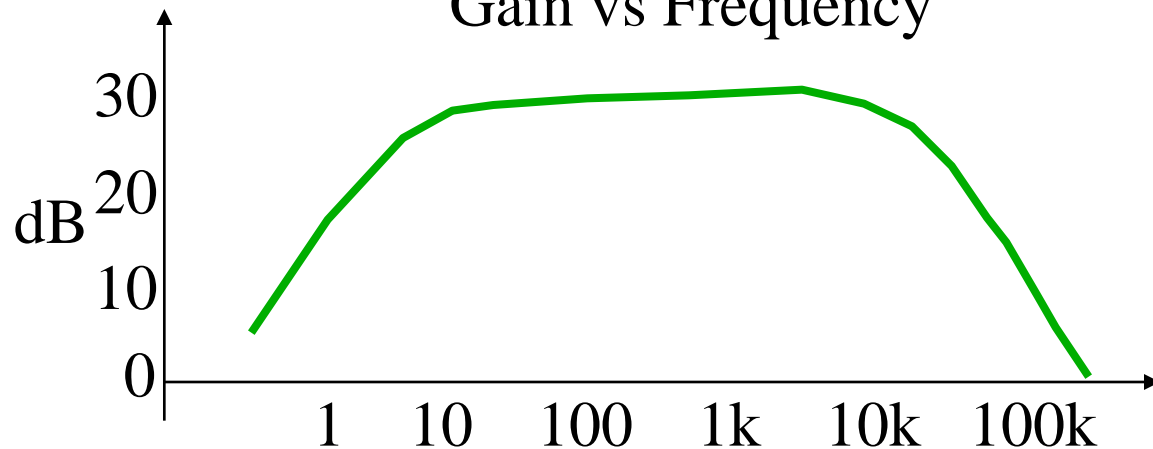

THE GAIN FUNCTION

The gain function, $A(s)$: an expression for V_o/V_{in} which is found in a straight forward manor from the ac equivalent circuit.

$V_o/V_{in} = A(s)$ or in particular $s=j\omega$ thus $A(j\omega)$


$$A(s) = \frac{a_0 + a_1 s + a_2 s^2 + a_3 s^3 \dots}{b_0 + b_1 s + b_2 s^2 + b_3 s^3 \dots}$$

$$A(s) = \frac{K (s-z_1)(s-z_2)(s-z_3)\dots}{(s-p_1)(s-p_2)(s-p_3)\dots}$$

Where z_1, z_2, z_3 are zeros, p_1, p_2, p_3 are poles


$$A(j\omega) = \frac{K (j\omega-z_1)(j\omega-z_2)(j\omega-z_3)\dots}{(j\omega-p_1)(j\omega-p_2)(j\omega-p_3)\dots}$$
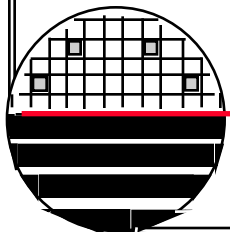
$$A(j\omega) = \frac{A_0 (j\omega/\omega_1)^N (j\omega/\omega_3+1)(j\omega/\omega_5+1)\dots}{(j\omega/\omega_2+1)(j\omega/\omega_4+1)(j\omega/\omega_6+1)\dots}$$



GOALS

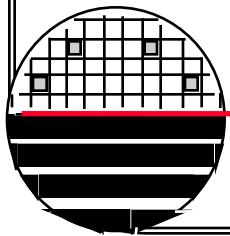
1. Obtain the gain function from the ac equivalent circuit.
2. Predict the frequency response of the gain function.
3. Use graphical techniques to sketch the frequency response
3. Introduce a new model for transistors at high frequencies.
5. Analyze and predict the frequency response of a common emitter amplifier stage



GRAPHICAL TECHNIQUES AND BODE PLOTS

Gain Function:



$$V_o = V_{in} \frac{1/sC}{R + 1/sC}$$

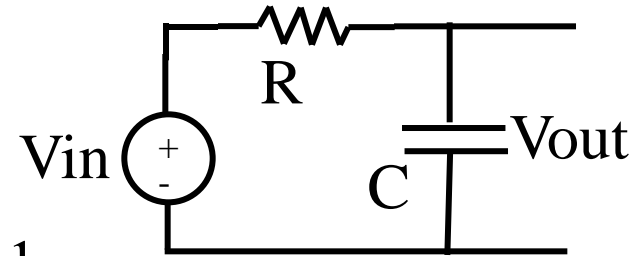

$$V_o/V_{in} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{j\omega RC + 1} = \frac{1}{j\omega/\omega_1 + 1}$$

Where $\omega_1 = 1/RC$ and $f_1 = 1 / 2 \pi RC$

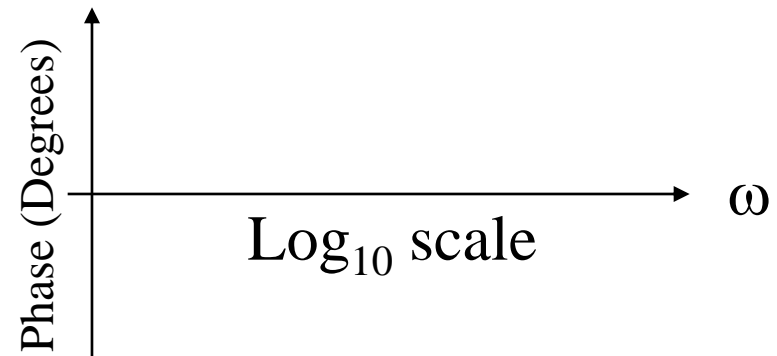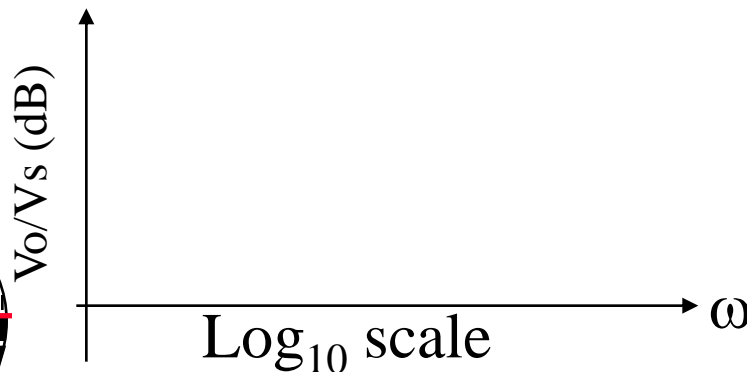Bode Plot: a plot of the gain function versus frequency (ω or f).
 Note: both magnitude and phase are a function of frequency. The Bode Plot plots this information separately.



CONTINUE PREVIOUS EXAMPLE 1

$$A_v = V_o/V_{in} = \frac{1}{j\omega/\omega_1 + 1}$$


At low ω $V_o/V_{in} = 1 \angle 0^\circ$; $|V_o/V_{in}|_{dB} = 0 \text{ dB}$ and $\Theta = 0^\circ$

At high ω $V_o/V_{in} = 1/(j\omega/\omega_1) \angle -90^\circ$
 $|V_o/V_{in}|_{dB} = \omega_1/\omega \text{ dB}$ and $\Theta = -90^\circ$




Note: at $\omega = 10 \omega_1$ $|V_o/V_{in}|_{dB} = -20 \text{ dB}$

Note: at $\omega = 100 \omega_1$ $|V_o/V_{in}|_{dB} = -40 \text{ dB}$

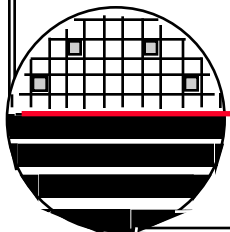Thus we see at high frequencies the gain decreases by -20 dB / decade




CONTINUE EXAMPLE 1

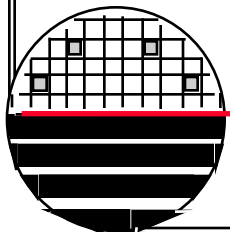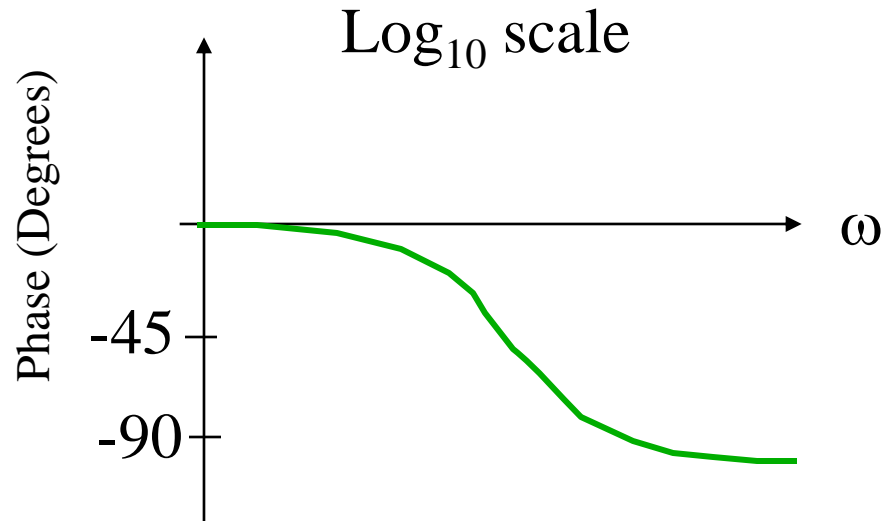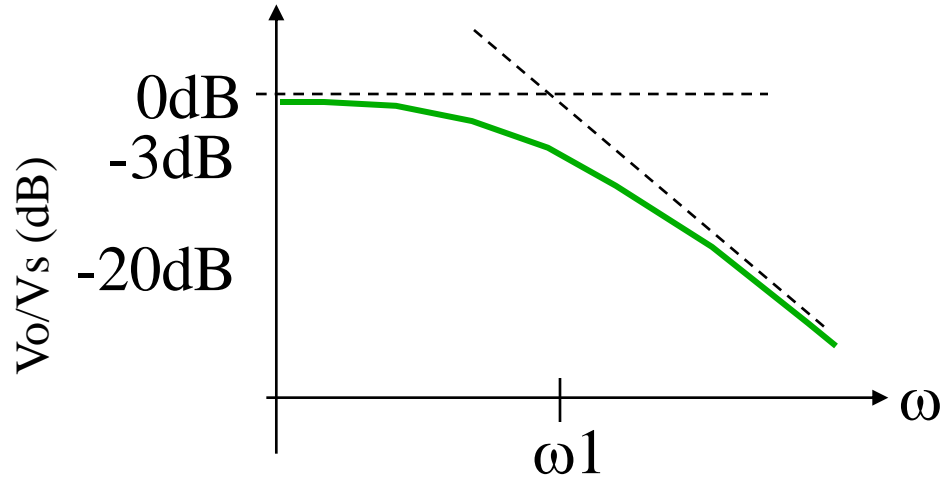

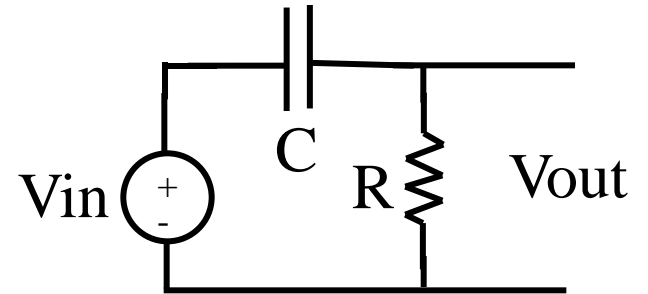EXAMPLE 2

Obtain the gain function for the network shown. Sketch the magnitude part of the Bode Plot.




POLES AND ZEROS

Poles and Zeros: the complex frequency at which the gain function goes to infinity in the case of poles or to zero in the case of zeros.


Example 1: $V_o/V_{in} = \frac{1}{sCR + 1}$

Pole at $s_1 = -1/RC$

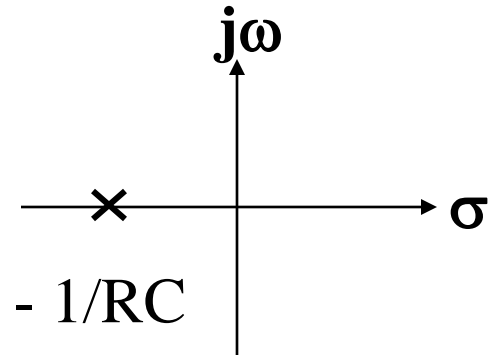

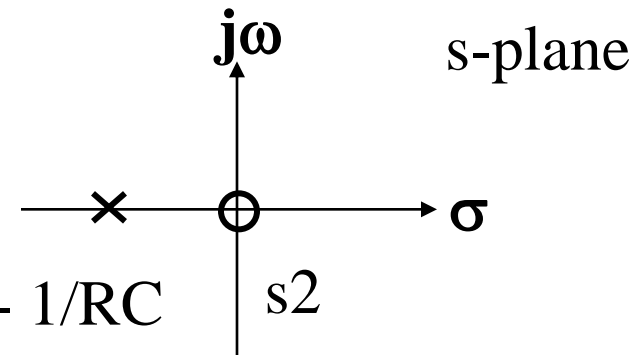Example 2: $V_o/V_{in} = \frac{sCR}{sCR + 1}$

Which has a Zero at zero and a Pole at $s_1 = -1/RC$



CORNER FREQUENCY


Corner frequencies: that frequency (f or ω) at which the real and imaginary parts of one term of the gain function are equal/

Example 1:
$$V_o/V_{in} = \frac{1}{j\omega CR + 1}$$

Has a corner at $\omega_1 = 1/RC$ or $f = 1/2\pi RC$


Example 2:
$$V_o/V_{in} = \frac{j\omega CR}{j\omega CR + 1}$$

Has a corner $\omega_1 = 1/RC$

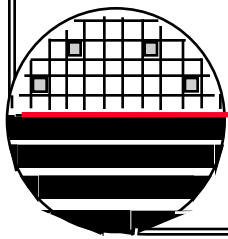

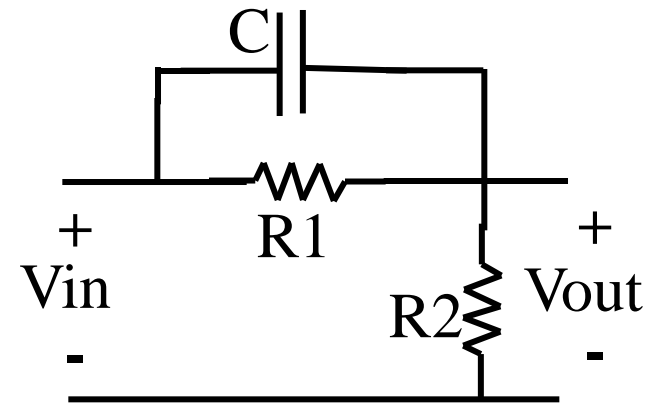EXAMPLE 3

Find the gain function, poles, zeros and corner frequencies for the network shown, sketch the Bode plot.



LOW FREQUENCY MODEL OF CE AMPLIFIER


Effect of the Coupling Capacitor, C_c
assume C_e , and C_{c2} act like a short.

Obtain the gain function from the ac equivalent circuit:

$$v_o = -g_m v_{be} R_y$$

$$v_{be} = \frac{v_s R_x}{(R_s + 1/sC_c + R_x)}$$

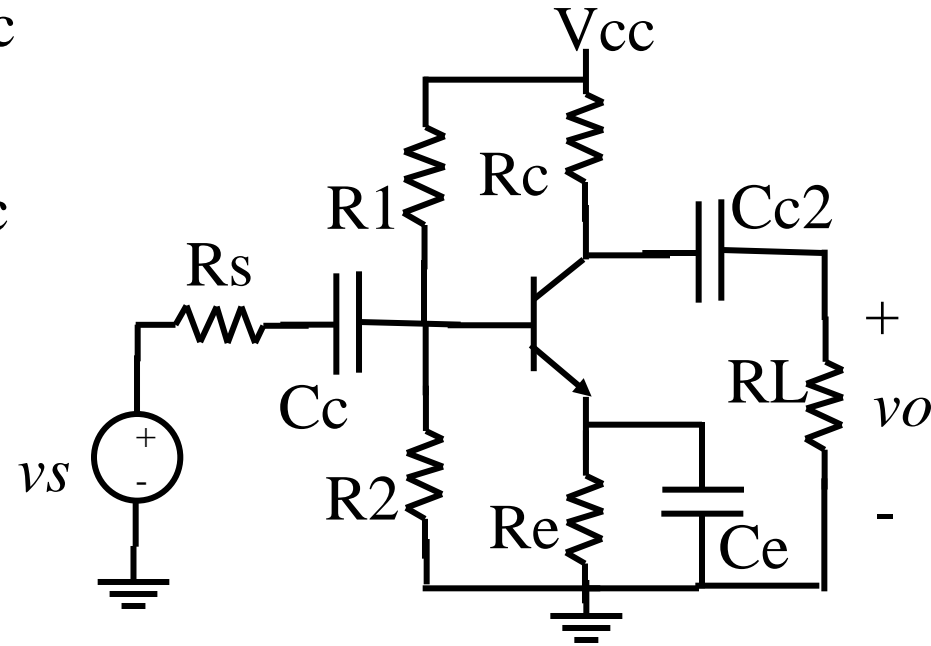
$$v_o/v_s = \frac{-g_m R_x R_y}{(R_s + 1/sC_c + R_x)}$$



$$R_x = R_{th} // r_{\pi}$$

$$R_y = r_o // R_c // R_L$$

$$s = j\omega$$

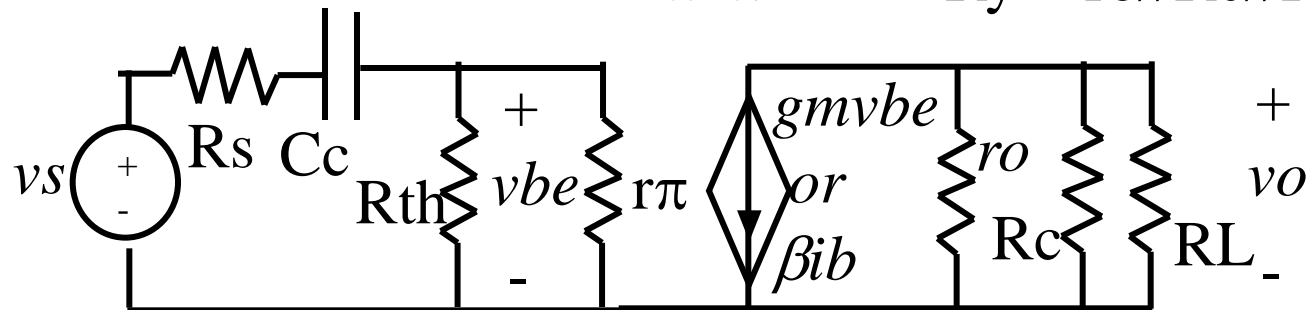

EFFECT OF COUPLING CAPACITOR C_c

Manipulate the gain function until we have a form from which we can easily obtain the bode plot.


$$v_o/v_s = -g_m R_y R_x \frac{s C_c}{(s C_c (R_s + R_x) + 1)} \quad 20 \log_{10} |A_{v \text{ mid}}|$$

$$v_o/v_s = -g_m R_y R_x \frac{s C_c (R_s + R_x)}{(s C_c (R_s + R_x) + 1)(R_s + R_x)}$$

$$v_o/v_s = \frac{-g_m R_y R_x}{(R_s + R_x)} \frac{s C_c (R_s + R_x)}{(s C_c (R_s + R_x) + 1)}$$

$$v_o/v_s = A_{v \text{ mid}} \frac{j \omega / \omega_1}{(j \omega / \omega_1 + 1)}$$

Where $\omega_1 = 1/C_c(R_s + R_x)$

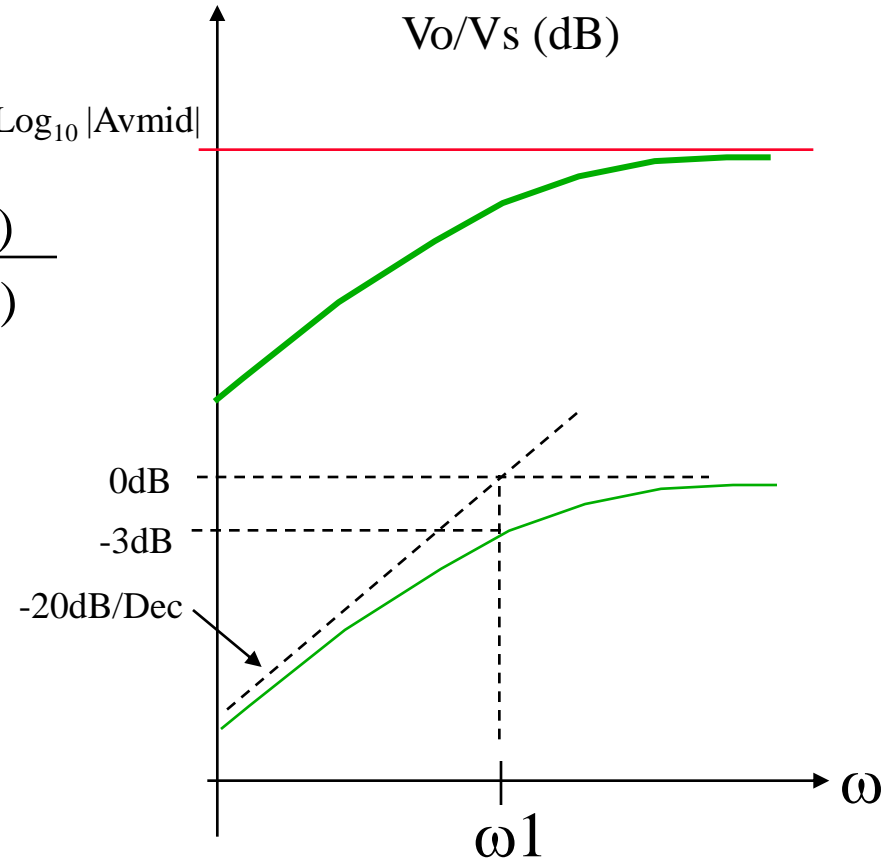

Log₁₀ scale

SUMMARY FOR EFFECT OF C_c


1. At low frequencies the coupling capacitor “opens” up and the voltage gain drops as the frequency decreases.
2. The corner frequency ω_1 equals the inverse of the product $R_{eq}C_c$ where R_{eq} is the resistance “seen” looking from the capacitor terminals with $V_{in} = \text{zero}$ in the ac equivalent circuit.
3. At mid frequencies the voltage gain is the expected gain.

$$A_{v\text{mid}} = \frac{-g_m R_y R_x}{(R_s + R_x)} = \frac{-\beta R_y R_x}{r_\pi (R_s + R_x)}$$
4. Summary 1, 2, and 3 above are true but the results are slightly different if the emitter bypass capacitor acts like an open near where C_c begins to open. (start with new ac equivalent circuit)

EFFECT OF C_e ON FREQUENCY RESPONSE

The ac equivalent circuit of the CE amplifier on page 14 above is shown. Here we assume C_c is a short (note: it is possible that C_c acts like an open rather than a short)

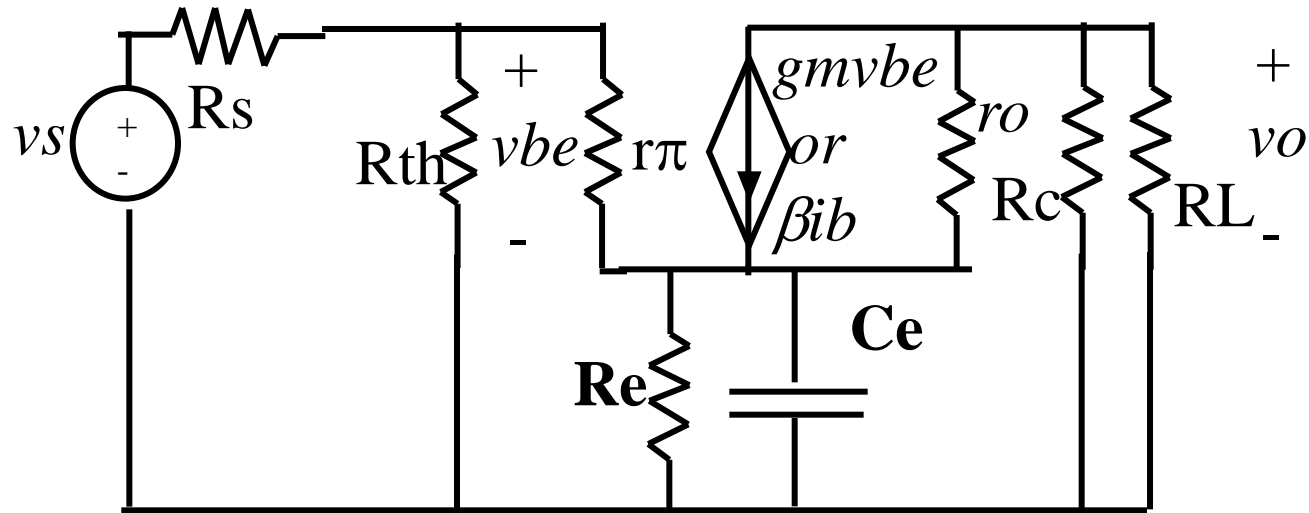Let $R_s = 0$ and $R_L = r_o = \text{infinity}$ to simplify the algebra



EFFECT OF C_e ON FREQUENCY RESPONSE

The gain function:

$$v_o = -\beta i_b R_c$$

$$v_s = i_b r_\pi + (\beta+1) i_b R_e // (1/sC_e)$$

$$v_o/v_s = -\beta R_c \frac{1}{r_\pi + (\beta+1) R_e // (1/sC_e)}$$

Manipulate the gain function:

$$v_o/v_s = -\beta R_c \frac{1}{r_\pi + \frac{(\beta+1) R_e / sC_e}{R_e + 1/sC_e}} = -\beta R_c \frac{1}{r_\pi + \frac{(\beta+1) R_e}{sC_e R_e + 1}}$$

EFFECT OF C_e ON FREQUENCY RESPONSE

$$v_o/v_s \equiv -\beta R_c \frac{sC_e R_e + 1}{(sC_e R_e + 1) r_\pi + (\beta + 1) R_e}$$

$$= -\beta R_c \frac{sC_e R_e + 1}{sC_e R_e r_\pi + r_\pi + (\beta + 1) R_e} = \frac{-\beta R_c}{r_\pi + (\beta + 1) R_e} \frac{sC_e R_e + 1}{\frac{sC_e R_e r_\pi}{r_\pi + (\beta + 1) R_e} + 1}$$

$$v_o/v_s = \underbrace{\frac{-\beta R_c}{r_\pi + (\beta + 1) R_e}}_{k=A_{vlow}} \frac{(j\omega/\omega_e + 1)}{(j\omega/\omega_{e1} + 1)}$$



Where: $\omega_e = 1/C_e R_e$

$\omega_{e1} = 1/(C_e R_e // (r_\pi / (\beta + 1)))$

Note: ω_{e1} is always $> \omega_e$

Note: $A_{vmid} = A_{vlow} \omega_{e1}/\omega_e$

EFFECT OF C_e ON FREQUENCY RESPONSE

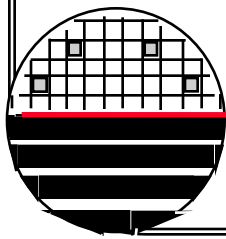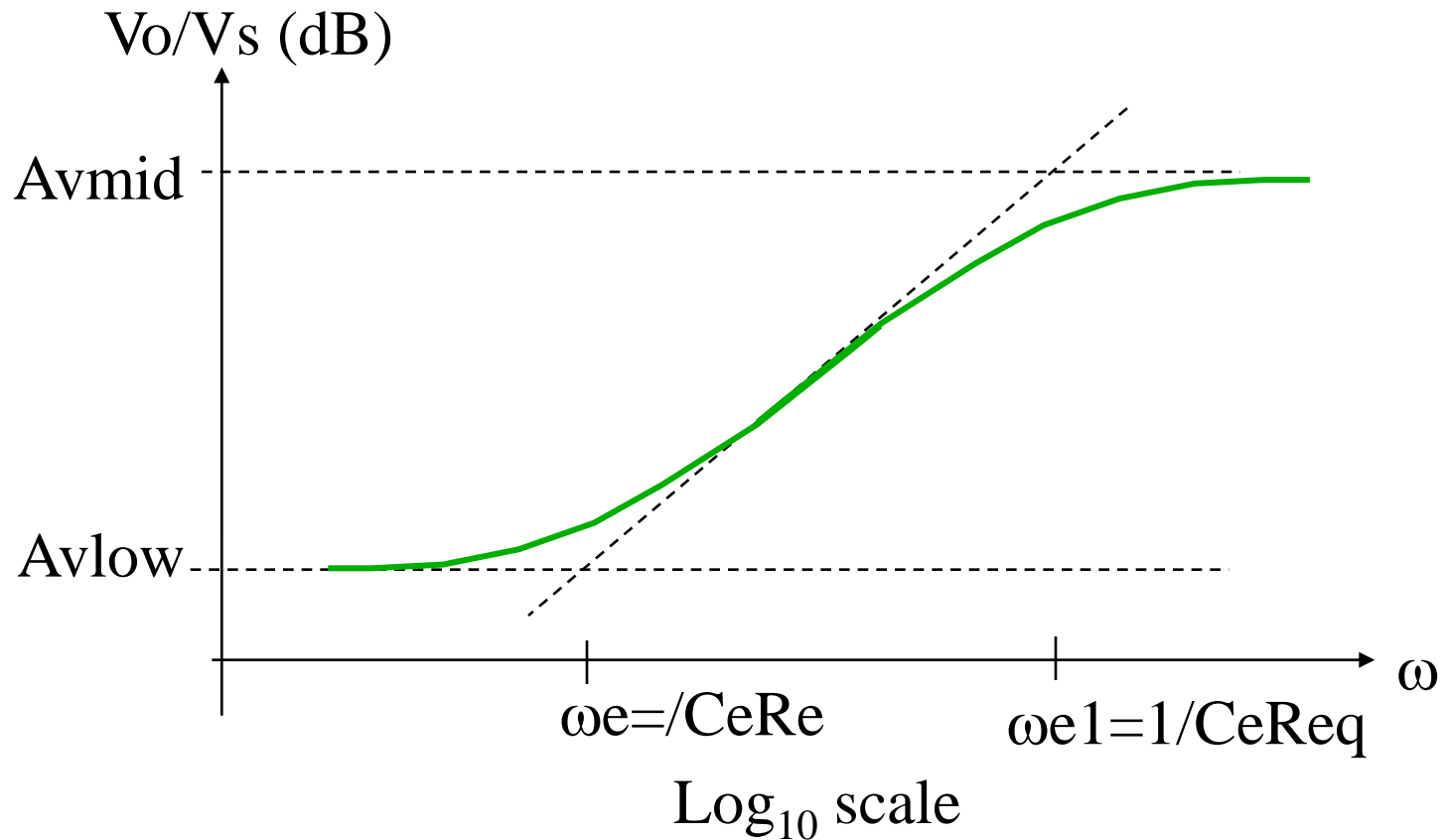

SUMMARY FOR EFFECT OF C_e

1. At low frequencies the bypass capacitor, C_e , opens up and the voltage gain becomes that of an unbypassed CE amplifier, A_{vlow}
2. At high frequencies the gain is A_{vmid}
3. Because of 1 and 2 we see that there are two corner frequencies. They are:

$$\omega_e = 1/R_e C_e$$

and


$$\omega_{e1} = 1/R_{eq} C_e$$

where R_{eq} is the resistance seen from the terminals of C_e

$$R_{eq} = R_e // r_{\pi} / (\beta + 1) \quad \text{if } R_s = 0 \text{ and } C_c \text{ "short"}$$


$$R_{eq} = R_e // (r_{\pi} + R_1 // R_2 // R_s) / (\beta + 1) \quad \text{if } R_s \text{ not } 0 \text{ and } C_c \text{ "short"}$$
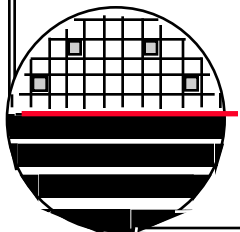
$$R_{eq} = R_e // (r_{\pi} + R_1 // R_2) / (\beta + 1) \quad \text{if } C_c \text{ "open"}$$



COMPLETE CE AMPLIFIER LOW FREQUENCY RESPONSE

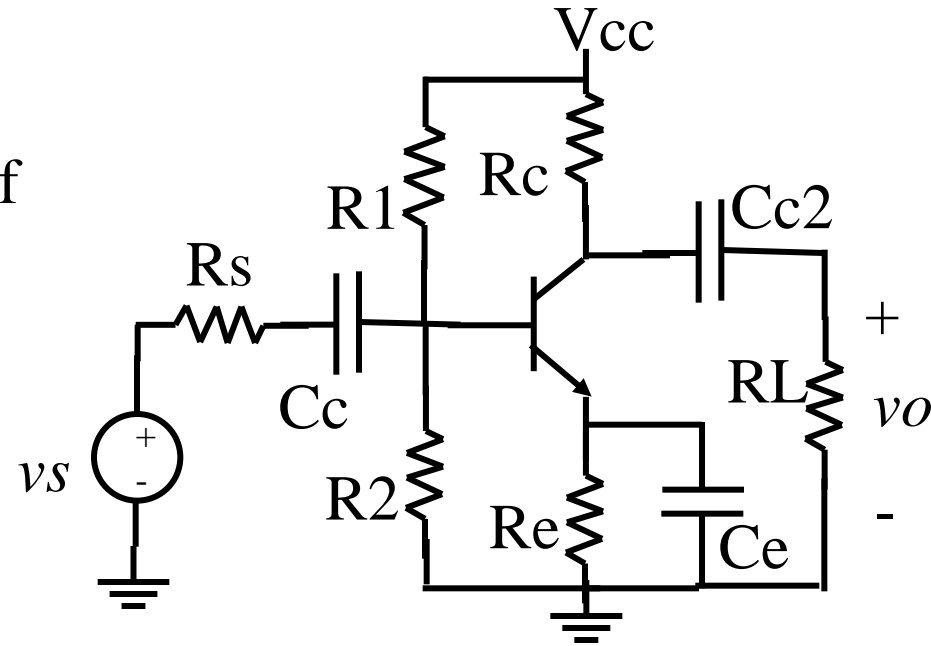$R_s = 2K$ $\beta = 100$
 $R_1 = 40K$ $V_{cc} = 20$
 $R_2 = 10K$ $C_c = C_e = C_{c2} = 10\mu f$
 $R_C = 4K$
 $R_e = 1K$
 $R_L = 2K$




Find k , ω_1 , ω_2 , ω_3 , ω_4

$$v_o/v_s = \frac{K (j\omega/\omega_1) (j\omega/\omega_2) (j\omega/\omega_3+1)}{(j\omega/\omega_1+1) (j\omega/\omega_2+1) (j\omega/\omega_4+1)}$$

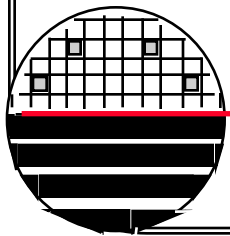EXAMPLE: SOLUTION

DC analysis:

A_{vmid} = Voltage gain including R_S and R_L assume all C's shorts



EXAMPLE: SOLUTION

$$\omega_1 = 1/R_{eq} C_{c1}$$

assume C_e is open unless C_e is 10X C_{c1}


$$\omega_2 = 1/R_{eq} C_{c2}$$

$$\omega_3 = 1/R_e C_e$$

$$\omega_4 = 1/R_{eq} C_e$$


$$K = A_{vlow} =$$

HIGH FREQUENCY BJT TRANSISTOR MODEL

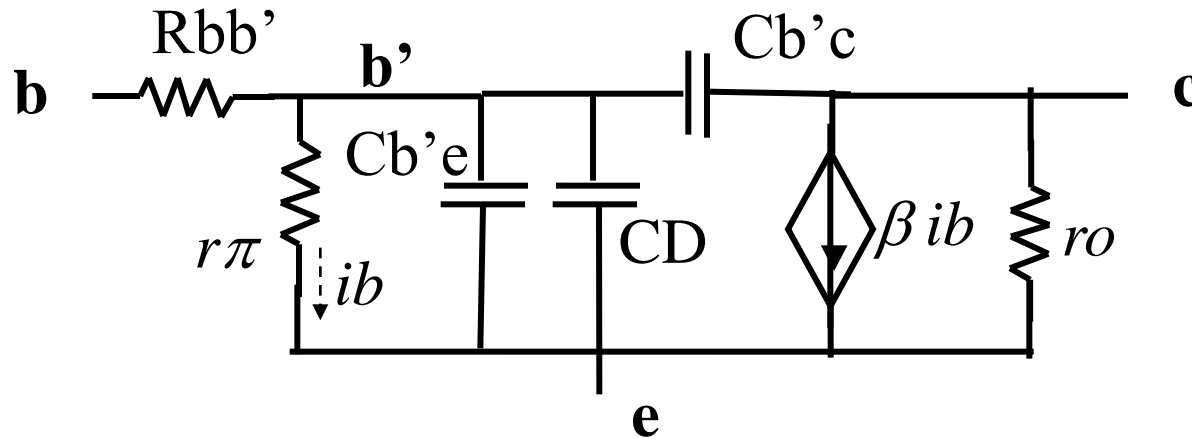

$R_{bb'}$ is the series base resistance

r_{π} is the base emitter small signal junction resistance

$C_{b'e}$ is the base emitter junction capacitance

$C_{b'c}$ is the base collector junction capacitance

CD is the diffusion capacitance, represents the change in charge stored in the base caused by a change in base emitter voltage


r_o is the small signal output resistance = V_A/IC

β is the short circuit common emitter current gain


MILLERS THEOREM

To predict the high frequency response of a common emitter amplifier we want to do some quick calculations. We would like to simplify the model given on the previous page. We can do this with the aid of Miller's theorem. The resulting model is approximate and might not give good results above the upper corner frequency where the voltage gain begins to fall off.

Millers Theorem: Consider a linear network with N nodes. An impedance, Z , between any two nodes, N_1 and N_2 , can be removed and another impedance Z_1 placed from N_1 to reference and impedance Z_2 placed from N_2 to reference. If $Z_1 = Z/(1-K)$ and $Z_2 = ZK/(K-1)$ where $K=V_2/V_1$, then the nodal equations will not be changed and the resulting circuit will yield equivalent node voltages, V_1 , V_2 , etc.


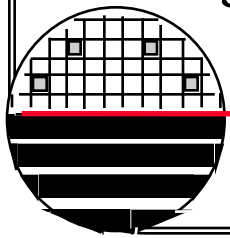


MILLERS THEOREM

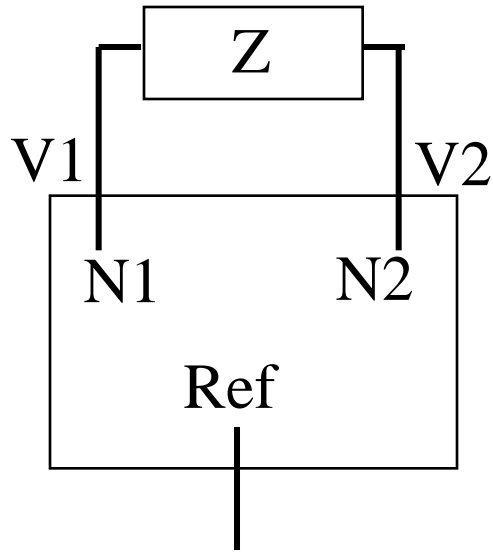

$$Z_1 = Z / (1 - K)$$


$$Z_2 = Z (K / (K - 1))$$

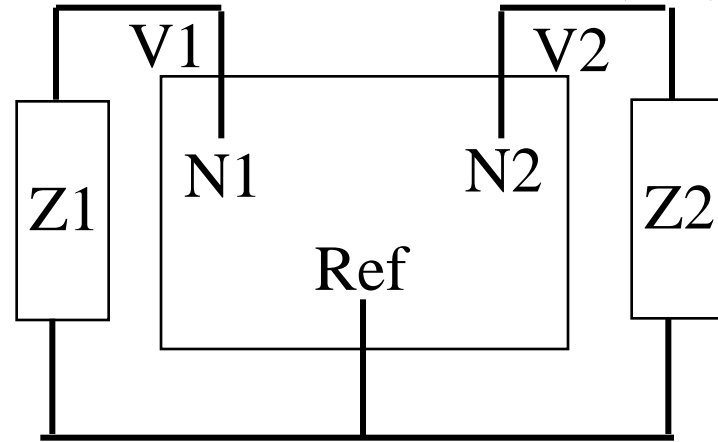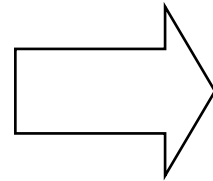


where $K = V_2 / V_1$

at N1 term $(V_1 - V_2) / Z$
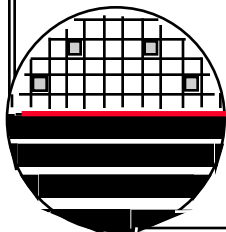
$$\begin{aligned} \text{at N1 term } V_1 / Z_1 &= V_1 / (Z / (1 - K)) \\ &= V_1 / (Z / (1 - V_2 / V_1)) \\ &= (V_1 - V_2) / Z \end{aligned}$$



HIGH FREQUENCY MODEL OF CE AMPLIFIER

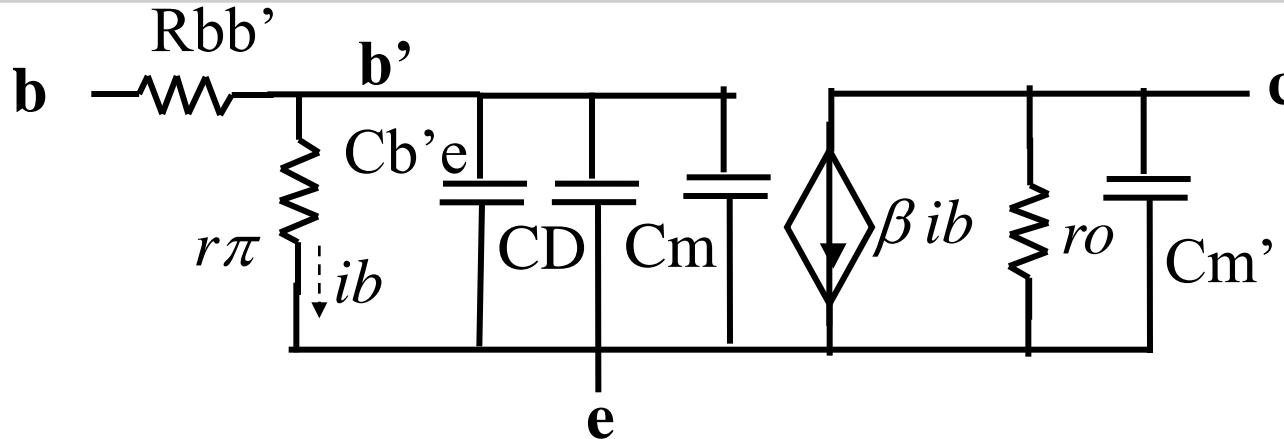

From: $Z1 = Z/(1-K)$ we have $1/sCm = \frac{1/sCb'c}{1-V2/V1}$

$V2 = -\beta ib ro$ and $V1 = ib r\pi$

Therefore: $Cm = Cb'c (1 - \beta ro/r\pi)$



Voltage gain

From: $Z2 = Z (K/(K-1))$

and : $Cm' = \sim Cb'c$

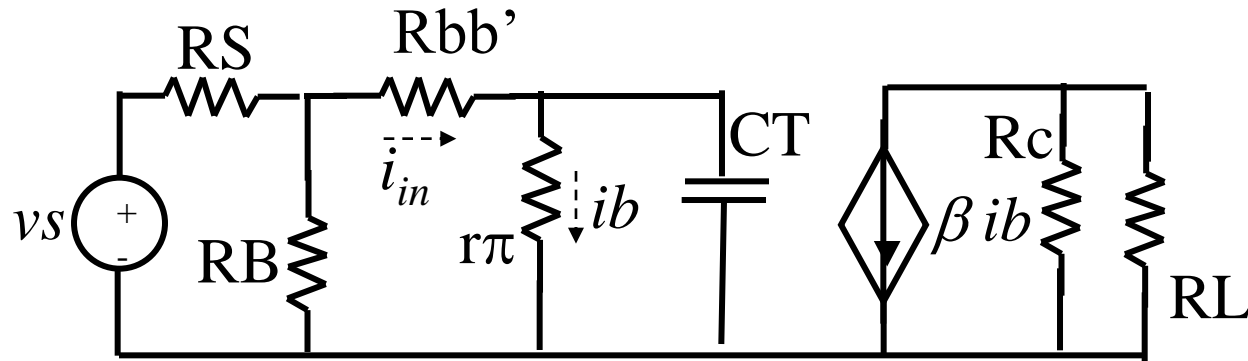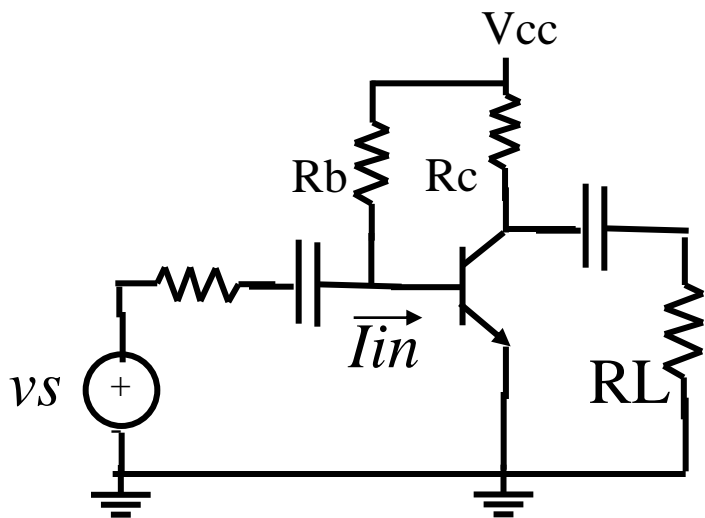EXAMPLE: HIGH FREQUENCY CE AMPLIFIER

$\beta = 100$
 $r\pi = 1K, R_{b'b} = 0$
 $C_{b'c} = 20\text{pf}$
 $C_{b'e} + C_D = 20\text{pf} + 1000\text{pf}$



Let $C_T = C_{b'e} + C_D + C_m$

and $C_m = C_{b'c}(1 - \beta R_L/r\pi)$

To find the gain function:

$$v_o = -\beta i_b R_c // R_L$$

$$i_b = V_{b'e} / r\pi$$

$$V_{b'e} = \frac{v_S (R_B // r\pi // (1/sC_T))}{R_S + (R_B // r\pi // (1/sC_T))}$$

Next
pg

EXAMPLE: HIGH FREQUENCY CE AMPLIFIER

The gain function:

$$v_o/v_s = \frac{-\beta R_c // R_L (R_B // r_\pi // (1/sC_T))}{r_\pi R_S + (R_B // r_\pi // (1/sC_T))}$$


Manipulate the gain function: Let $R_B // r_\pi = R$

$$v_o/v_s = \frac{-\beta R_c // R_L}{r_\pi} \frac{\frac{R(1/sC_T)}{R + (1/sC_T)}}{R_S + \frac{R(1/sC_T)}{R + (1/sC_T)}}$$

$$v_o/v_s = \frac{-\beta R_L}{r_\pi} \frac{\frac{R}{sC_T R + 1}}{R_S + \frac{R}{sC_T R + 1}}$$

$$v_o/v_s = \frac{-\beta R_L}{r_\pi} \frac{R}{(sC_T R + 1)R_S + R}$$

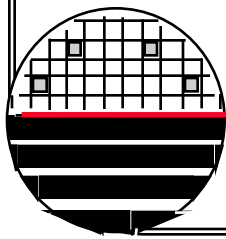
$$v_o/v_s = \frac{-\beta R_c // R_L}{r_\pi} \frac{R}{(R_S + R)} \frac{1}{\left[\frac{sC_T R R_S}{(R_S + R)} + 1 \right]}$$



EXAMPLE: HIGH FREQUENCY CE AMPLIFIER

$$v_o/v_s = \underbrace{\frac{-\beta R_{c//RL}}{r_{\pi}} \frac{R}{(R_S + R)}}_{A_{vmid}} \left[\frac{1}{j\omega \frac{C_T R R_S}{(R_S + R)} + 1} \right]$$

$$\omega_h = 1 / C_T (R // R_S)$$

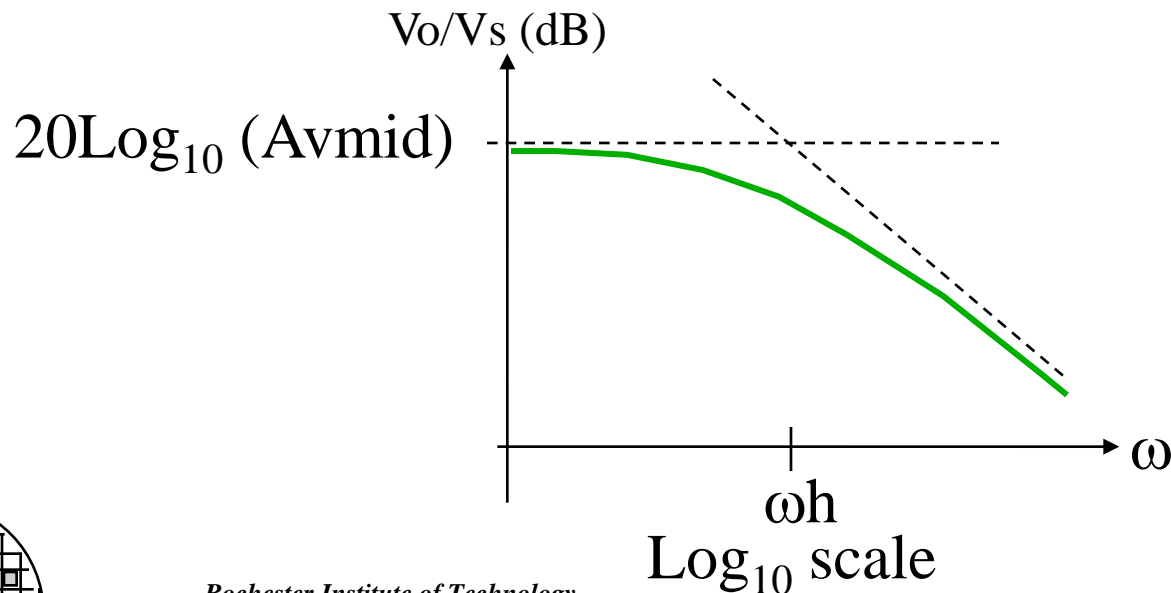

SUMMARY: HIGH FREQUENCY RESPONSE OF CE AMP

1. At high frequencies the internal capacitances in the transistor causes the voltage gain to decrease

2. At mid frequencies the gain is $A_{vmid} = -\beta \frac{R_c // R_L}{r_\pi} \frac{R}{(R_S + R)}$

3. The corner frequency is $\omega_h = 1 / (R_{eq} C_T)$

where $C_T = C_{b'e} + C_D + C_m$

and R_{eq} = the equivalent resistance as “seen” from the terminals of the capacitor C_T . ($v_s = \text{zero}$)



4. There is a second corner due to the miller capacitance C_m' . Since ω_h occurs first we are not normally interested in the corner due to C_m'

HOW DOES MANUFACTURER SPECIFY C_D , C_{be} , C_{bc}

$C_{b'c}$ is usually given by the manufacturer as the common base output capacitance which it is.

$C_{b'e}$ and C_D are given indirectly by the manufacturers specification of the transition frequency f_T

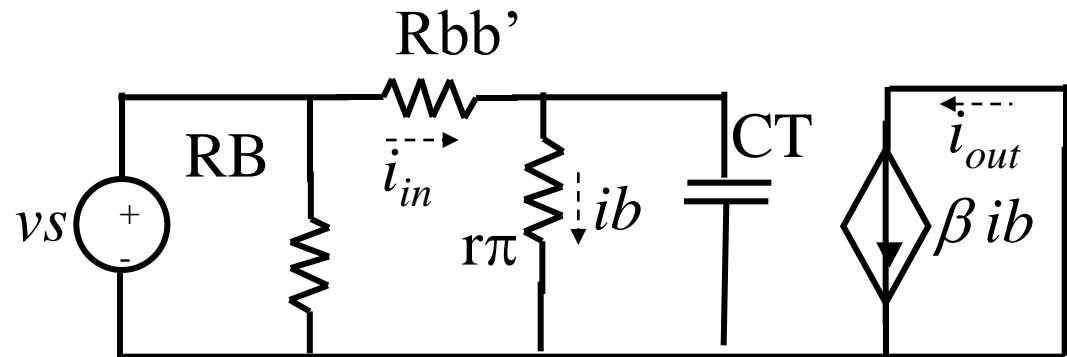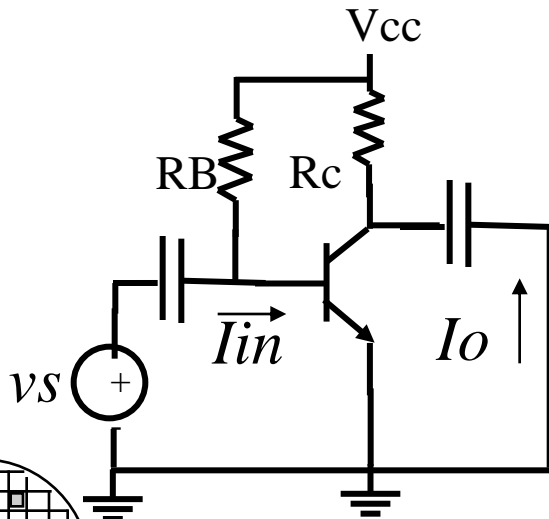f_T is the frequency at which the CE short circuit current gain goes to 1




Frequency Response


2N3904



2N3904

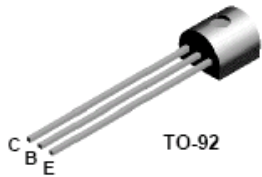

MMBT3904

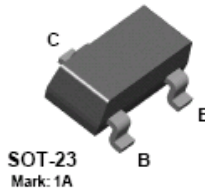

SMALL SIGNAL CHARACTERISTICS

f_T	Current Gain - Bandwidth Product	$I_C = 10 \text{ mA}, V_{CE} = 20 \text{ V}, f = 100 \text{ MHz}$	300	MHz
C_{obo}	Output Capacitance	$V_{CB} = 5.0 \text{ V}, I_E = 0, f = 1.0 \text{ MHz}$	4.0	pF
C_{ibo}	Input Capacitance	$V_{EB} = 0.5 \text{ V}, I_C = 0, f = 1.0 \text{ MHz}$	8.0	pF
NF	Noise Figure	$I_C = 100 \mu\text{A}, V_{CE} = 5.0 \text{ V}, R_S = 1.0 \text{ k}\Omega, f = 10 \text{ Hz to } 15.7 \text{ kHz}$	5.0	dB

NPN General Purpose Amplifier

This device is designed as a general purpose amplifier and switch. The useful dynamic range extends to 100 mA as a switch and to 100 MHz as an amplifier.

Absolute Maximum Ratings* $T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CE0}	Collector-Emmitter Voltage	40	V
V_{CB0}	Collector-Base Voltage	60	V
V_{EB0}	Emitter-Base Voltage	6.0	V
I_C	Collector Current - Continuous	200	mA
T_J, T_{stg}	Operating and Storage Junction Temperature Range	-55 to +150	$^\circ\text{C}$

*These ratings are limiting values above which the semiconductor device may be damaged.

Spice Model

NPN (Is=6.734f Xti=3 Eg=1.11 Vaf=74.03 Bf=416.4 Ne=1.259 Ise=6.734 Ikf=66.78m Xtb=1.5 Br=.7371 Nc=2 Isc=0 Ikr=0 Rc=1 Cjc=3.098p Mjc=.3085 Vjc=.75 Fc=.5 Cje=4.493p Mje=.2593 Vje=.75 Tr=239.5n Tf=301.2p Itf=.4 Vtf=4 Xtf=2 Rb=10)

Rb = 10 ohms

ANALYSIS OF SHORT CIRCUIT CURRENT GAIN TO EXTRACT $Cb'e + CD$


$$i_{out} = \beta i_b$$

$$i_b = i_{in} \frac{1/sCT}{r\pi + 1/sCT}$$

$$i_{out}/i_{in} = \frac{\beta}{sCT r\pi + 1}$$

$$i_{out}/i_{in} = \frac{\beta}{j\omega CT r\pi + 1}$$
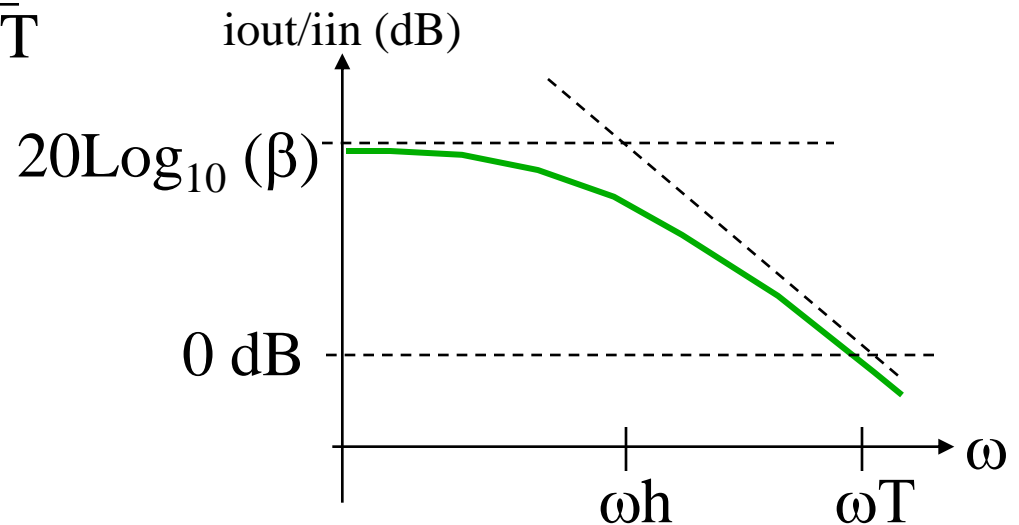
$$i_{out}/i_{in} = \frac{\beta}{j\omega/\omega_b + 1}$$



$$\omega_b = 1/(CT r\pi)$$

$$\omega_T = 2\pi f_T = \text{transition freq in radians/s}$$

ANALYSIS OF SHORT CIRCUIT CURRENT GAIN TO EXTRACT $C_{b'e} + C_D$

$$\text{at } \omega_T, i_{out}/i_{in} = 1 = \sim \frac{\beta}{j\omega/\omega_b}$$

$$2\pi f_T = \frac{\beta}{C_T r_{\pi}}$$

$$\text{So } C_T = \frac{\beta}{2\pi f_T r_{\pi}} = C_{b'e} + C_D + C_m$$

and $C_m = C_{b'c}$ since $A_v = \text{zero}$

Finally


$$C_{b'e} + C_D = \frac{\beta}{2\pi f_T r_{\pi}} - C_{b'c}$$

EXAMPLE: DETERMINATION OF $C_{b'c}$, $C_{b'e} + C_D$


Given:

1. Common-Base Open Circuit Output Capacitance of 12 pf is measured at $f = 1$ Mhz, $V_{CB} = 10V$ and $I_E = \text{zero}$.
2. A transition frequency of 100 Mhz is measured using the following test conditions, $V_{CE} = 2V$, $I_C = 50mA$, β response with frequency is extrapolated at -20 dB/Dec to f_T at which $\beta = 1$ from $f = 20Mhz$ where $\beta = 100$

Find $C_{b'c}$, $C_{b'e} + C_D$

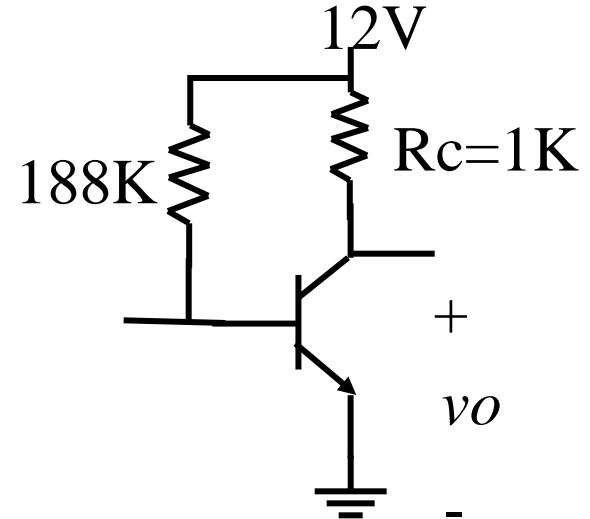



SOLUTION TO EXAMPLE ON PREVIOUS PAGE

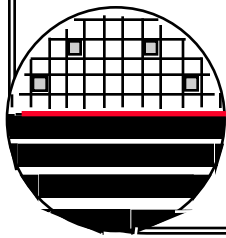


ANOTHER EXAMPLE

$V_{CC} = 15$ $\beta = 100$
 $R_s = 100$ $V_A = \text{infinity}$
 $R_1 = 150K$ $R_{b'b} = 100$
 $R_C = 500$ $C_{b'c} = 20\text{pf at } V_{cb} = 5$
 $f_T = 100 \text{ Mhz}$

Find r_π , C_m , C_T and ω_h

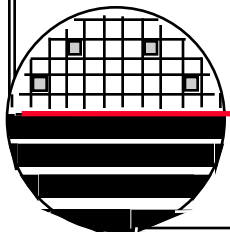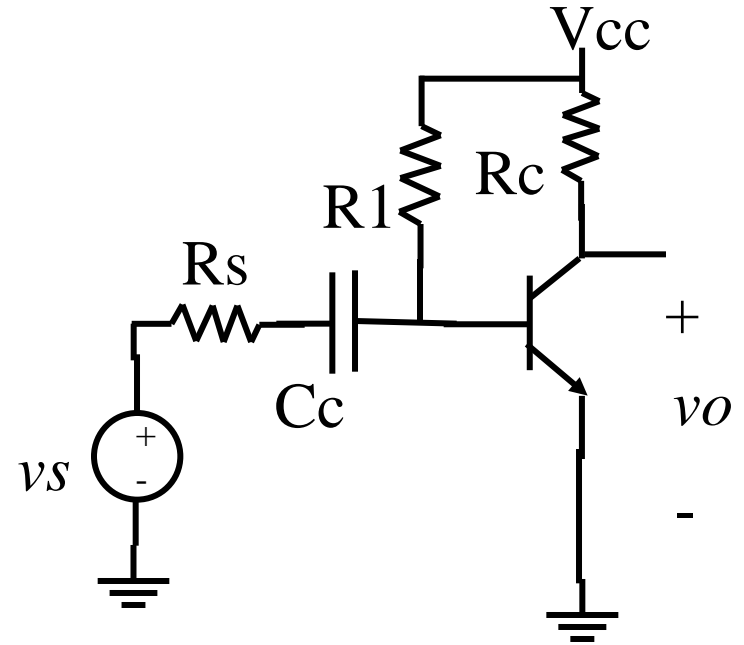

EXAMPLE FROM OLD EXAM

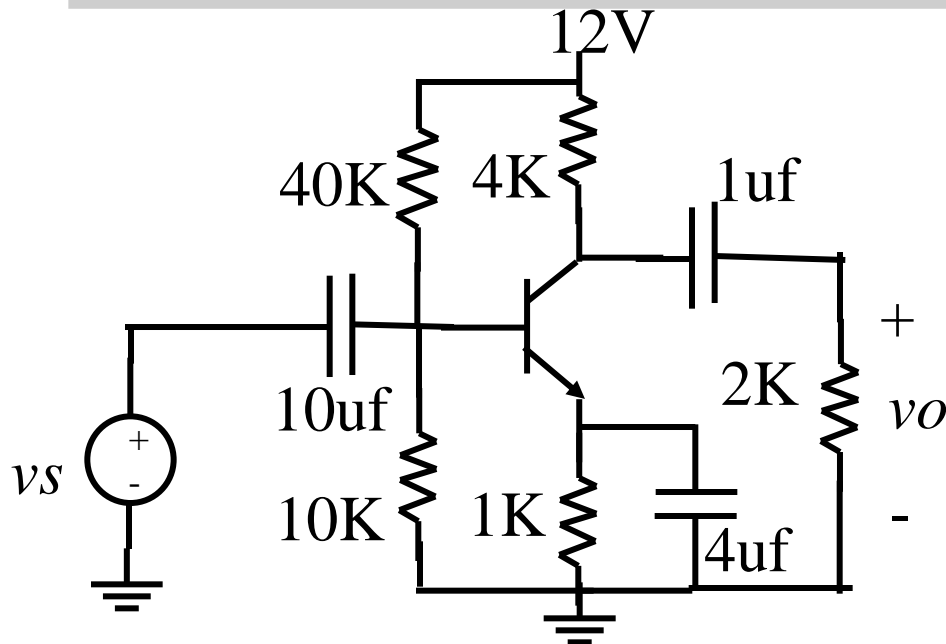


Assume $\beta = 150$
 $V_A = 100$
 $C_{b'c} = 10 \text{ pF @ } 10 \text{ V}$
 $f_T = 200 \text{ MHz}$
 $R_{b'b} = 100 \text{ ohms}$

Find k , ω_1 , ω_2 , ω_3 , ω_4 , **each 5 pts** and ω_h **10 pts**

$$v_o/v_s = \frac{k (j\omega/\omega_1) (j\omega/\omega_2) (j\omega/\omega_3+1)}{(j\omega/\omega_1+1) (j\omega/\omega_2+1) (j\omega/\omega_4+1) (j\omega/\omega_h+1)}$$

REFERENCES

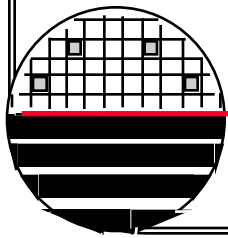1. Sedra and Smith, chapter 5.
2. Device Electronics for Integrated Circuits, 2nd Edition, Kamins and Muller, John Wiley and Sons, 1986.
3. The Bipolar Junction Transistor, 2nd Edition, Gerald Neudeck, Addison-Wesley, 1989.
4. Data sheets for 2N3904



HOMWORK – FREQUENCY RESPONSE OF CE AMP

1. For the circuit on page 22 find A_{vmid} , k , ω_1 , ω_2 , ω_3 , ω_4 given:

$$R_s = 1K$$

$$\beta = 150$$

$$R_1 = 50K$$

$$V_{cc} = 24$$

$$R_2 = 10K$$

$$C_c = 1\mu f$$

$$R_C = 5K$$

$$C_e = 2\mu f$$

$$R_e = 1K$$

$$C_{c2} = 10\mu f$$

$$R_L = 5K$$

2. Create a spread sheet to analyze CE circuits like that in problem 1 to find A_{vlow} , A_{vmid} , k , low frequency corners.

Extra points if you also do high frequency analysis?


3. If $C_{b'c}$ is measured at $V_{cb} = 5$ what is it at $V_{cb} = 10$?

4. Find $C_{b'e} + C_D$ for $f_T = 200$ Mhz and $I_C = 5mA$, $\beta = 150$ and $C_{b'c} = 10pf$

5. Create a spread sheet to calculate and graph the magnitude part of the Bode Plot given k , ω_1 , ω_2 , ω_3 , ω_4 and ω_h

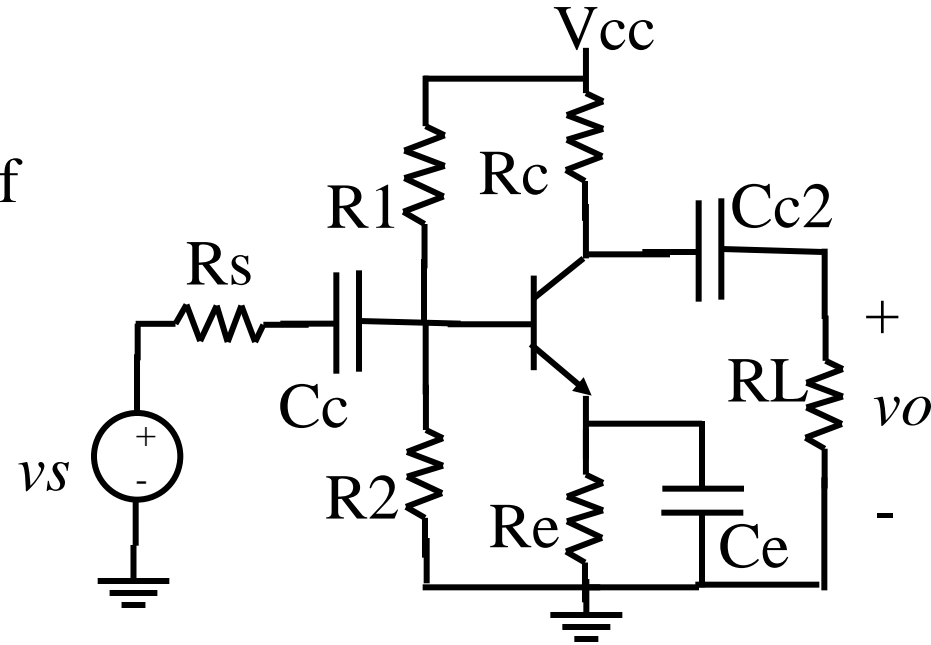EXAMPLE PROBLEM FROM PAGE 22

$R_s = 2K$ $\beta = 100$
 $R_1 = 40K$ $V_{cc} = 20$
 $R_2 = 10K$ $C_c = C_e = C_{c2} = 10\mu f$
 $R_C = 4K$
 $R_e = 1K$
 $R_L = 2K$



Find k , ω_1 , ω_2 , ω_3 , ω_4

$$v_o/v_s = \frac{K (j\omega/\omega_1) (j\omega/\omega_2) (j\omega/\omega_3+1)}{(j\omega/\omega_1+1) (j\omega/\omega_2+1) (j\omega/\omega_4+1)}$$

EXAMPLE pg 22: SOLUTION

DC analysis: $R_{th} = R1//R2 = (10)(40)/(10+40) = 8K$
 $V_{th} = V_{cc} R2/(R1+R2) = 20 (10)/(10+40) = 4V$

KVL: $I_B R_{th} + 0.7 + (B+1)I_B R_e - V_{th} = 0$

$$I_B = 4 - 0.7 / (R_{th} + 101K) = 30.3\mu A$$

$$I_C = B I_B = 100 (30.3\mu A) = 3.03 \text{ mA}$$

$$g_m = I_C/V_T = 3.03/0.026 = 117 \text{ mS}$$

$$r_\pi = V_t/I_B = 0.026/30.3\mu A = 858 \text{ ohms}$$

$$r_o = V_A/I_C = \text{assume large}$$

A_{vmid} = Voltage gain including R_S and R_L assume all C's shorts

$$V_o = g_m R_c // R_L V_{in}$$

$$V_{in} = V_s R_{in} / (R_{in} + R_s)$$

$$V_o/V_s = V_o/V_{in} \times V_{in}/V_s = -(g_m R_c // R_L) \{ R_{in} / (R_{in} + R_s) \}$$

$$V_o/V_s = -117m (4K // 2K) (R_{th} // r_\pi) / ((R_{th} // r_\pi) + 2K)$$

$$= -43.6$$

EXAMPLE pg 22: SOLUTION(continued)

$\omega_1 = 1/R_{eq} C_{c1}$ assume C_e is open unless it is 10X C_{c1}

$$R_{eq} = R_s + R_{th} // (r_{\pi} + (B+1)R_e) = 2K + 8K // (0.858K + 101K) \\ = 9.42K$$

$$\omega_1 = 1 / (9.42K \cdot 10 \mu F) = 10.6 \text{ r/s} \quad \text{or} \quad 1.69 \text{ Hz}$$

$\omega_2 = 1/R_{eq} C_{c2}$

$$R_{eq} = R_L + R_c = 6K$$

$$\omega_2 = 1 / (6K \cdot 10 \mu F) = 16.7 \text{ r/s} \quad \text{or} \quad 2.65 \text{ Hz}$$

$\omega_3 = 1/R_e C_e = 1 / (1K \cdot 10 \mu F) = 100 \text{ r/s} \quad \text{or} \quad 15.9 \text{ Hz}$

$\omega_4 = 1/R_{eq} C_e$

$$R_{eq} = R_e // ((r_{\pi} + R_{th} // R_s) / (B+1)) = 1K // ((0.858K + 8K // 2K) / 101) \\ = 24.3 \text{ ohms}$$

$$\omega_4 = 1 / (24.3 \cdot 10 \mu F) = 4214 \text{ r/s} \quad \text{or} \quad 671 \text{ Hz}$$

$K = A_{vlow} = A_{vmid} \omega_3 / \omega_4 = -42 (100 / 4214) = -0.99$


SPREAD SHEET SOLUTION

1	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q		
1	ROCHESTER INSTITUTE OF TECHNOLOGY								CE-BJT-Analysis-DC-AC-Freq.XLS										
2	ELECTRICAL AND MICROELECTRONIC ENGINEERING								4/27/2011				freq (hz)	20Log10(Av)	Av (mag)	Av (mag)			
3													10	-0.214836654	-1.238078701	-0.341425321	1.364667403	-3.491E-08	
4	CALCULATIONS FOR CE BJT AMPLIFIER DESIGN								DR. LYNN FULLER				316.3	6.678151604	-0.140883526	-0.035359918	6.854395397	-3.492E-07	
5													100	15.87649119	-0.01430232	-0.003550596	15.89434759	-3.491E-06	
6	To use this spreadsheet change the values in the white boxes. The rest of the sheet is												316.3	25.02073855	-0.001431699	-0.000355028	25.0225602	-3.492E-05	
7	protected and should not be changed unless you are sure of the consequences. The												1000	30.80170688	-0.000143257	-3.55203E-05	30.80223473	-0.0003491	
8	calculated results are shown in the purple boxes.												3163	32.22099164	-1.43193E-05	-3.55042E-06	32.22450059	-0.0034911	
9													10000	32.36130294	-1.43259E-06	-3.55205E-07	32.39607402	-0.0347693	
10	This spread sheet calculates dc and ac parameters												31630	32.0777048	-1.43194E-07	-3.55043E-08	32.4136204	-0.3359154	
11	given all the resistor values, dc voltage supply												100000	29.85347957	-1.43259E-08	-3.55205E-09	32.41537796	-2.5618984	
12	values, and transistor parameter values.												316300	22.85303706	-1.43194E-09	-3.55042E-10	32.41555386	-9.5625168	
13	This spread sheet can be used once an amplifier												1000000	13.31036233	-1.4326E-10	-3.552E-11	32.41557144	-19.105209	
14	design is done to study how the amplifier performs												3163000	3.356679533	-1.43193E-11	-3.55065E-12	32.41557319	-29.058894	
15	if transistor or circuit parameters values are												10000000	-6.636479564	-1.43203E-12	-3.54873E-13	32.41557337	-39.052053	
16	changed.												31630000	-16.63797713	-1.4272E-13	-3.47158E-14	32.41557339	-49.053551	
17													100000000	-26.63594468	-1.44649E-14	-3.85731E-15	32.41557339	-59.051518	
18													316300000	-36.63792366	-9.64327E-16	0	32.41557339	-69.053497	
19													1000000000	-46.63593933	0	0	32.41557339	-79.051513	
20																			
21																			
22	CONSTANTS				VARIABLES														
23	K	1.38E-23	J/K	Temp=	300	K	Cc1=	10	µF										
24	q	1.60E-19	Coul	VCC=	20.00	Volts	Cc2=	10	µF										
25	εo	8.85E-14	F/cm	Re1	0	ohms	Ce	10	µF										
26	εr	11.7		Re2	1000	ohms													
27					Rs	2	Kohms												
28					R1	40	Kohms												
29					R2	10	Kohms												
30					Rc	4	Kohms												
31					RL	2	Kohms												
32	Transistor Specifications:																		
33	Early Voltage Va =	100	Volts	at	10	volts													
34	Beta = β =	100																	
35	Cb'c =	10	pF																
36	fT =	100	Mhz																
37	Rb'b =	100	ohm																
38																			

SPREAD SHEET SOLUTION

39	CALCULATIONS:	
40	$g_m = \frac{I_C}{V_T}$	$V_T = KT/q = 0.0258874$ Volts
41		$V_{th} = 4.00$ Volts
42		$R_{th} = R1/R2 = 8.00$ Kohm
43	$r_{\pi} = \beta / g_m = V_T / I_B$	$I_B = 30.28$ uA
44		$I_C = 3.03$ mA
45	$r_o = V_A / I_C$	Specification for V_{pp} swing = $V_{cc} - 5 = 15.00$ Volts
46		VCE at Q point = 4.86 Volts
47		$g_m = 0.117$ mho
48	$A_v = -(R_c // R_L) / R_{e1}$	$r_{\pi} = 0.855$ Kohm
49	$A_v = [R_{in} / (R_{in} + R_s)] [\beta (R_c // R_L) / (r_{\pi} + (\beta + 1) R_{e1})]$	$r_o = 33.03$ Kohm
50		$R_{in} = (r_{\pi} + (\beta + 1) R_{e1}) // R1 // R2 = 0.773$ Kohm
51		$R_{out} = r_o // R_c = 3.568$ Kohm
52		$A_v = V_o / V_{in}$ (with no R_L) = -417.27 V/V
53		$A_v = V_o / V_{in}$ (include R_L) = -149.88 V/V
54		$V_{in} / V_s = 0.28$ V/V
55		$A_{vmid} = V_o / V_s$ (include R_L and R_s) = -41.76 V/V = 32 dB
56		V_o p-p = 7.79 Volts
57		$(r_{\pi} + R_s // R_{th}) / (\beta + 1) = 24.31$ ohm
58	$C_b'e + C_D = \frac{\beta}{2 \pi f T r_{\pi}} - C_b'c$	$C_b'c$ at VCEQ = 15.50 pF
59		$C_m = C_b'c (1 - V_o / V_{in}) = 2339$ pF
60		$C_b'e + C_D = 171$ pF
61	If C_e is assumed short	$\omega_1 = 1 / (R_{eq1} C_{c1}) = 36$ r/s or $f_1 = 6$ Hz
62	If C_e is assumed open	$\omega_1 = 1 / (R_{eq1} C_{c1}) = 10$ r/s or $f_1 = 2$ Hz
63		$\omega_2 = 1 / (R_{eq2} C_{c2}) = 18$ r/s or $f_2 = 3$ Hz
64		$\omega_e = 1 / (R_e C_e) = 100$ r/s or $f_e = 16$ Hz
65		$\omega_{e1} = 1 / (R_{eq} C_e) = 4214$ r/s or $f_{e1} = 671$ Hz
66		$\omega_h = 1 / (R_{eq} C_T) = 700461$ r/s or $f_h = 0.112$ Mhz
67		$k = A_{vmid} \omega_e / \omega_{e1} = -0.99$ V/V

LTSPICE SOLUTION

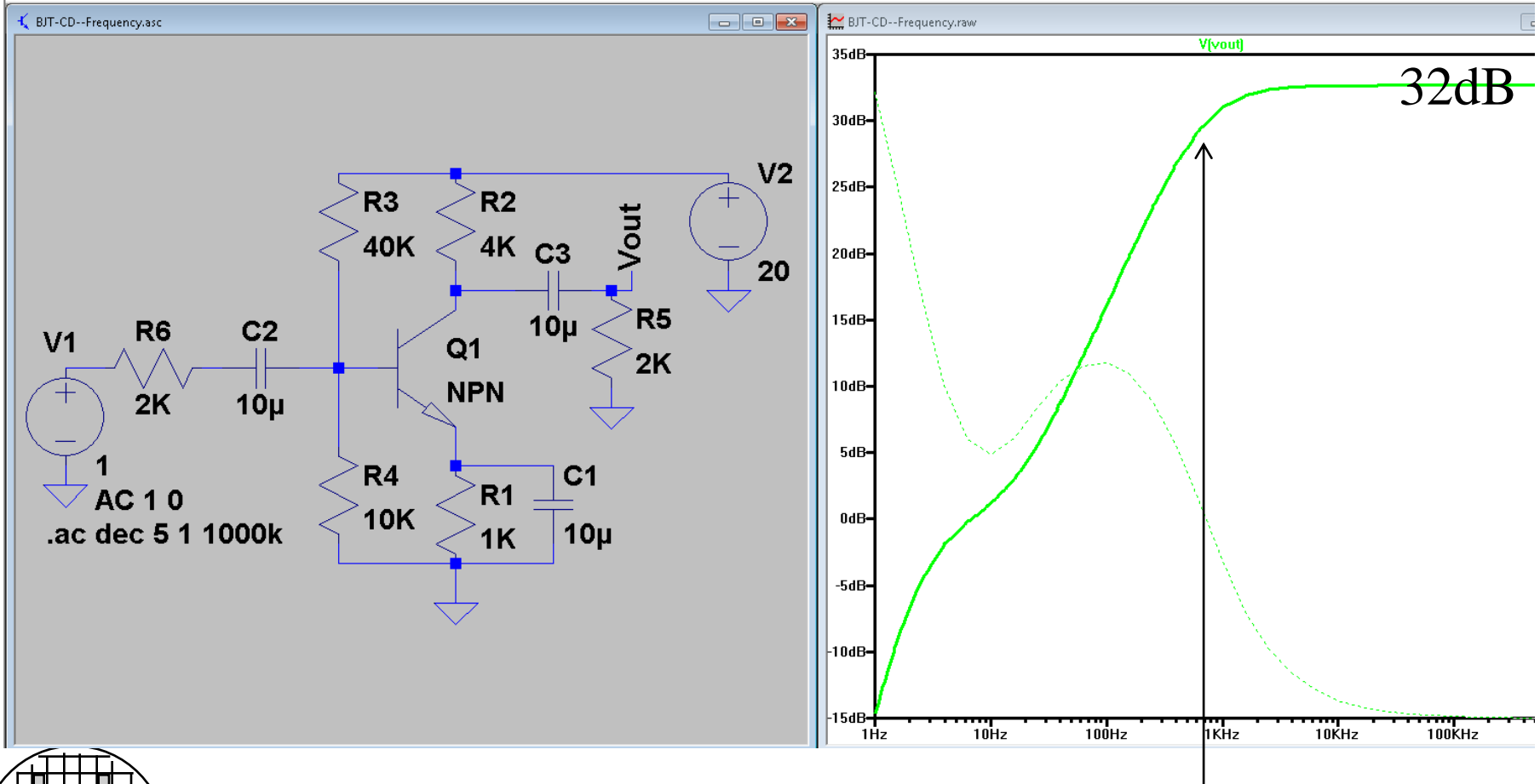

SOLUTION


Given:

1. Common-Base Open Circuit Output Capacitance of 12 pf is measured at $f = 1 \text{ Mhz}$, $V_{CB} = 10\text{V}$ and $I_E = \text{zero}$.
2. A transition frequency of 100 Mhz is measured using the following test conditions, $V_{CE} = 2\text{V}$, $I_C = 50\text{mA}$, β response with frequency is extrapolated at -20 dB/Dec to f_T at which $\beta = 1$ from $f = 20\text{Mhz}$ where $\beta = 100$

Find $C_{b'c}$, $C_{b'e} + C_D$

First do DC analysis to find I_C and V_{CB}
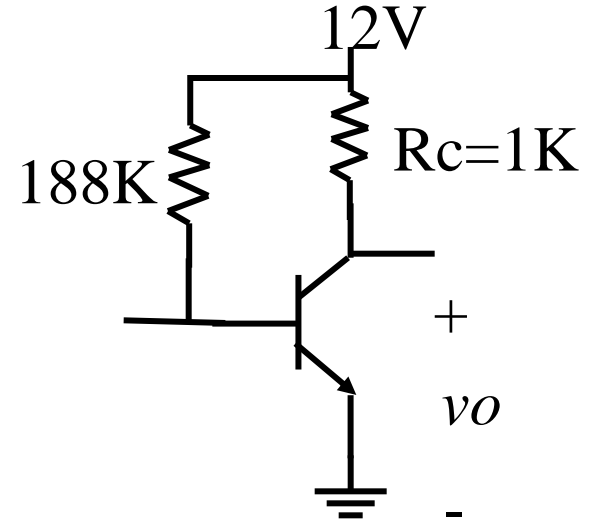
$$\begin{aligned} \text{KVL } I_B 188\text{K} + 0.7 &= 12 = 0 \\ I_B &= (12-0.7)/188\text{K} = 60\mu\text{A} \\ I_C &= \text{Beta } I_B = 100 \cdot 60\mu\text{A} = 6\text{mA} \\ V_{CB} &= 12 - R_c 6\text{mA} - 0.7 = 5.3 \text{ volts} \end{aligned}$$



SOLUTION TO EXAMPLE ON PREVIOUS PAGE


Find $r_{\pi} = 0.026/I_B = 0.026/0.060 \text{ mA} = 433 \text{ ohms}$

Find $C_{b'c}$ at the VCB of 5.3 volts = $12 \text{ pF} \sqrt{\frac{10 \text{ volts}}{5.3 \text{ volts}}} = 16.5 \text{ pF}$

$$C_{b'e} + C_D = \frac{\beta}{2 \pi f T r_{\pi}} - C_{b'c}$$

Beta = 100 and $f_T = 100 \text{ MEG}$

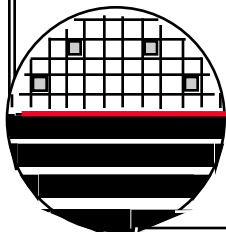$C_{b'e} + C_D = 368 \text{ pF} - 16.5 \text{ pF} = 352 \text{ pF}$




SOLUTION

$$\begin{aligned} V_{cc} &= 15 & \beta &= 100 \\ R_s &= 100 & V_A &= \text{infinity} \\ R_1 &= 150K & R_{b'b} &= 100 \\ R_C &= 500 & C_{b'c} &= 20\text{pf at } V_{cb} = 5 \\ & & f_T &= 100 \text{ Mhz} \end{aligned}$$

Find r_π , C_m , C_T and ω_h

First do DC analysis to find I_C and V_{CB}
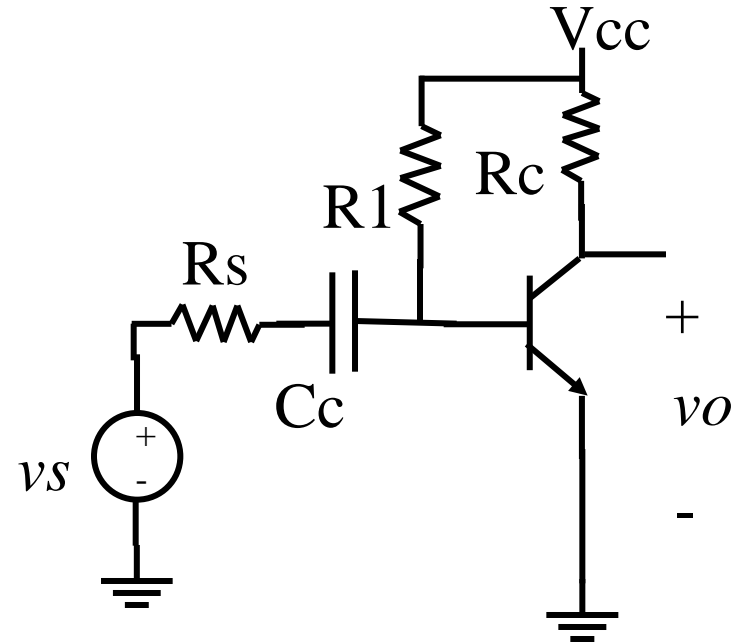
$$\begin{aligned} \text{KVL } I_B \ 150K + 0.7 &= 15 = 0 \\ I_B &= (15-0.7)/150K = 95.3\mu\text{A} \\ I_C &= \text{Beta } I_B = 100 \ 95.3\mu\text{A} = 9.53\text{mA} \\ V_{CB} &= 15 - R_C \ 9.53\text{mA} - 0.7 = 9.54 \text{ volts} \end{aligned}$$



SOLUTION TO EXAMPLE ON PREVIOUS PAGE

Find $r_{\pi} = 0.026/I_B = 0.026/0.0953 \text{ mA} = 273 \text{ ohms}$

Find $C_{b'c}$ at the VCB of 9.54 volts = $20 \text{ pF} \sqrt{\frac{5 \text{ volts}}{9.54 \text{ volts}}} = 14.5 \text{ pF}$

$$C_{b'e} + C_D = \frac{\beta}{2 \pi f T r_{\pi}} - C_{b'c}$$

Beta = 100 and $f_T = 100 \text{ MEG}$

$C_{b'e} + C_D = 583 \text{ pF} - 14.5 \text{ pF} = 569 \text{ pF}$

SOLUTION TO EXAMPLE ON PREVIOUS PAGE

Voltage gain $V_o / V_{b'e}$ at mid frequencies is used for miller capacitance Calculations.

$$V_o = -\beta i_b R_C // R_L // r_o = -100 i_b 500$$

$$i_b = V_{b'e} / r_\pi = V_{b'e} / 273$$

$$V_o / V_{b'e} = -183$$


$$C_m = C_{b'c} (1 - -183) = 14.5 \text{ pF} \times 184 = 2668 \text{ pF}$$

$$C_T = C_{b'e} + C_D + C_m = 569 \text{ pF} + 2668 \text{ pF} = 3237 \text{ pF}$$

$$\omega_h = 1 / R_{eq} C_T$$


$$R_{eq} = ((R_S // R_{th}) + R_{bb'}) // r_\pi = 199.9 // 273 = 115$$
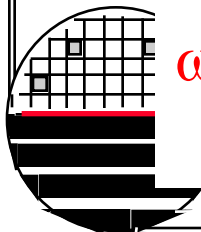
$$\omega_h = 1 / R_{eq} C_T = 1 / (115 \times 3237 \text{ pF}) = 2.69 \text{ M r/s} = 0.428 \text{ MHz}$$



COMPARE TO SPREAD SHEET

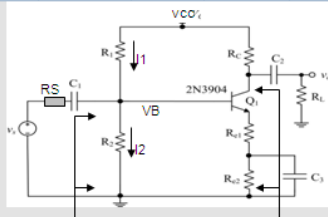9
10 This spread sheet calculates dc and ac parameters
11 given all the resistor values, dc voltage supply
12 values, and transistor parameter values.
13 This spread sheet can be used once an amplifier
14 design is done to study how the amplifier performs
15 if transistor or circuit parameters values are
16 changed.



Rin=Vin/lin Rout

CONSTANTS	VARIABLES
K	1.38E-23 J/K
q	1.60E-19 Coul
εo	8.85E-14 F/cm
εr	11.7
Temp	300 °K
VCC	15.00 Volts
Re1	0 ohms
Re2	0.001 ohms
Rs	0.1 Kohms
R1	150 Kohms
R2	999999 Kohms
Rc	0.5 Kohms
RL	999999 Kohms


Transistor Specifications:
 Early Voltage Va = #### Volts
 Beta = β = 100
 Cb'c = 20 pF
 fT = 100 Mhz
 Rbb = 100 ohm

at 5 volts

CALCULATIONS:

$g_m = \frac{I_C}{V_T}$	$V_T = K T / q = 0.025887375$ Volts
	$V_{th} = 15.00$ Volts
	$R_{th} = R_1 // R_2 = 149.98$ Kohm
$r_{\pi} = \beta / g_m = V_T / I_B$	$I_B = 95.33$ uA
	$I_C = 9.53$ mA
$r_o = V_A / I_C$	Specification for Vpp swing = Vcc - S = 10.00 Volts
	VCE at Q point = 10.23 Volts
	$g_m = 0.368$ mho
$A_v = -(R_c // R_L) / r_{\pi}$	$r_{\pi} = 0.272$ Kohm
$A_v = [R_{in} (R_{in} + R_s)] / \{ \beta (R_c // R_L) / (r_{\pi} + (\beta - 1) R_{e1}) \}$	$r_o = 1048959.35$ Kohm
	$R_{in} = (r_{\pi} + (\beta + 1) R_{e1}) // R_1 // R_2 = 0.271$ Kohm
	$R_{out} = r_o // R_c = 0.500$ Kohm
	$A_v = V_o / V_{in} \text{ (with no } R_L) = -184.13$ V/V
	$A_v = V_o / V_{in} \text{ (include } R_L) = -184.13$ V/V
	$V_{in} / V_s = 0.73$ V/V
	$A_{vmid} = V_o / V_s \text{ (include } R_L \text{ and } R_s) = -134.51$ V/V = 43 dB
	$V_o \text{ p-p} = 10.23$ Volts
	$(r_{\pi} + R_s // R_{th}) (\beta + 1) = 3.68$ ohm
$C_b'e + C_D = \frac{\beta}{2 \pi f T r_{\pi}} - C_b'c$	$C_b'c \text{ at VCEQ} = 14.48$ pF
	$C_m = C_b'c (1 - V_o / V_{in}) = 2681$ pF
	$C_b'e - C_D = 572$ pF
If Ce is assumed short	$\omega_1 = 1 / (R_{eq1} C_{e1}) = 270$ r/s or $f_1 = 43$ Hz
If Ce is assumed open	$\omega_1 = 1 / (R_{eq1} C_{e1}) = 212$ r/s or $f_1 = 34$ Hz
	$\omega_2 = 1 / (R_{eq2} C_{e2}) = 0$ r/s or $f_2 = 0$ Hz
	$\omega_s = 1 / (R_s C_s) = 100000000$ r/s or $f_s = 15923567$ Hz
	$\omega_{e1} = 1 / (R_{eq} C_e) = 100027188$ r/s or $f_{e1} = 15927896$ Hz
	$C_T = 3253$ pF
	$R_{eq} = 115$ ohm
	$\omega_h = 1 / (R_{eq} C_T) = 2669314$ r/s or $f_h = 0.425$ MHz
	$k = A_{vmid} \omega_s \omega_{e1} = -134.47$ V/V

10000	42.57001537	-7.99796E-05	0	42.57249852	-0.00240:
31630	42.54850757	-7.99437E-06	0	42.57249853	-0.02398:
100000	42.33853153	-7.99803E-07	0	42.57249861	-0.23396:
316300	40.6586721	-7.99438E-08	0	42.57249945	-1.91382:
1000000	34.42003342	-7.99803E-09	0	42.57250779	-8.15247:
3163000	25.06167889	-7.99437E-10	0	42.57258812	-17.5109:
10000000	15.134129	-7.99804E-11	0	42.57316623	-27.4390:
31630000	5.140416152	-7.99427E-12	0	42.57438221	-37.4339:
100000000	-4.85647514	-8.00392E-13	0	42.57480135	-47.4312:
316300000	-14.8583359	-8.00392E-14	0	42.57485378	-57.4331:
1E+09	-24.8563397	-8.67895E-15	0	42.57485916	-67.431:

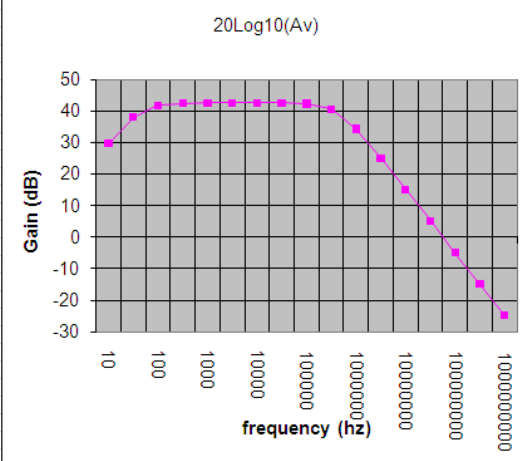

$$v_o/v_s = \frac{k (j\omega/\omega_1) (j\omega/\omega_2) (j\omega/\omega_3+1)}{(j\omega/\omega_1+1) (j\omega/\omega_2+1) (j\omega/\omega_4+1) (j\omega/\omega_h+1)}$$