

**ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING**

MOS Inverters

Dr. Lynn Fuller

Webpage: <http://people.rit.edu/lffee>

Microelectronic Engineering

Rochester Institute of Technology


82 Lomb Memorial Drive

Rochester, NY 14623-5604

Tel (585) 475-2035


Email: Lynn.Fuller@rit.edu

 Department webpage: <http://www.microe.rit.edu>



OUTLINE

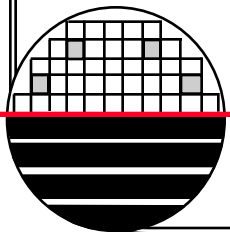
Introduction
Voltage Transfer Curve (VTC)
Noise Margin
Inverter Current vs. V_{in}
PMOS Inverter
NMOS Inverter
CMOS Inverter
Pseudo NMOS Inv, NAND and NOR
References
Homework



INTRODUCTION

There are many ways to make an inverter. In this document we will investigate various MOS inverters, their voltage transfer curve, current, noise margin, speed etc. The inverter is the simplest logic gate to analyze and can give useful results for the comparison of different inverter designs and fabrication technologies.



SYMBOL

 



TRUTH TABLE

V_{IN}	V_{OUT}
0	1
1	0


INVERTER TYPES - V_{OUT} VS V_{IN} (VTC)

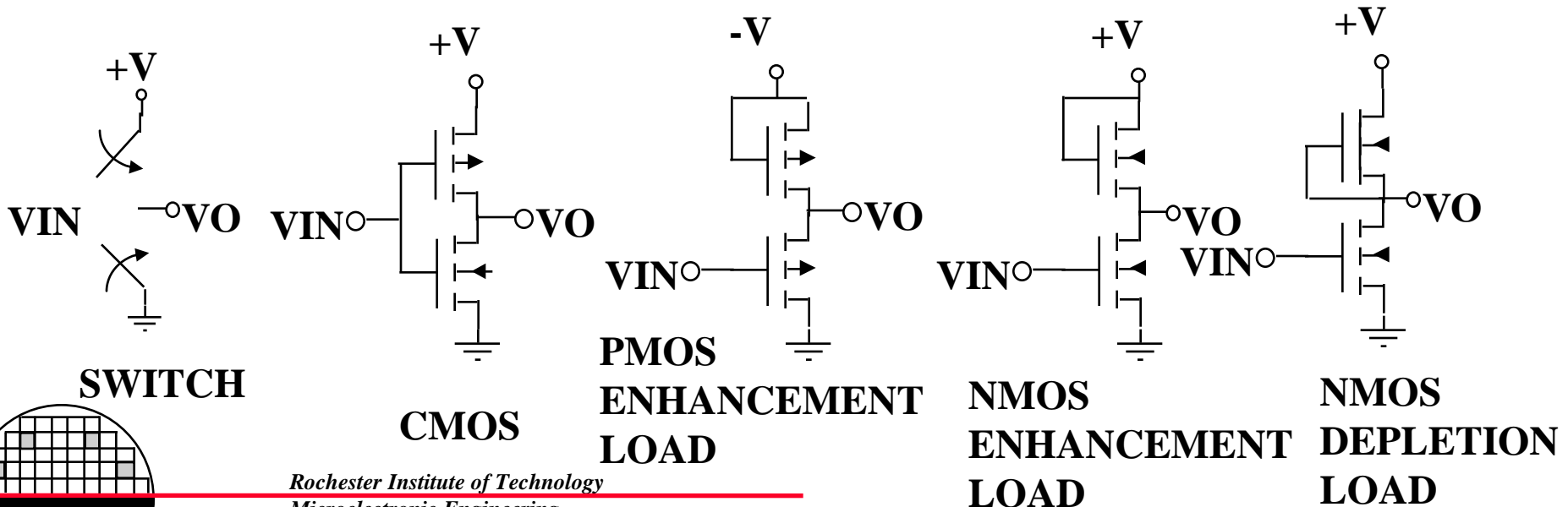 

  VOLTAGE TRANSFER CURVE NMOS-RESISTOR LOAD





RESISTOR LOAD

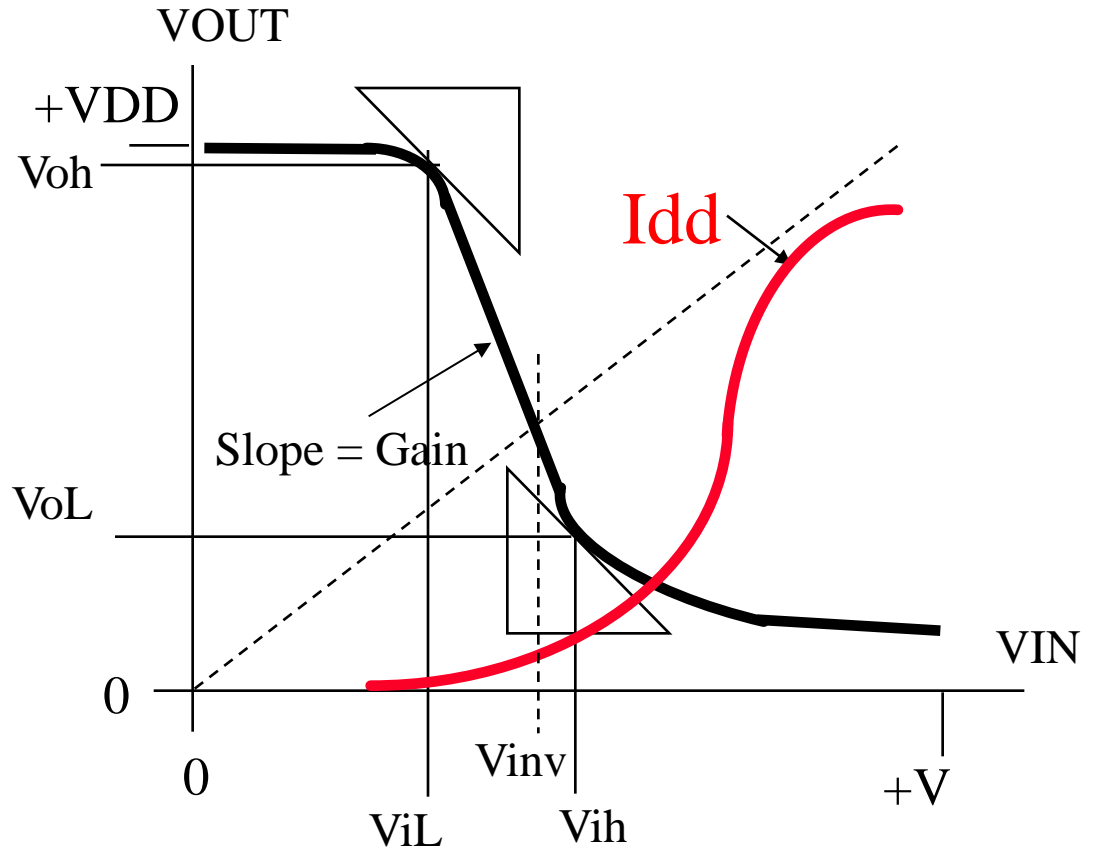

NML, noise margin low, $\Delta 0 = V_{iL} - V_{oL}$

NMH, noise margin high, $\Delta 1 = V_{oH} - V_{iH}$


CALCULATION OF VTC

 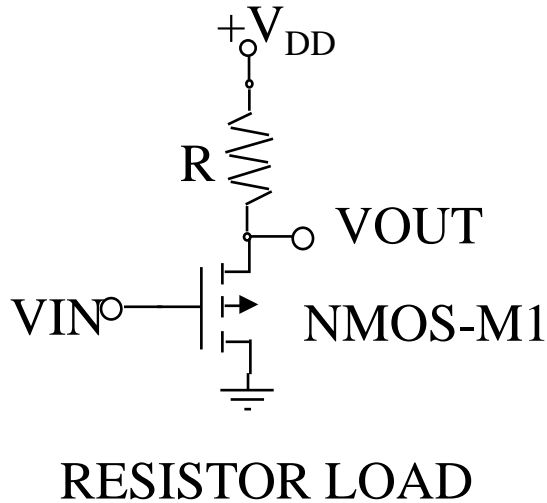


First figure out if the transistor is
 sub-threshold or off, $V_{gs} < V_{th}$ and $V_{gd} < V_{th}$
 non-saturation, $V_{gs} > V_{th}$ and $V_{gd} > V_{th}$
 saturation region, $V_{gs} > V_{th}$ and $V_{gd} < V_{th}$

Note: $V_{in} = V_{gs}$, $V_{out} = V_{ds}$, therefore $V_{gd} = V_{in} - V_{out}$
 V_{th} might be +1 volt

CALCULATION OF VTC

 

RESISTOR LOAD

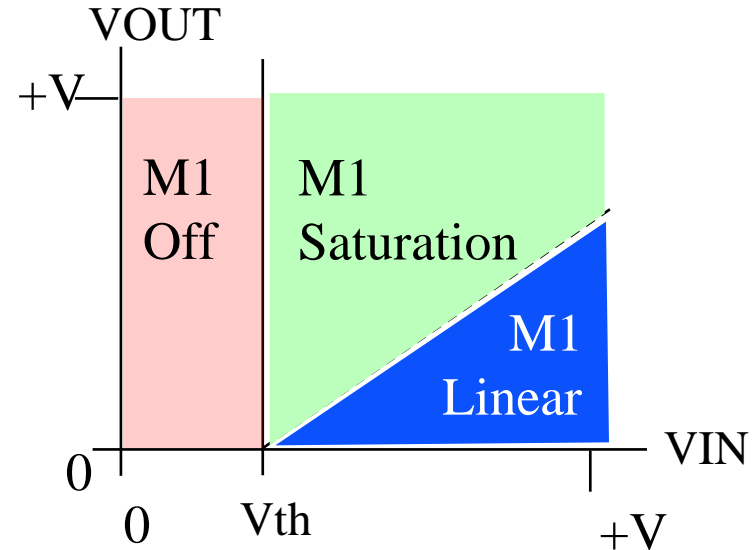

Next calculate $V_{out} = V_{DD} - I_D R$ using the correct equation for I_D for the transistor depending on region of operation

Linear (Non-Saturation)

$$I_D = \frac{\mu W C_{ox}'}{L} (V_g - V_t - V_d/2) V_d$$

Saturation

$$I_D = \frac{\mu W C_{ox}'}{2L} (V_g - V_t)^2$$

$$C_{ox}' = C_{ox}/\text{Area} = \epsilon_0 \epsilon_r / X_{ox}$$

CALCULATION OF VTC

$$M1 \text{ in Saturation } V_{out} = V_{DD} - R I_D = V - R \frac{\mu W C_{ox}' (V_{in} - V_t)^2}{2L}$$

$$C_{ox}' = C_{ox}/\text{Area} = \epsilon_0 \epsilon_r / X_{ox}$$

$$\epsilon_0 = 8.85e-14 \text{ F/cm}$$


$\epsilon_r = 3.9$ for oxide

X_{ox} = gate oxide thickness

W = width of MOSFET

L = Length of MOSFET

V_t = Threshold Voltage

 

CALCULATION OF VTC

M1 in Non-Saturation $V_{out} = V_{DD} - I_D R$

$$V_{out} = V_{DD} - I_D R = V_{DD} - \left(\frac{R \mu W C_{ox}}{L} \right) (V_g - V_t - V_d/2) V_d$$

$\rightarrow K_X$

$$V_o = V_{DD} - R K_X (V_{in} - V_t - V_o/2) V_o$$

$$V_o = V_{DD} - R K_X (V_{in} - V_t) V_o - R K_X V_o^2/2$$

$$0 = V_{DD} - R K_X (V_{in} - V_t - 1) V_o - R K_X V_o^2/2$$

quadratic formula


$$\mathbf{a x^2 + b x + c = 0}$$

$$\mathbf{x = -b \pm \sqrt{b^2 - 4ac}}$$

CALCULATION OF VTC


M1 in Non-Saturation $V_{out} = b^2 \pm \sqrt{b^2 - 2V_{DD}/KxR}$

$$b = (V_{in} - V_t + 1/KxR)$$

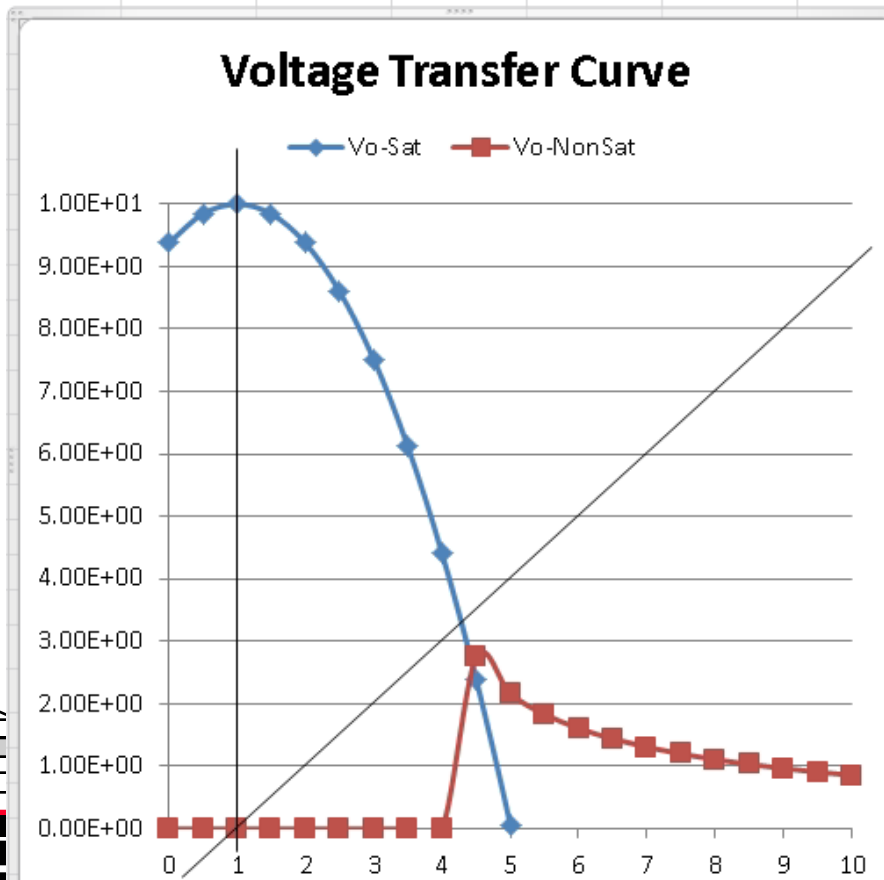


V _{in}	V _{o-Sat}	V _{o-NonSat}	b	ID - Sat
0	9.38E+00	#NUM!	-1.95E-01	6.21E-04
0.5	9.84E+00	#NUM!	3.05E-01	1.55E-04
1	1.00E+01	#NUM!	8.05E-01	0.00E+00
1.5	9.84E+00	#NUM!	1.30E+00	1.55E-04
2	9.38E+00	#NUM!	1.80E+00	6.21E-04
2.5	8.60E+00	#NUM!	2.30E+00	1.40E-03
3	7.51E+00	#NUM!	2.80E+00	2.49E-03
3.5	6.12E+00	#NUM!	3.30E+00	3.88E-03
4	4.41E+00	#NUM!	3.80E+00	5.59E-03
4.5	2.39E+00	2.74E+00	4.30E+00	7.61E-03
5	5.97E-02	2.16E+00	4.80E+00	9.94E-03
5.5	-2.58E+00	1.83E+00	5.30E+00	1.26E-02
6	-5.53E+00	1.61E+00	5.80E+00	1.55E-02
6.5	-8.79E+00	1.44E+00	6.30E+00	1.88E-02
7	-1.24E+01	1.31E+00	6.80E+00	2.24E-02
7.5	-1.62E+01	1.20E+00	7.30E+00	2.62E-02
8	-2.04E+01	1.11E+00	7.80E+00	3.04E-02
8.5	-2.49E+01	1.03E+00	8.30E+00	3.49E-02
9	-2.98E+01	9.67E-01	8.80E+00	3.98E-02
9.5	-3.49E+01	9.09E-01	9.30E+00	4.49E-02
10	-4.03E+01	8.58E-01	9.80E+00	5.03E-02

CALCULATION OF VTC

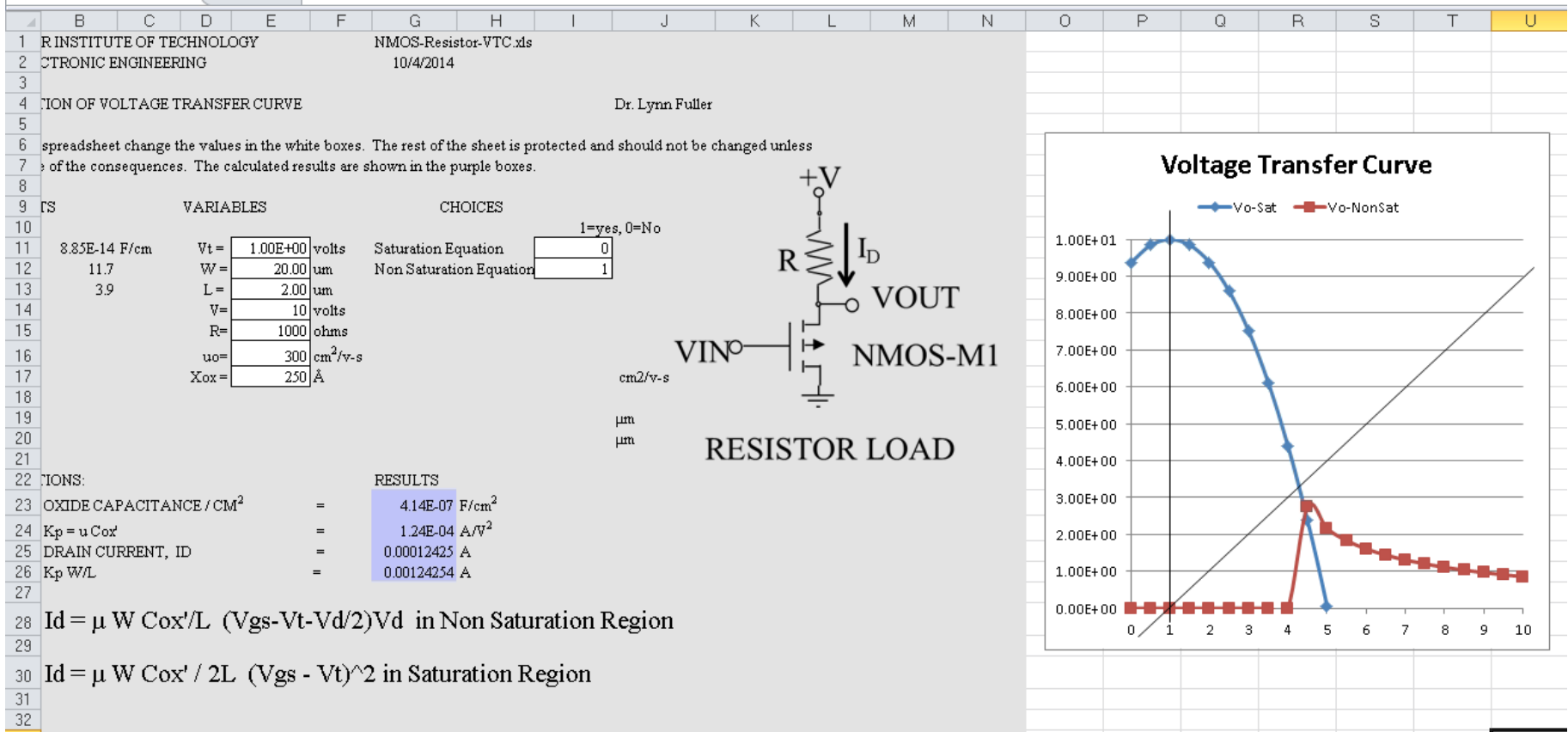

Note: Equations only valid in specific regions

LTSPICE – RESISTOR LOAD INVERTER - VTC

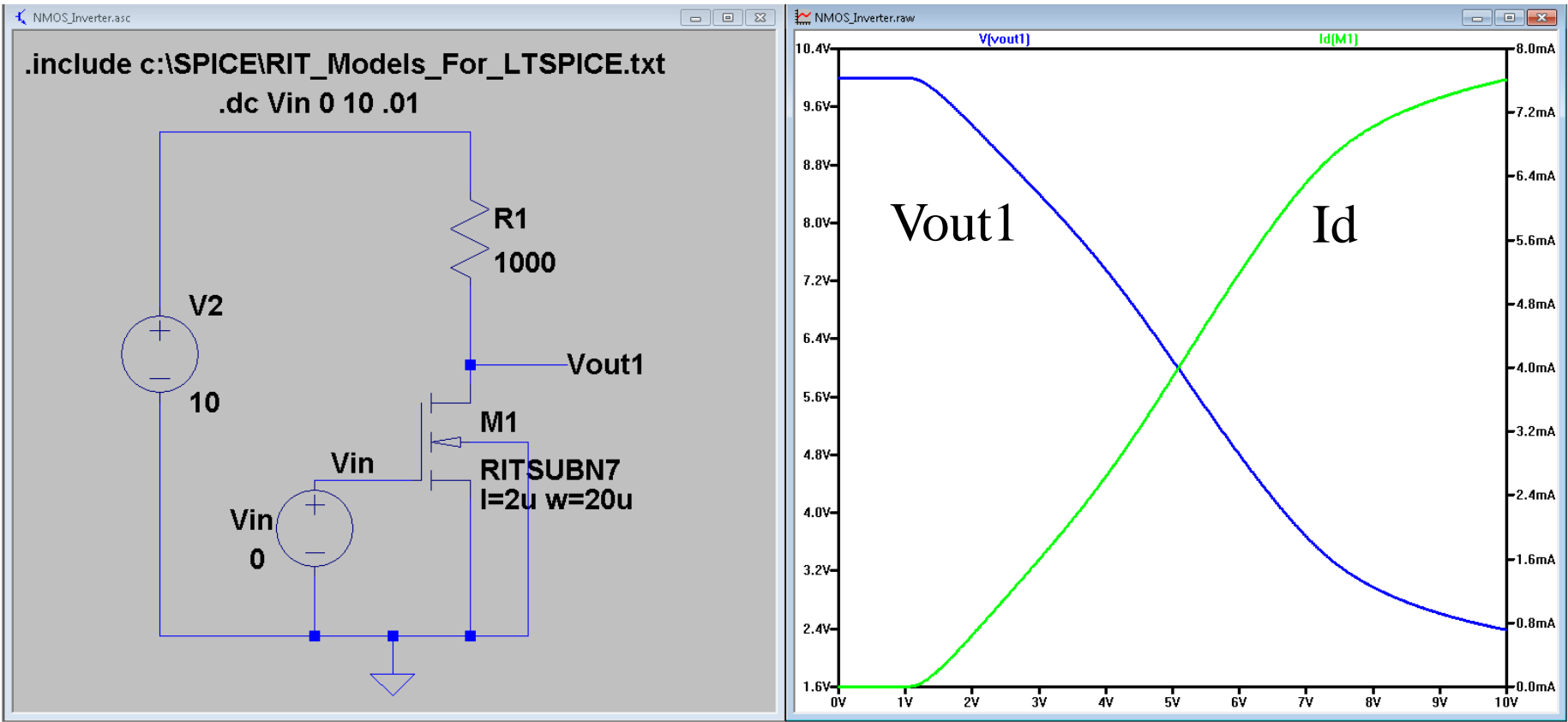

CALCULATION OF NOISE MARGINS

Approach

Take derivative set equal to -1


find V_{IL} and V_{IH}

V_{OH} and V_{OL}

Find point where $V_{in} = V_{out}$

Find I

Find Power

 

SPICE CALCULATIONS FOR NOISE MARGINS

$RL = 1K$

$V_{IL} = 3.31$

$V_{IH} = 6.95$

$V_{OH} = 8.09$

$V_{OL} = 3.37$


$\Delta 0 = V_{IL} - V_{OL}$

$= 3.31 - 3.73 = -0.42$

$\Delta 1 = V_{OH} - V_{IH} =$

$= 8.09 - 6.95 = 1.14$

Max Gain = -1.32

 

SPICE CALCULATIONS FOR NOISE MARGINS

$R_L = 10K$

$V_{IL} = 1.0$

$V_{IH} = 2.91$


$V_{OH} = 10.0$

$V_{OL} = 0.91$

$\Delta 0 = V_{IL} - V_{OL}$
 $= 1.0 - 0.91 = 0.08$



$\Delta 1 = V_{OH} - V_{IH} =$
 $= 10 - 2.91 = 7.09$

Max Gain = -7.2

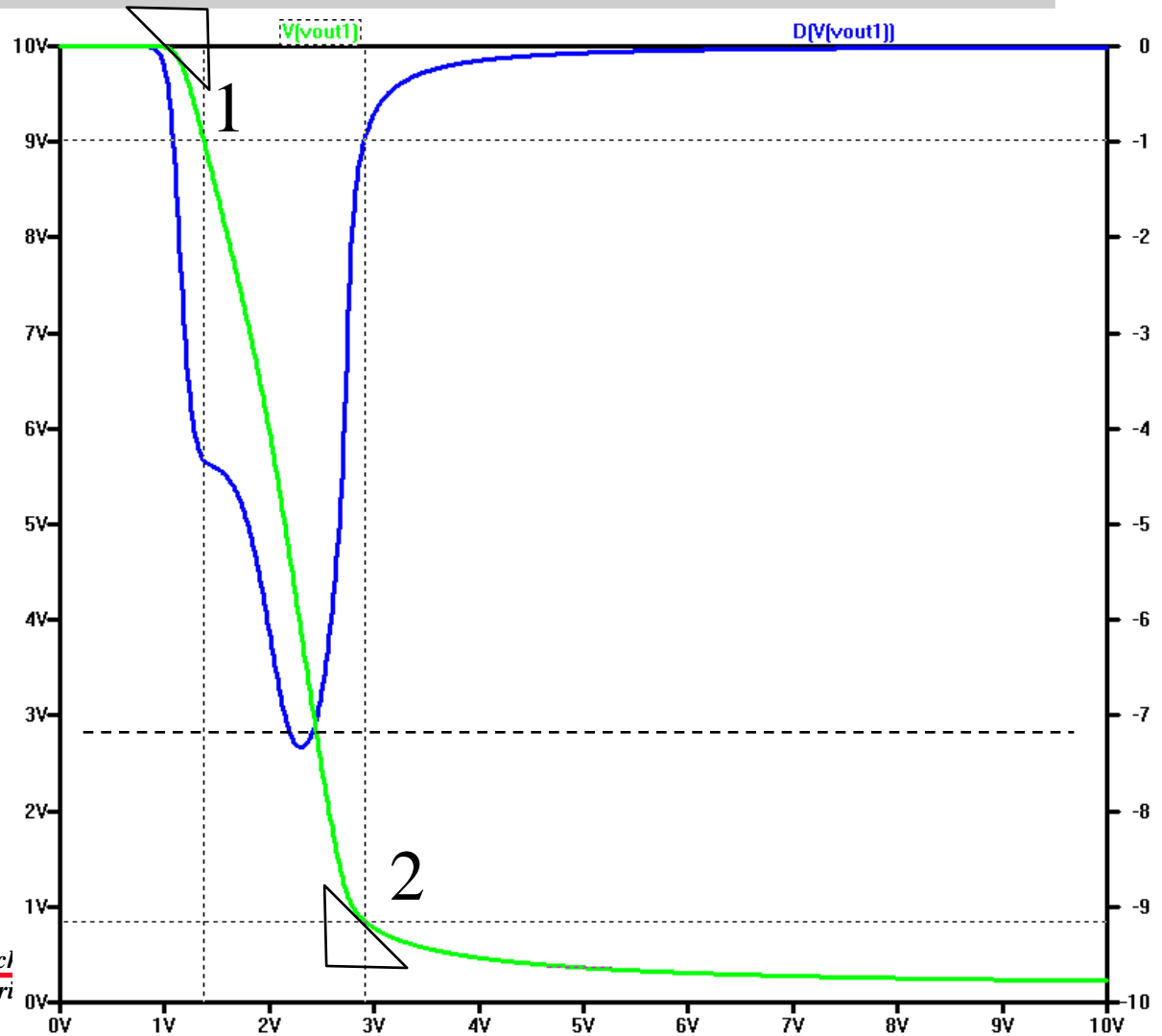


Rochester Institute of Technol
 Microelectronic Engineeri

 
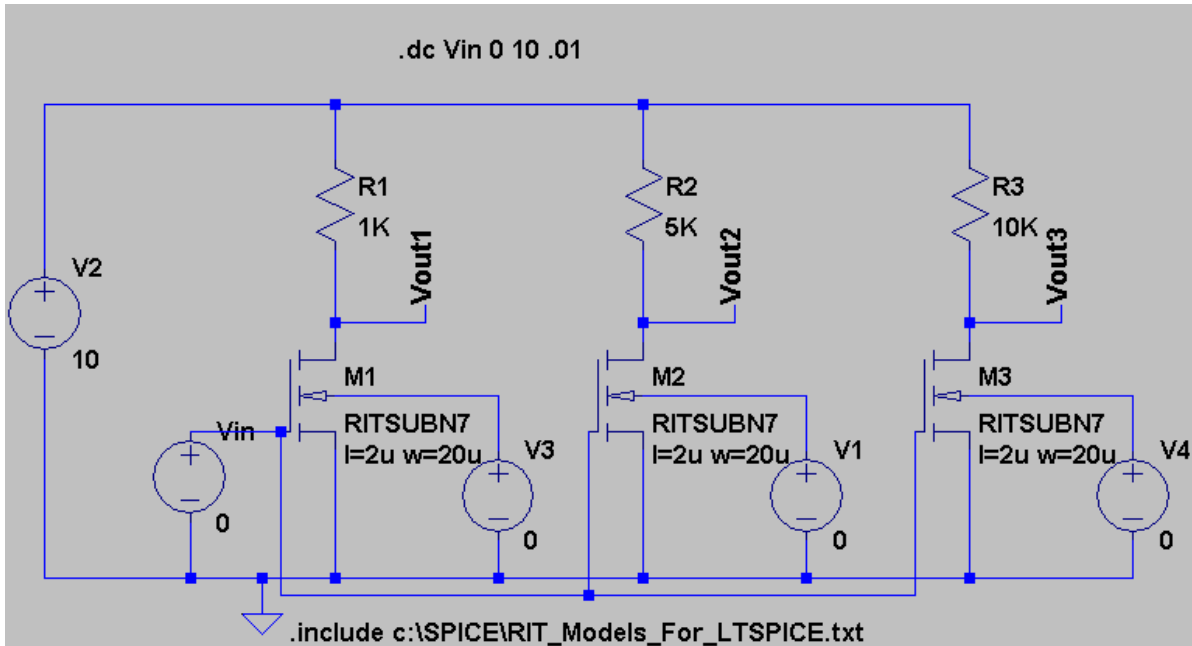
LTSPICE - INVERTER VTC – FOR DIFFERENT RL



LTSPICE – INVERTER VTC FOR DIFFERENT W

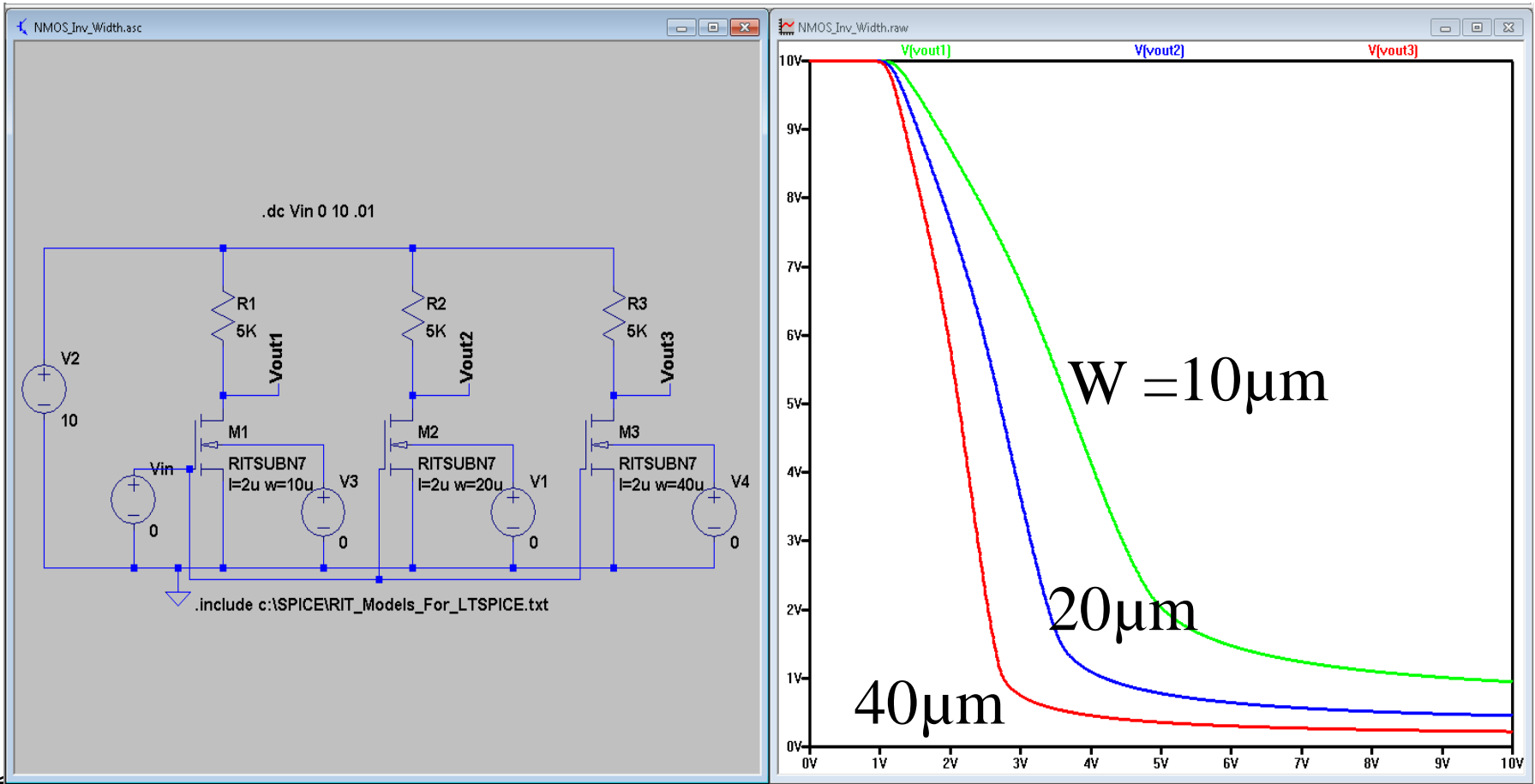

VTC PMOS INVERTER- PMOS ENHANCEMENT LOAD

 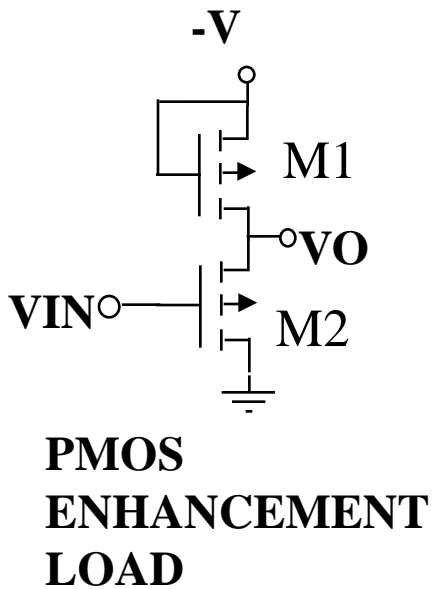

$$\text{Gain} = \sqrt{\frac{W2/L2}{W1/L1}}$$


M2 is the switch and M1 is the load. The load limits the current when M2 is on. The load could be a resistor but a PMOS transistor with gate connected to the drain is smaller in size and also limits current. See the I-V characteristics. In the first quadrant the transistor approximates the resistor. However, Vout high is below VDD by the threshold voltage of M1

VTC PMOS INVERTER- PMOS ENHANCEMENT LOAD

Note: Supply and input V is negative


$I=40e-6$ $w=20e-6$ $ad=320e-12$ $as=320e-12$ $pd=100e-6$ $ps=100e-6$

.dc V1 0 -10 -0.01

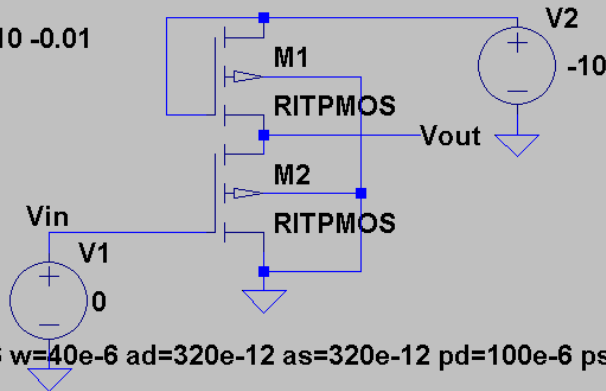



$I=20e-6$ $w=40e-6$ $ad=320e-12$ $as=320e-12$ $pd=100e-6$ $ps=100e-6$
 
```
.MODEL RITPMOS PMOS (LEVEL=7 VERSION=3.1 CAPMOD=2 MOBMO
+TOX=5.0E-8 XJ=3E-6 NCH=1.00E15 NSUB=1.00E15 PCLM=5
+WINT=2.0E-7 LINT=2.26E-6 NGATE=5E20 VTH0=-1.77
+RSH=120 JS=3.35E-7 JSW=3.35E-7 CJ=1.8E-4 MJ=0.5 PB=0.88
+CJSW=4.97E-10 MJSW=0.5 PBSW=0.88
+CGSO=1.09E-10 CGDO=1.09E-10 CGBO=6.90E-10 )
```



-10 Volts is Logic High
0 Volts is Logic Low



VTC NMOS INVERTER- NMOS ENHANCEMENT LOAD

 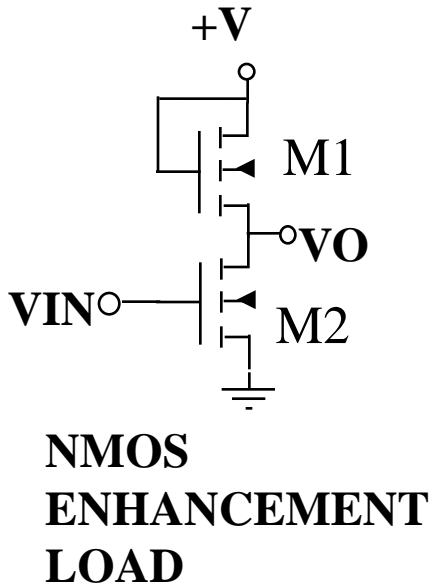

$$\text{Gain} = \sqrt{\frac{W2/L2}{W1/L1}}$$


M2 is the switch and M1 is the load. The load limits the current when M2 is on. The load could be a resistor but an NMOS transistor with gate connected to the drain is smaller in size and also limits current. See the I-V characteristics. In the first quadrant the transistor approximates the resistor. However, Vout high is below VDD by the threshold voltage of M1

VTC NMOS INVERTER- NMOS ENHANCEMENT LOAD

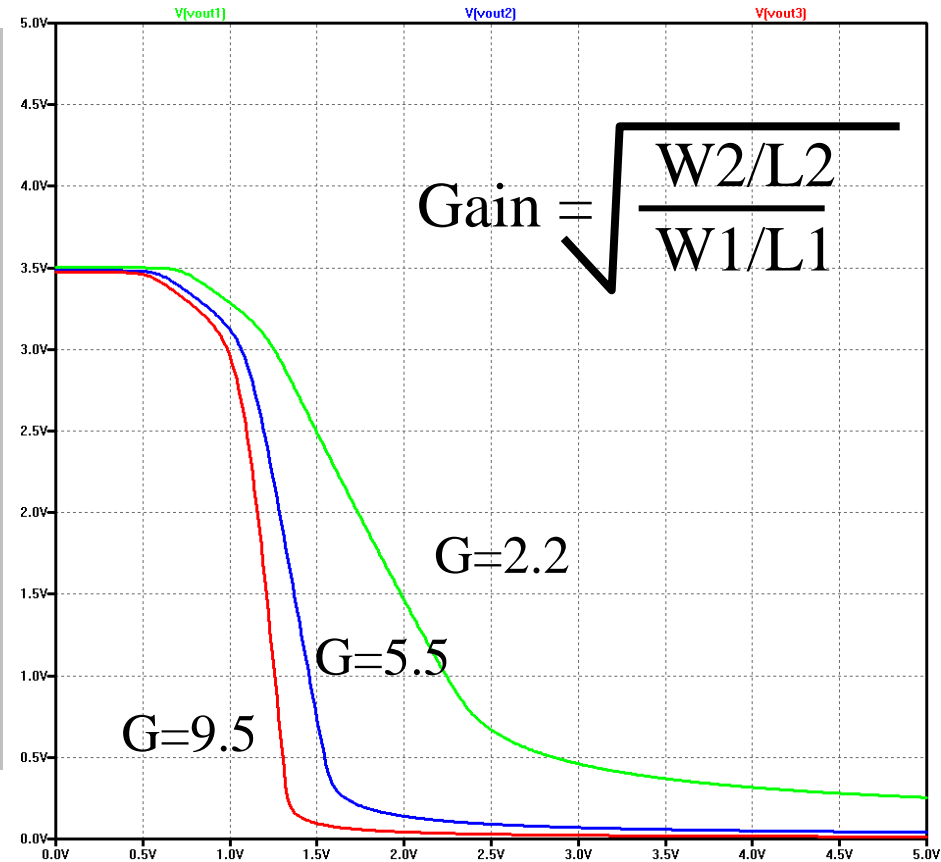 

Note: increasing L of the load is equivalent to increasing R of a resistor load, Vout high is $V_{DD} - V_{t_{M1}}$, Gain is shown.

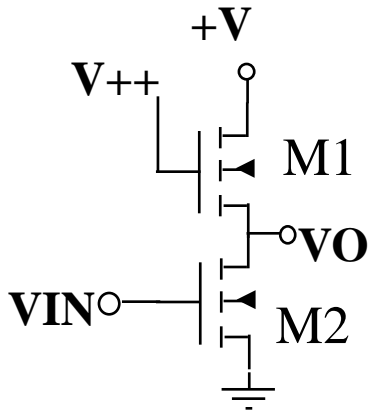VTC NMOS INVERTER- NMOS ENHANCEMENT LOAD AND V₊₊ GATE BIAS





NMOS
ENHANCEMENT
LOAD V₊₊ GATE BIAS

$$\text{Gain} = \sqrt{\frac{W_2/L_2}{W_1/L_1}}$$



M2 is the switch and M1 is the load. The load limits the current when M2 is on. The load could be a resistor but an NMOS transistor with gate connected to the drain is smaller in size and also limits current. See the I-V characteristics. In the first quadrant the transistor approximates the resistor. **M1 is always on because the gate voltage is above the supply voltage. V_{out} max is the supply voltage.**

 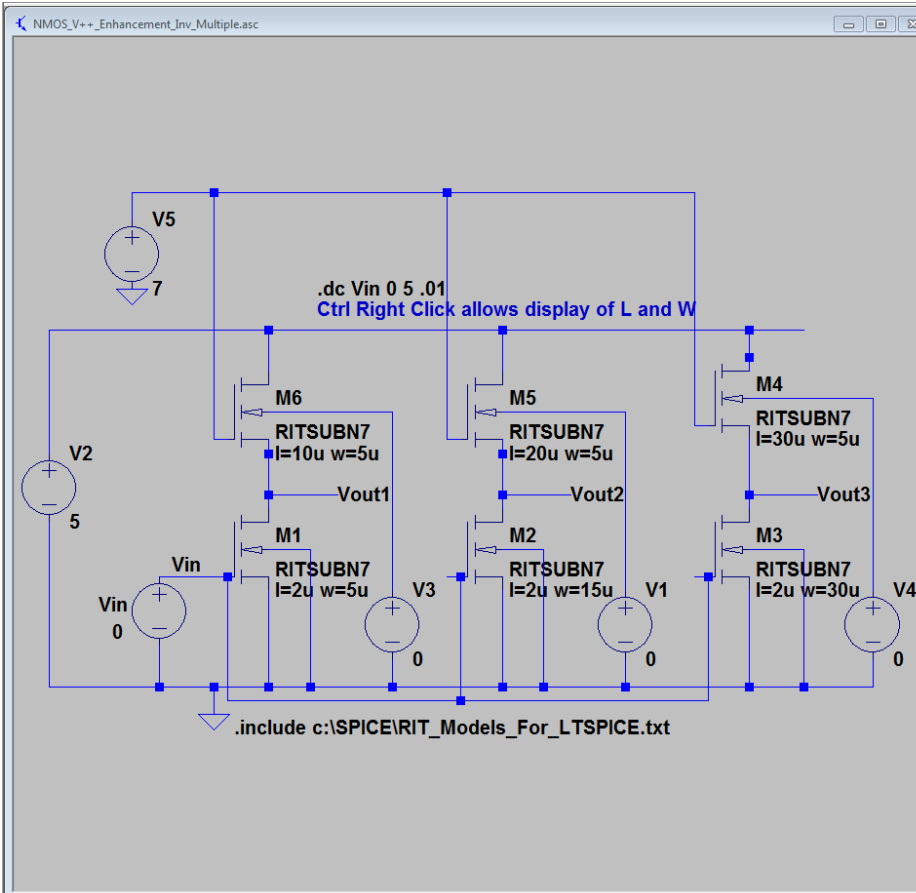VTC NMOS INVERTER- NMOS ENHANCEMENT LOAD AND V++ GATE BIAS




Note: increasing L of the load is equivalent to increasing R of a resistor load, **Vout high is Vdd**, Gain is shown.

VTC NMOS INVERTER – NMOS DEPLETION LOAD

 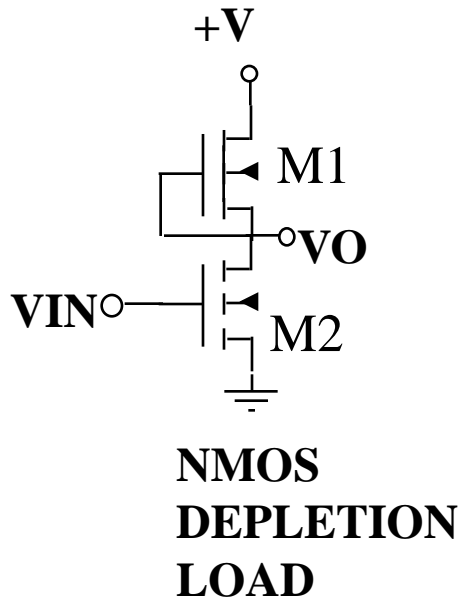

$$\text{Gain} = \sqrt{\frac{W2/L2}{W1/L1}}$$

M2 is the switch and M1 is the load. The load limits the current when M2 is on. The load could be a resistor but an NMOS transistor with gate connected to the drain is smaller in size and also limits current. See the I-V characteristics. In the first quadrant the transistor approximates the resistor. **M1 is always on because its threshold voltage is set to zero or slightly negative by ion implant.**

 


VTC NMOS INVERTER – NMOS DEPLETION LOAD

* From Sub-Micron CMOS Manufacturing Classes in MicroE ~ 1um Technology

```
.MODEL RITSUBN7E NMOS (LEVEL=7
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
+VTH0=-1.0 U0= 600 WINT=2.0E-7 LINT=1E-7
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```



Need a new SPICE model for the Enhancement mode NMOS. New model name and negative VTH0. Using ion implant the VTH0 can be made negative.

VTC NMOS INVERTER – NMOS DEPLETION LOAD

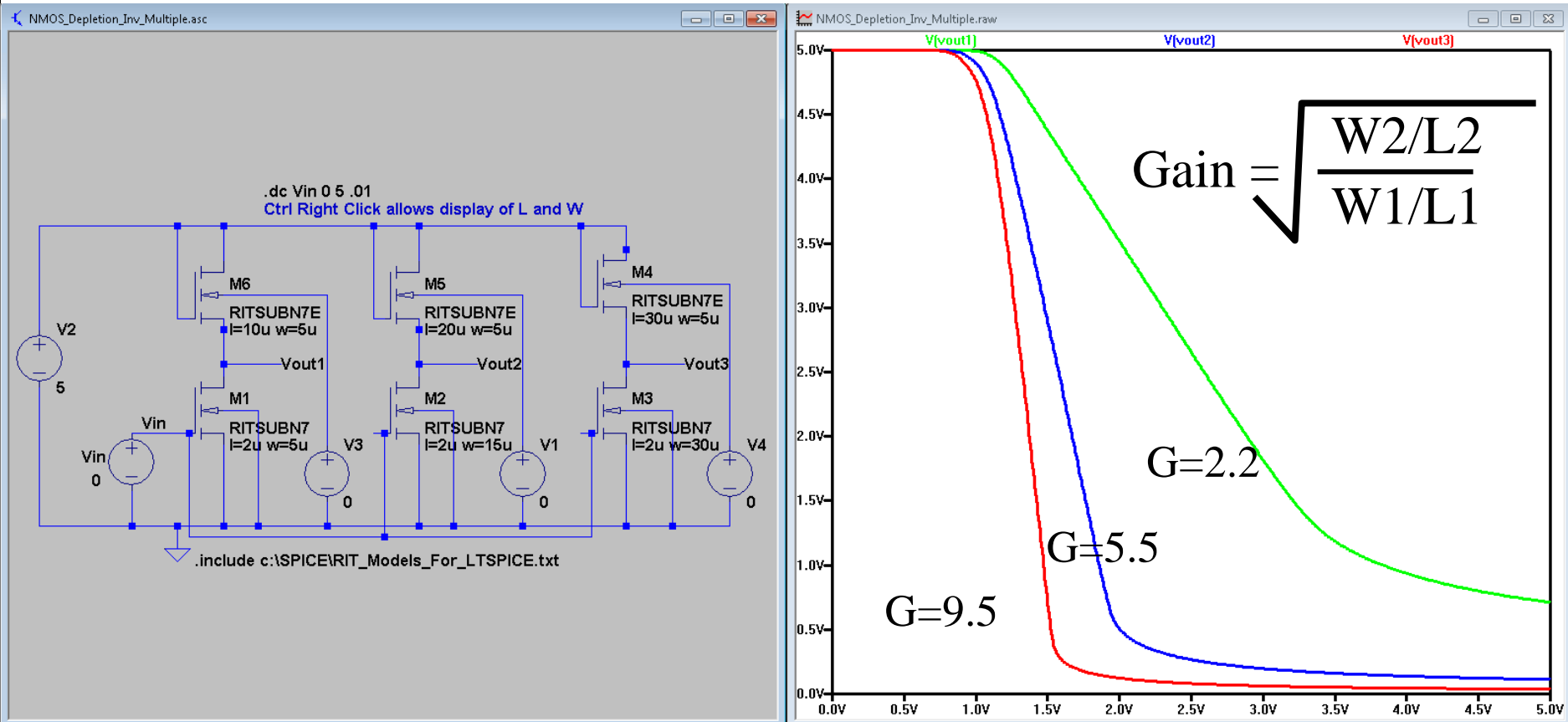

Note: increasing L of the load is equivalent to increasing R of a resistor load, **Vout high is Vdd**, Gain is shown.



CMOS - CALCULATION OF VTC

 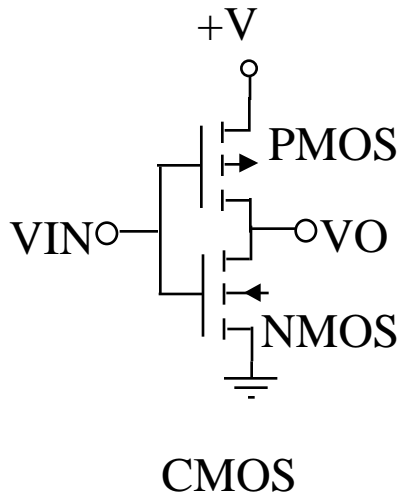


First figure out if the transistor is
 sub-threshold or off, $V_{gs} < V_{th}$ and $V_{gd} < V_{th}$
 non-saturation, $V_{gs} > V_{th}$ and $V_{gd} > V_{th}$
 saturation region, $V_{gs} > V_{th}$ and $V_{gd} < V_{th}$

Note: $V_{in} = V_{gs}$, $V_{out} = V_{ds}$, therefore $V_{gd} = V_{in} - V_{out}$
 V_{th} might be +1 volt

CMOS INVERTER

  


CMOS

 

NML, noise margin low, $\Delta 0 = V_{iL} - V_{oL}$
 NMH, noise margin high, $\Delta 1 = V_{oH} - V_{iH}$

LTSPICE – CMOS INVERTER

 


NML, noise margin low, $\Delta 0 = V_{iL} - V_{oL} = 2.2 - 0.5 = 1.7$

NMH, noise margin high, $\Delta 1 = V_{oH} - V_{iH} = 4.5 - 2.5 = 2.0$


COMPARISON OF 10u, 1u AND 100n CMOS INVERTERS

VDD = 5 volts

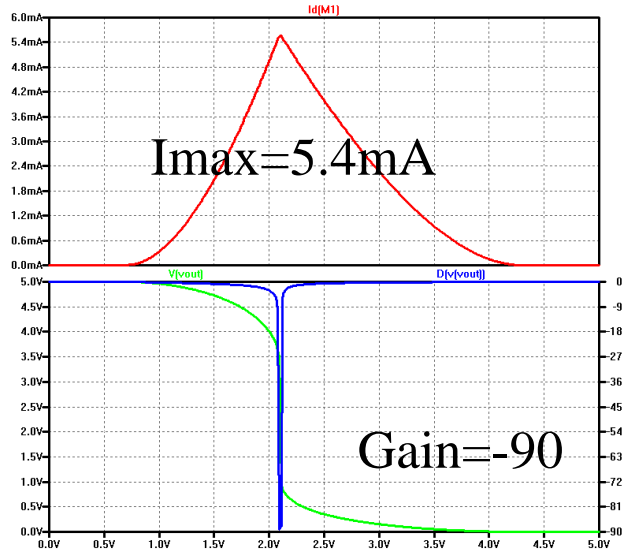


RITALDN3/RITALDP3
 $L = 10\mu$ $W = 880\mu$
 $L = 10\mu$ $W = 880\mu$

VDD = 3.3 volts

 

RITSUBN7/RITSUBP7
 $L_n = 1\mu$ $W_n = 2\mu$
 $L_p = 1\mu$ $W_p = 2\mu$




VDD = 2.5 volts

 


EECMOSN/EECMOSP
 $L_n = 180\text{n}$ $W_p = 200\text{n}$
 $L_n = 180\text{n}$ $W_p = 200\text{n}$

PSEUDO – CMOS

   There are situations where we want a large number of inputs. Rather than have CMOS where there will be many transistors in series (which will not work) we can use a single PMOS transistor that is always on.




PSEUDO – CMOS INVERTER

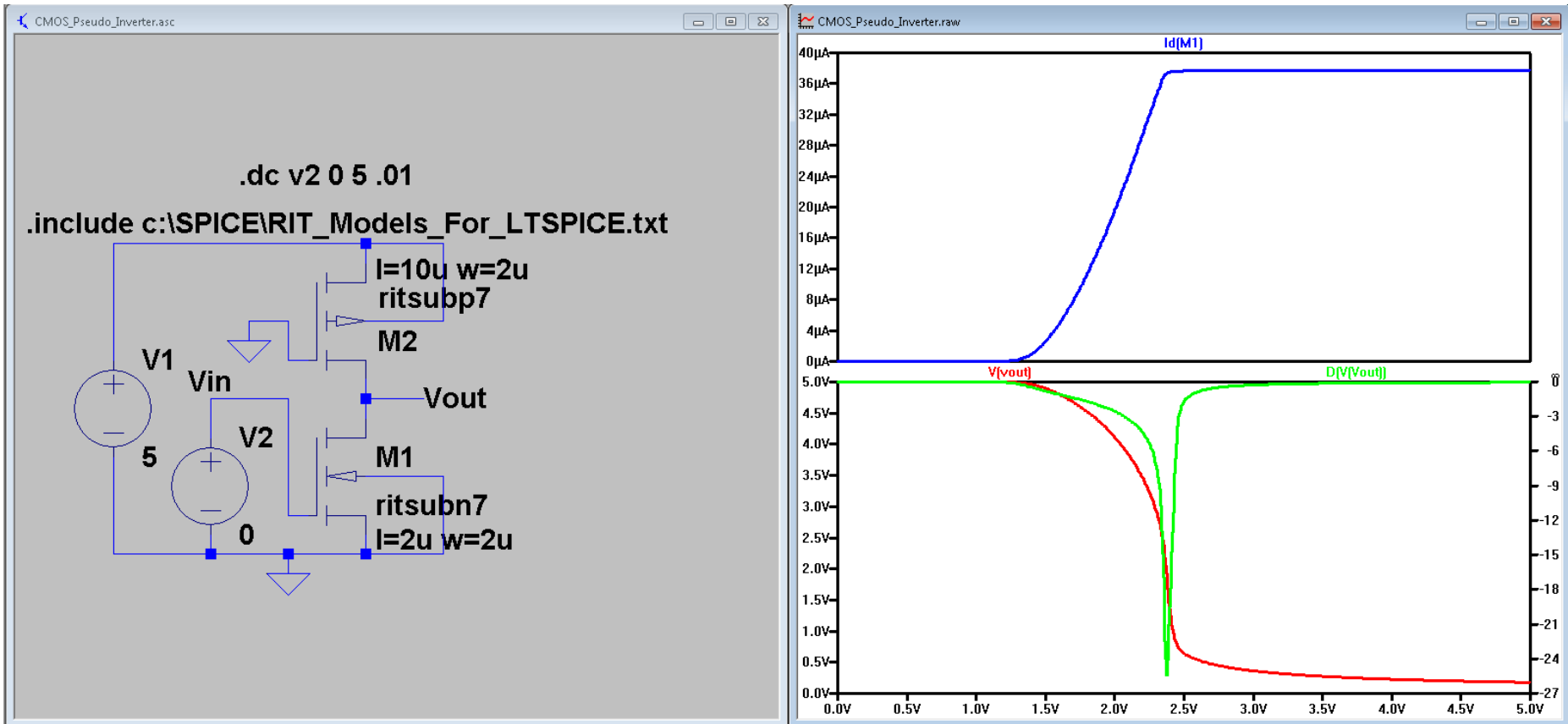


No advantages over CMOS inverter
 $\Delta 0=1.0$, $\Delta 1=3.0$

PSEUDO – CMOS NOR

 

Note: noise margin $\sim \Delta 0=1.3$, $\Delta 1=2.8$
max current drive 50uA
static current not zero for $V_{out}=\text{low}$
gate delay ?


CMOS NOR-4

 

Note: noise margin $\sim \Delta 0=1.2$, $\Delta 1=3.2$
max current drive 50 μA
static current is zero
gate delay ?

REFERNCES


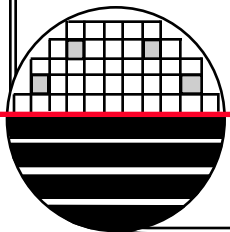
1. Hodges Jackson and Saleh, Analysis and Design of Digital Integrated Circuits, Chapter 4.
2. Sedra and Smith, Microelectronic Circuits, Sixth Edition, Chapter 13.
3. Dr. Fuller's Lecture Notes, <http://people.rit.edu/lffeee>



HOMWORK – MOS INVERTERS

1. Using SPICE obtain the VTC for a CMOS inverter with gate lengths of $\sim 1\mu\text{m}$. Let the width of both transistors be $2\mu\text{m}$. Determine the noise margins. Determine the maximum current and voltage gain. (Use the SPICE models given below) Make appropriate assumptions.
2. Repeat problem 1 for gate L and W of $\sim 200\text{nm}$.
3. Given the layout shown below of a CMOS inverter find L, W, AD, AS, PD, PS.
4. The schematic below is for a tristate inverter. This device should be able to make the output high or low when the enable (EN) is high. When the enable is low the inverter is effectively disconnected from the load (high impedance, Z). Use SPICE to show that this circuit operates as intended.

INVERTER LAYOUT

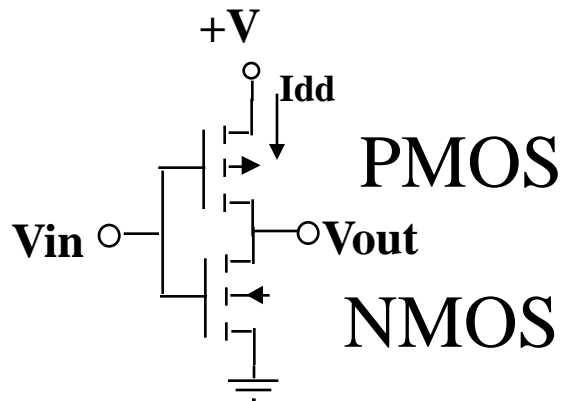
 


CMOS


TRUTH TABLE

VIN	VOUT
0	1
1	0

  
*Rochester Institute of Technology
Microelectronic Engineering*



 $W = 40 \mu\text{m}$
 $L_{\text{poly}} = 2.0 \mu\text{m}$




HOMWORK – MOS INVERTERS

 

Tristate Inverter

EN	VIN	VO
0	0	High Z
0	1	High Z
1	0	1
1	1	0

 

SPICE MODELS FOR MOSFETS

*SPICE MODELS FOR RIT DEVICES - DR. LYNN FULLER 4-10-2014

*LOCATION DR.FULLER'S WEBPAGE - <http://people.rit.edu/lffeee/CMOS.htm>

*

*Used in **Electronics II** for CD4007 inverter chip

*Note: Properties L=1u W=200u

```
.MODEL RIT4007N7 NMOS (LEVEL=7
```

```
+VERSION=3.1 CAPMOD=2 MOBMOD=1
```

```
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
```

```
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7
```

```
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
```

```
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
```

```
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*Used in **Electronics II** for CD4007 inverter chip

*Note: Properties L=1u W=200u

```
.MODEL RIT4007P7 PMOS (LEVEL=7
```

```
+VERSION=3.1 CAPMOD=2 MOBMOD=1
```


```
+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8
```

```
+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7
```

```
+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
```

```
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94
```
 
```
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```



SPICE MODELS FOR MOSFETS

*Used for ALD1103 chips

*Note: Properties L=10u W=880u

```
.MODEL RITALDN3 NMOS (LEVEL=3
```

```
+TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7
```

```
+U0= 1215 VTO=0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5
```

```
+NSUB=1.57E16 +XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11
```

```
+CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)
```

*

*Used for ALD1103 chips

*Note: Properties L=10u W=880u


```
.MODEL RITALDP3 PMOS (LEVEL=3
```

```
+TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7
```

```
+U0=550 VTO=-0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5
```

```
+NSUB=1.57E16 +XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11
```
 
```
+CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)
```



SPICE MODELS FOR MOSFETS

*4-4-2013 LTSPICE uses Level=8

*For **RIT Sub-CMOS 150 process with L=2u**

.MODEL RITSUBN8 NMOS (LEVEL=8

+VERSION=3.1 CAPMOD=2 MOBMOD=1

+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8

+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7

+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95

+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5

+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)

*

*4-4-2013 LTSPICE uses Level=8

*For **RIT Sub-CMOS 150 process with L=2u**

.MODEL RITSUBP8 PMOS (LEVEL=8

+VERSION=3.1 CAPMOD=2 MOBMOD=1


+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8

+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7

+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94

+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94

 +CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)



SPICE MODELS FOR MOSFETS

* From **Sub-Micron CMOS Manufacturing Classes in MicroE ~ 1um Technology**

```
.MODEL RITSUBN7 NMOS (LEVEL=7
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*From **Sub-Micron CMOS Manufacturing Classes in MicroE ~ 1um Technology**

```
.MODEL RITSUBP7 PMOS (LEVEL=7
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8
+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7
+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```

SPICE MODELS FOR MOSFETS

*4-4-2013 LTSPICE uses Level=8

* From **Electronics II EEEE482 FOR ~100nm Technology**

```
.model EECMOSN NMOS (LEVEL=8
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*4-4-2013 LTSPICE uses Level=8

* From **Electronics II EEEE482 FOR ~100nm Technology**

```
.model EECMOSP PMOS (LEVEL=8
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```

*

Rochester Institute of Technology
Microelectronic Engineering